

## BUILDING A 400MHz WIDE-BAND DIFFERENTIAL AMPLIFIER: IT'S A BREEZE WITH THE DIAMOND TRANSISTOR OPA660.

*By Christian Henn and Ernst Rau, Burr-Brown International GmbH*

In radio frequency (RF) technology, signals from oscilloscopes, monitors, transient recorders, and many other devices are usually connected to sensors and generators via coaxial lines. In any transmission, however, interference voltages caused by differences in potential between the sender and receiver and by electromagnetic interference distort the results, particularly when the signals being transmitted are sensitive and wide-band. Designers of this type of transmission system need shielded, symmetrical transmission lines and input differential amplifiers with high common-mode rejection, which bring home the signals without humming or radio interference.

Designing this type of differential amplifier used to be quite a chore, involving extensive and complicated hardware. But the development of new, monolithic ICs such as the Diamond Transistor OPA660 has changed all that. The OPA660 makes it easy to design a 400MHz differential amplifier offering -60dB common-mode rejection at a 1MHz frequency. This amplifier uses an open-loop amplifier structure with two identical high-impedance inputs and no feedback. The parameters such as wide bandwidth, stable operation, and excellent pulse processing, common-mode rejection, and harmonic distortion let the performance speak for itself.

### BASIC TRANSMISSION STRUCTURES

Figure 1 shows a symmetrical transmission path with signal voltage  $V_s$  and cable termination resistors  $R_{IN}$  and  $R_T$ . A symmetrical voltage source normally uses amplifiers with complementary outputs or transformers to balance or adapt the circuits. The relatively high-impedance input resistor  $R_b$  limits the input potential drift through the input bias currents ( $I_{BIAS}$ ), and the symmetrical differential amplifier input rejects interference voltages superimposed upon the input signal and its reference potential. The voltage-controlled

current source converts the symmetrical input voltage  $V_{IN}$  either into an output current or into the asymmetrical output voltage  $V_{OUT}$  when a voltage drop is present at the external resistor  $R_{OUT}$ .  $V_{IN}$  and  $V_{OUT}$  are related as follows:  $V_{OUT} = V_{IN} \cdot gm \cdot R_{OUT}$ , where  $gm$  is the transconductance of the operational transconductance amplifier (OTA). The buffer following the input amplifier decouples the low-impedance load resistor from the high-impedance OTA output.

Instead of symmetrical signal excitation, many applications use the type of transmission path shown in Figure 2. A single-ended signal voltage  $V_{IN}$  drives an asymmetrical coaxial cable terminated on both sides. In this structure as well, the symmetrical differential amplifier input rejects interference voltages superimposed on the signal.

### INSTRUMENTATION AMPLIFIER WITH FEEDBACK

OTAs and buffers have conventionally been designed using differential amplifiers as shown in Figure 3. The feedback path from the op amp output over  $R_4$  generates a relatively low-impedance inverting input, which is equal to the  $R_3$  resistor value. Inserting the buffer amplifier, BUF2, converts the low-impedance input to high impedance, while inserting the buffer amplifier, BUF1, optimizes the input symmetry and thus the common-mode rejection at DC and vs frequency.

The gain is  $R_4/R_3$  during signal excitation at the inverting input and  $1 + R_4/R_3$  during signal excitation at the noninverting input. A divider is inserted between  $R_1$  and  $R_2$  to compensate for these differing gains. Buffer 1 also synchronizes the signal delay times of the two inputs, which is important for good common-mode rejection at high frequencies. To achieve high common-mode rejection over frequency, it is important that the gain curve of the two input buffers be as identical as possible.

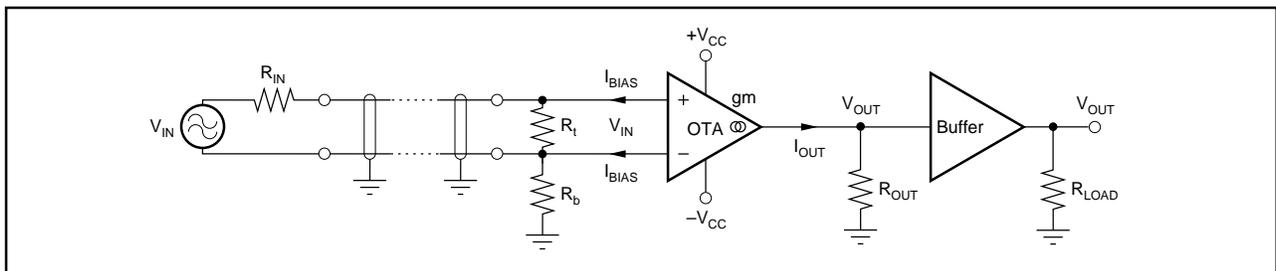


FIGURE 1. Basic Structure of a Symmetrical Transmission Path.

In addition to requiring more hardware, this type of system also has smaller bandwidth than the open-loop amplifier shown in Figure 2 due to the delay time in its amplifier feedback loop (phase shift).

**A SYNTHESIS: OPEN-LOOP AMPLIFIER USING THE DIAMOND TRANSISTOR**

The open-loop amplifier using the Diamond Transistor OPA660 and buffer amplifier BUF601 combines the best of

both worlds, offering better bandwidth than a normal open-loop amplifier, excellent pulse responses down to rise/fall times of 1ns, and reduced hardware. The basic concept is shown in Figure 4.

The gain can be determined according to the following equation:

$$V_{OUT} = V_{IN} \frac{R_{OUT}}{R_E + 2/gm}$$

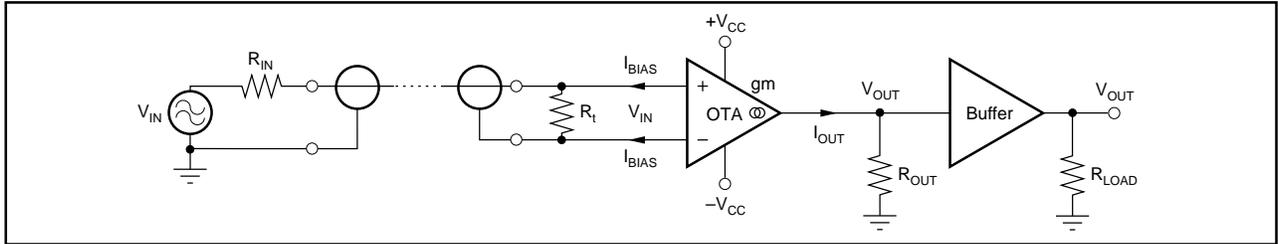


FIGURE 2. Signal Transmission Using an Asymmetrical Coaxial Cable and a Signal Voltage Referred to Ground.

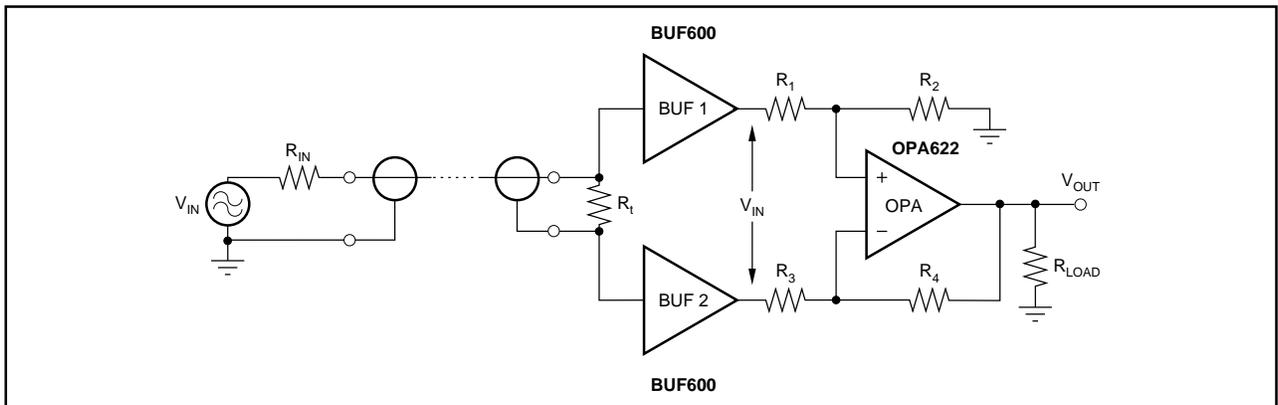


FIGURE 3. Instrumentation Amplifier with Feedback.

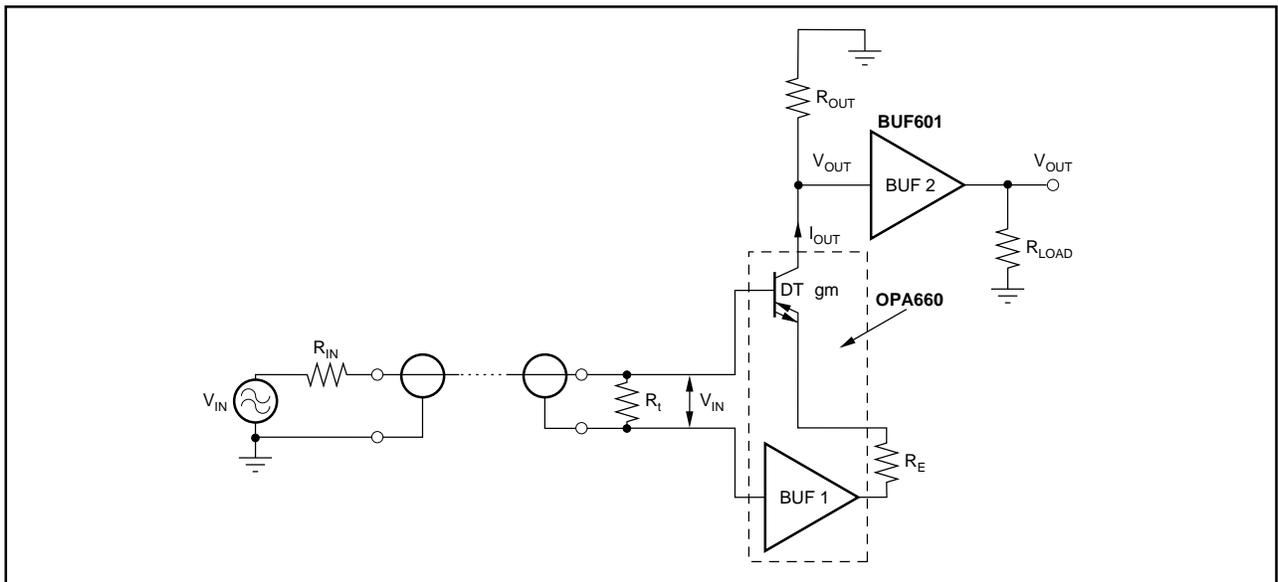


FIGURE 4. Wide-Band Open-Loop Amplifier.



## HIGH PROCESSING POWER, LOW POWER REQUIREMENTS

The most important job of a differential amplifier is to reject common-mode interference arising during the transmission of analog signals. The 400MHz differential amplifier using the OPA660 impressively demonstrates how easy it now is to design wide-band input amplifiers for test devices, monitors, transient recorders, and other RF devices. While achieving excellent parameters for bandwidth, common-mode rejection, and frequency response, the OPA660 and BUF601 also offer such low power consumption that the entire differential amplifier can be powered from a separate battery supply—a truly compact, high-performance alternative.

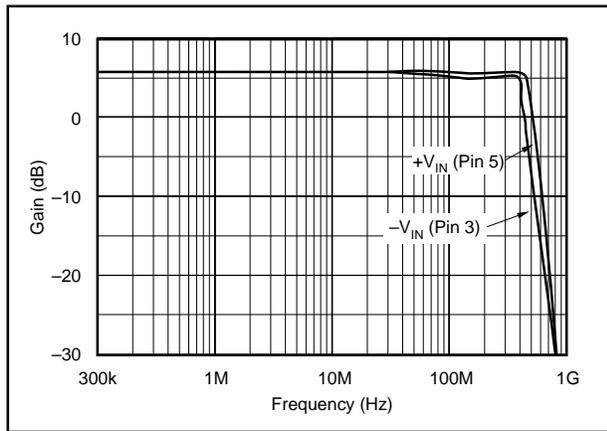


FIGURE 6. Frequency Responses of the Inputs In+ and In-.

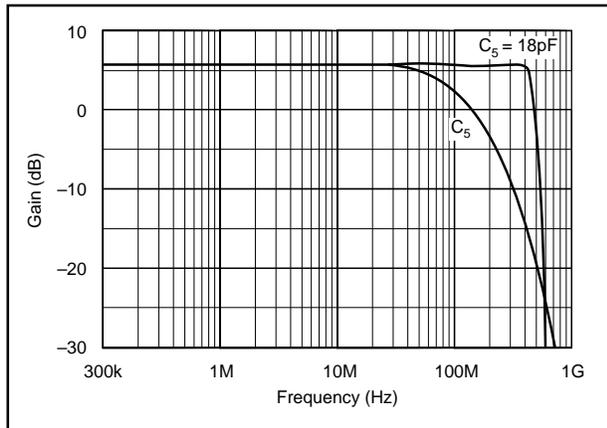


FIGURE 7. Impact of Capacitor  $C_s$  on the Bandwidth.

f	$V_{OUT}$	HARMONIC DISTORTION
10MHz	1Vp-p 1st Harmonic	-61dB
10MHz	1Vp-p 2nd Harmonic	-64dB
10MHz	2Vp-p 1st Harmonic	-57dB
10MHz	2Vp-p 2nd Harmonic	-55dB

TABLE II. Harmonic Distortion.

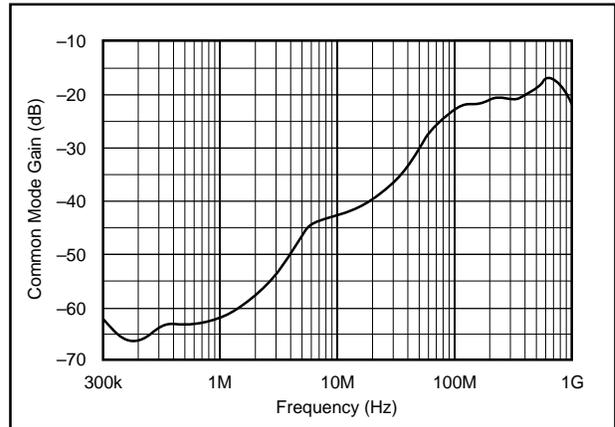


FIGURE 8. Common-Mode Gain.

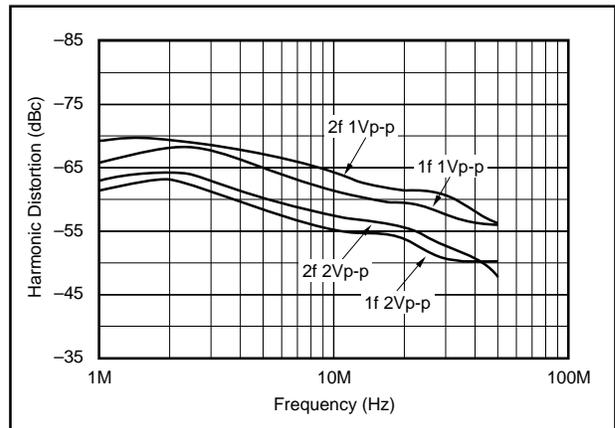


FIGURE 9. Harmonic Distortion.

## **IMPORTANT NOTICE**

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.