

Optimizing TPS6206x External Component Selection

Antonio Fadhel

PMP-DC/DC Low-Power Converters

ABSTRACT

The TPS6206x internal compensation network is optimized for an LC output filter composed of a 1- μ H inductor and a 10- μ F ceramic capacitor. The device is designed to operate with nominal inductor values of 1 μ H to 1.2 μ H and with ceramic capacitor values of 10 μ F to 22 μ F. By selecting the proper feedforward capacitor, a wider range of output inductors and capacitors can be used with the TPS6206x. Adjusting these three components can optimize the device for smaller solution size, faster load-step response, lower output voltage ripple, increased output current, and/or increased control loop stability. This application report can be used with any of the TPS62060, TPS62065, or TPS62067 3-MHz, synchronous step-down converters.

Reducing Solution Size

The output inductor is the largest component in the power supply, covering approximately 30% of the total area. Choosing an inductor with a smaller package has the greatest impact on the solution size. [Table 1](#) shows different LC filter combinations that have been tested with the TPS62065. A stable design can be achieved with inductances as low as 0.56 μ H.

[Table 1](#) was generated with extensive laboratory testing of the various inductor and capacitor values. The corner frequency ([Equation 1](#)) of each LC combination is listed in each cell. Cells shaded white are recommended by the data sheet. The data sheet's recommendations produce a recommended corner frequency between 31 kHz and 50.3 kHz. Other LC combinations that yield corner frequencies within this range are shaded in green and can produce stable designs with an appropriate feedforward capacitor (Cff). Cells shaded in grey have produced stable designs in the laboratory (with a Cff), whereas cells shaded in blue are unstable and not recommended. The data in [Table 1](#) is taken with a 5-V input and a 1.8-V output with a load current of 1.6 A.

$$\left(f_c = \frac{1}{2\pi\sqrt{LC}} \right) \tag{1}$$

Lower inductances are typically available in smaller packages. However, the inductor saturation current typically decreases with decreasing volume. With lower inductances, the ripple current in the inductor is higher, resulting in higher peak currents that can saturate the inductor or trip the IC's current limit. The inductor must be selected carefully so its saturation current is higher than the peak inductor current. Also, it is important to note that as the inductor volume decreases, ac and dc losses generally increase due to an increase in ripple current and DCR. An increase in these losses reduces the efficiency of the converter.


Table 1. TPS62065 Stability with Different LC Corner Frequencies

Inductance Value	Capacitance Value					
	2.2 μF	4.7 μF	10 μF	22 μF	47 μF	100 μF
Corner Frequencies						
0.56 μH	143.4 kHz	98.1 kHz	67.3 kHz	45.3 kHz	31.0 kHz	21.3 kHz
0.68 μH	130.1 kHz	89.0 kHz	61.0 kHz	41.1 kHz	28.2 kHz	19.3 kHz
1.0 μH	107.3 kHz	73.4 kHz	50.3 kHz	33.9 kHz	23.2 kHz	15.9 kHz
1.2 μH	98.0 kHz	67.0 kHz	45.9 kHz	31.0 kHz	21.2 kHz	14.5 kHz
1.5 μH	87.6 kHz	59.9 kHz	41.1 kHz	27.7 kHz	19.0 kHz	13.0 kHz
1.8 μH	80.0 kHz	54.7 kHz	37.5 kHz	25.3 kHz	17.3 kHz	11.9 kHz
2.2 μH	72.3 kHz	49.5 kHz	33.9 kHz	22.9 kHz	15.7 kHz	10.7 kHz

Legend:	
	Recommended in data sheet
	Stable with Cff (outside recommended LC corner frequency range)
	Stable with Cff (within recommended LC corner frequency range)
	Unstable

Optimizing Load-Step Response

The load step response can be optimized for a lower voltage droop or for a faster response. During a load step, the output capacitor needs to supply the load with current until the regulator can increase its output current to react to the change. A larger capacitor is able to provide this current with a smaller amount of output voltage droop; however, a smaller capacitor increases the bandwidth of the device and provides a faster response. Figure 1 shows TPS62065 load-step responses using a (a) 2.2- μF and (b) 22- μF output capacitors with a 1- μH inductor. The response with the 22- μF capacitor has approximately 50% less voltage droop but is significantly slower.

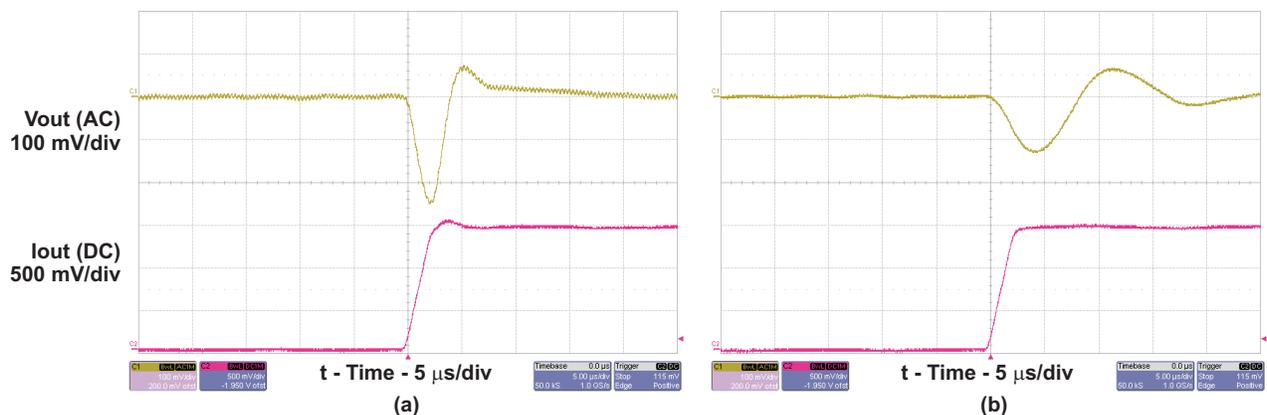
Figure 1. TPS62065 Load-Step Response Using (a) 2.2- μF and (b) 22- μF Output Capacitors

Reducing Output Voltage Ripple

The output voltage ripple is given by $V_{\text{ripple}} = I_{\text{ripple}} \times Z_{\text{Cap}}$. A larger ceramic output capacitor has a lower impedance (Equation 2) at the switching frequency, reducing the output voltage ripple. Figure 2 shows the output voltage ripple with (a) 2.2- μF and (b) 22- μF output capacitors and a 0.68- μH inductor. Ignoring high-frequency spikes, the larger capacitor has about 30% less ripple.

$$Z_{\text{Cap}} = \text{ESR}_{\text{Cap}} + \frac{1}{2\pi \times f_{\text{sw}} \times C_{\text{Cap}}} + 2\pi \times f_{\text{sw}} \times \text{ESL} \quad (2)$$

Another way of reducing the output voltage ripple is to reduce the current ripple. The current ripple is inversely proportional to the inductance. Therefore, increasing the inductor value also reduces the voltage ripple.

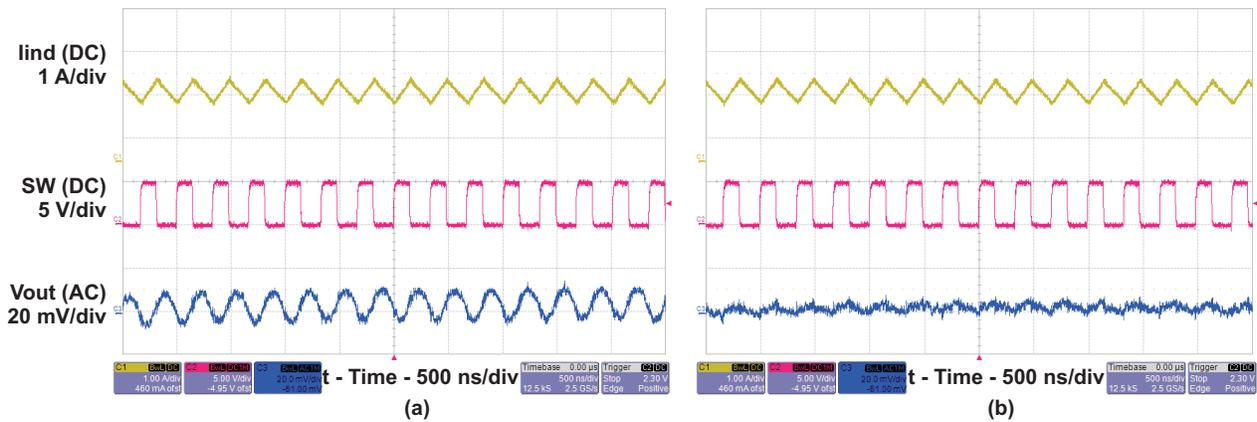


Figure 2. Output Voltage Ripple With (a) 2.2-µF and (b) 47-µF Output Capacitors

Increasing Maximum Output Current

The peak inductor current can be calculated using

$$I_{Lmax} = I_{outmax} + \frac{\Delta I_L}{2},$$

$$\text{where: } \Delta I_L = V_{out} \times \frac{1 - \frac{V_{out}}{V_{in}}}{L \times f_{sw}}$$

(3)

For a TPS62065 design with a 5-V input, 1.8-V output, 2.75-A peak inductor current (the IC’s current limit), and the recommended 1-µH inductor, $I_{outmax} = 2.56$ A. Using a 2.2-µH inductor decreases the peak-to-peak output current ripple by 210 mA, allowing 2.66 A of output current.

Feedforward Capacitor Selection

Figure 3 shows a typical TPS62065 application circuit. Along with resistors R1 and R2, the required feedforward capacitor (Cff) adds a zero and a pole to the closed-loop transfer function of the TPS6206x. This provides a phase boost that reaches a maximum at the geometric mean of the pole and zero frequencies. The application report *Optimizing Transient Response of Internally Compensated dc-dc Converters With Feedforward Capacitor* (SLVA289) details the process of empirically selecting a feedforward capacitor for an internally compensated converter.

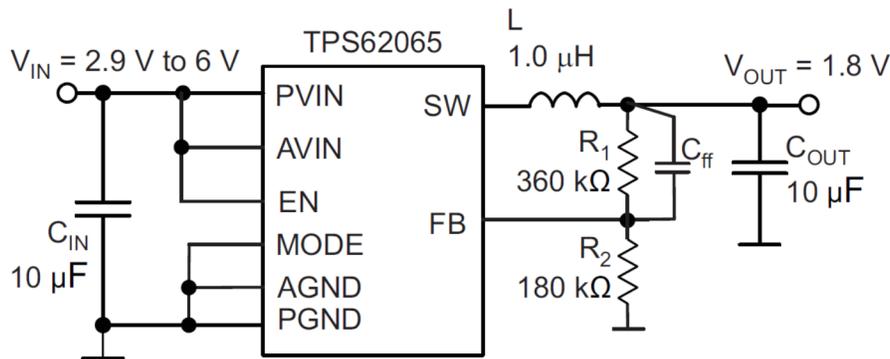


Figure 3. Typical TPS62065 Application Circuit

For optimum stability, Cff selection is a two-step process. First, the crossover frequency with an unpopulated Cff needs to be measured. Once the crossover frequency is determined, Equation 4 is used to calculate the Cff that provides the maximum phase boost at the crossover frequency.

$$C_{ff_{op}} = \frac{1}{2\pi \times f_{noCff}} \times \sqrt{\frac{1}{R1} \times \left(\frac{1}{R1} + \frac{1}{R2} \right)} \quad (4)$$

Table 2 shows recommended Cff values and measured crossover frequencies and phase margins for different LC output filter combinations. This data was taken with a 5-V input, 1.8-V output, and 1.6 A of output current. Different operating conditions affect the loop response of the system. In each cell, the optimal feedforward capacitor (Cff), loop bandwidth, and phase margin are listed. Phase margins above 30 degrees are considered stable. However, some LC combinations with phase margins slightly less than 30 also were considered stable. In these cases, the phase remained close to 30 degrees at frequencies several decades higher than the crossover frequency.

Table 2. TPS62065 Measured Stability Data, Vin = 5 V, Vout = 1.8 V, Iout = 1.6 A

Inductance Value	Capacitance Value					
	2.2 μF	4.7 μF	10 μF	22 μF	47 μF	100 μF
	Cff, BW, PM					
0.56 μH	2.7 pF	3.9 pF	4.7 pF	10.0 pF	15.0 pF	33.0 pF
	396.5 kHz	252.5 kHz	193.2 kHz	86.7 kHz	63.5 kHz	53.6 kHz
	48.8°	55.2°	57.0°	54.2°	40.5°	29.6°
0.68 μH	2.7 pF	3.9 pF	5.6 pF	10.0 pF	15.0 pF	
	402.4 kHz	247.9 kHz	204.6 kHz	90.5 kHz	62.1 kHz	
	48.8°	55.8°	58.3°	57.8°	48.4°	
1.0 μH	3.3 pF	4.7 pF	5.6 pF	12.0 pF	22.0 pF	
	342.6 kHz	227.1 kHz	188.4 kHz	88.3 kHz	55.2 kHz	
	52.7°	55.6°	54.8°	45.2°	29.8°	
1.2 μH	3.9 pF	5.6 pF	8.2 pF	15.0 pF		
	275.6 kHz	177.5 kHz	144.4 kHz	73.6 kHz		
	51.0°	50.1°	49.5°	29.8°		
1.5 μH	3.9 pF	5.6 pF	8.2 pF	15.0 pF		
	248.5 kHz	168.1 kHz	133.0 kHz	63.7 kHz		
	54.4°	51.7°	50.3°	28.2°		
1.8 μH	4.7 pF	6.8 pF	8.2 pF			
	230.9 kHz	152.3 kHz	117.0 kHz			
	52.4°	48.8°	45.1°			
2.2 μH	4.7 pF	6.8 pF	8.2 pF			
	216 kHz	148 kHz	111 kHz			
	52.4°	48.8°	44.8°			
Legend:						
	Stable					
	Unstable					

The inductors used to gather the stability data are listed in Table 3. The output capacitors were 6.3-V ceramic X5R. Due to the dc bias effect, the actual capacitances are lower than the values listed.

Table 3. Inductors Used for Stability Data

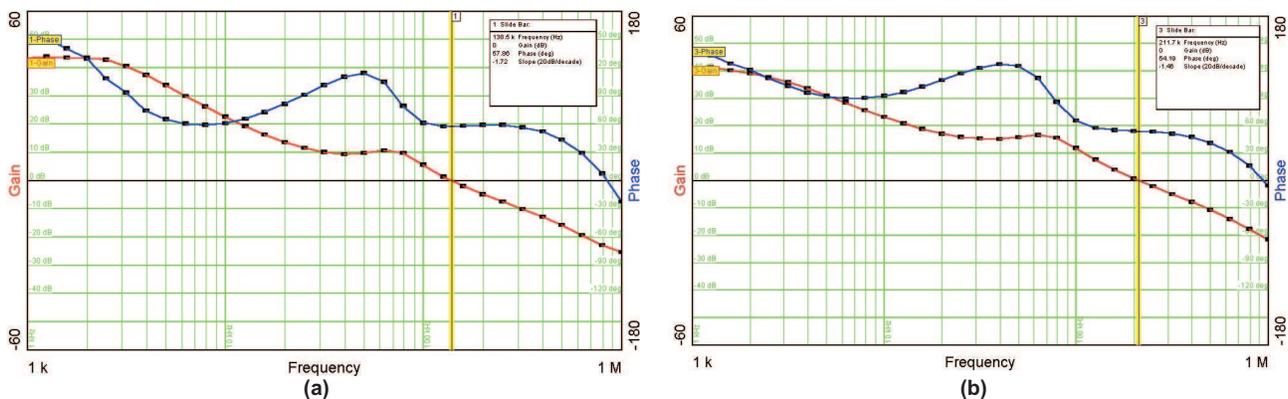
Inductance (μH)	Description
0.56	Coilcraft LPS4018-561
0.68	Coilcraft LPS4012-681
1.0	Murata LQH44PN1R0NP0L

Table 3. Inductors Used for Stability Data (continued)

Inductance (μH)	Description
1.2	Coilcraft LPS5030-122
1.5	Coilcraft LPS4012-152
1.8	Coilcraft LPS5015-182
2.2	Coilcraft LPS4018-222

Optimizing Cff for Higher Bandwidth

At the expense of phase margin, a larger Cff can increase the bandwidth of the device. The feedforward capacitor can be increased as long as the phase margin is higher than 30 degrees. Figure 4 shows the closed-loop frequency responses with a 0.68- μH , 10- μF LC filter and a (a) 5.6-pF and (b) 47-pF Cff capacitor. With the larger capacitor, the loop bandwidth is increased by 73.2 kHz while the phase margin is decreased by 3.67 degrees.


Figure 4. Closed Loop Frequency Response With (a) 5.6-pF and (b) 47-pF Feedforward Capacitors

The user must empirically measure power supply performance after modifying the external components. A large increase in feedforward capacitance increases ringing during load transients. The application report [SLVA289](#) provides detailed information regarding the effects of varying the Cff value.

Conclusion

By choosing the appropriate external components, a TPS6206x design can be optimized for smaller solution size, faster load-step response, lower output voltage ripple, increased output current, and/or increased control loop stability. Following the outlined empirical method, the feedforward capacitor is selected to ensure stability with the LC combination of the design.

References

1. *Optimizing Transient Response of Internally Compensated dc-dc Converters With Feedforward Capacitor* application report ([SLVA289](#))
2. *TPS62065/7, 3-MHz 2A Step Down Converter in 2x2 SON Package* datasheet ([SLVS833](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated