

# A better bootstrap/bias supply circuit

By **Michael O'Loughlin** (Email: michael\_oloughlin@ti.com)


Member, Applications Engineering

In some power-supply applications, the pulse width modulator (PWM) controller is powered up by the configuration in Figure 1 from an auxiliary winding tapped off the power stage's transformer. This technique is used to reduce power loss and keep the overall efficiency high. The auxiliary winding, D1, and C1 provide power and hold-up energy for the PWM. Resistor R1 is used to trickle charge C1 off the input voltage. C1 has to be sized to hold up the supply voltage ( $V_{CC}$ ) long enough for the PWM to start switching the gate of the power MOSFET, causing energy to be stored in the power transformer and delivered to the PWM's  $V_{CC}$  through the auxiliary winding. This technique is known as bootstrapping. However, at light-load conditions this circuit is problematic for the power-supply designer.

## Problems with traditional bootstrapping/bias supply scheme


Under light-load conditions, C1 has to supply all the energy. C1 generally has to be large enough to hold up  $V_{CC}$  for at least 10 switching cycles. However, under light-load and no-load conditions, the current into the PWM ( $I_{CC}$ ) will discharge  $V_{CC}$  to the point that the PWM will go into undervoltage lockout (UVLO), causing the output to become unstable. The designer might think that he can reduce the size of R1 or increase the size of

**Figure 1. Traditional bootstrapping/bias supply**

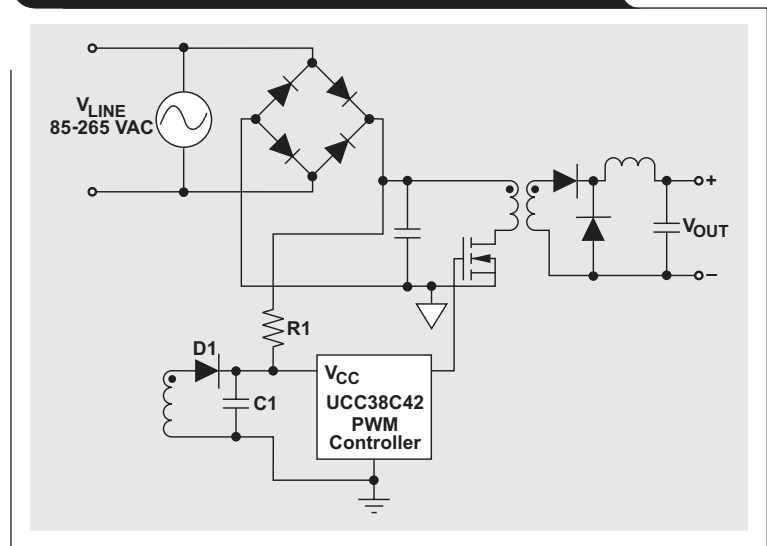

C1. Reducing the size of R1 only increases losses and decreases the overall efficiency. Increasing the size of C1 only decreases the start-up time of the PWM. The circuit in Figure 2 will reduce the size of the hold-up capacitor and provide power under no-load conditions while maintaining high efficiencies at the converter's full output power.

**Figure 2. Adding series-pass regulator reduces size of C1**

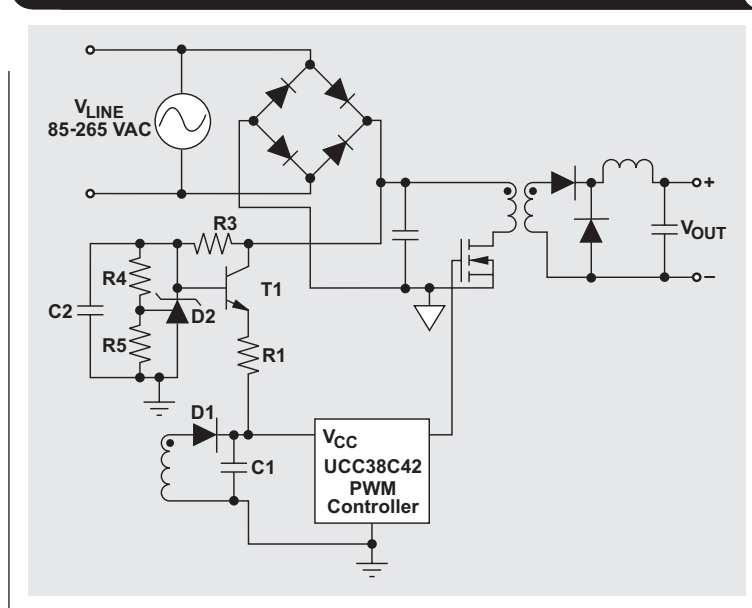

## Theory of operation

Electrical components C2, D2, R3, R4, R5, and T1 form a series-pass regulator that provides power to the PWM's  $V_{CC}$  under light- to no-load conditions. Resistor R1 provides current limiting to protect the series-pass transistor (T1). All of these components together form a bootstrap/bias supply circuit. The series-pass regulator is designed to supply a bias voltage that is less than the bias voltage developed by the auxiliary winding. When the auxiliary winding starts to supply  $V_{CC}$  voltage, it produces a voltage large enough to back bias the base emitter junction of T1, causing the series-pass regulator to turn off. This circuit enables the designer to take advantage of lower losses from powering the PWM with an auxiliary winding and also supplies energy to the control circuitry at light loads.

## Setting up the circuit

First we set up the shunt regulator voltage. Knowing the voltage from the auxiliary supply ( $V_{AUX}$ ), we can use the following equation to calculate the shunt voltage ( $V_{SHUNT}$ ):

$$V_{SHUNT} = V_{AUX} - 1 \text{ V}$$

It is important to note that  $V_{SHUNT}$  minus  $V_{AUX}$  should not exceed the maximum reverse voltage of the base-to-emitter junction of T1. This information can be found in the transistor's data sheet.

Once we have decided on the shunt voltage, we can easily set up the series-pass regulator. To minimize losses, R3 is typically sized to allow just enough current to bias the shunt regulator. Typically this is set for twice the shunt regulator's minimal bias current ( $I_{D2}$ ):

$$R3 = \frac{V_{IN} - V_{SHUNT}}{2 \times I_{D2}}$$


R4 and R5 program the shunt voltage. R4 can be selected by choosing a resistor for R5 and plugging the reference voltage ( $V_{REF}$ ) into the following equation:

$$R4 = R5 \times \frac{V_{SHUNT} - V_{REF}}{V_{REF}}$$

R1 limits the current through T1, protecting it from overcurrent conditions. It can easily be selected based on the maximum current rating ( $I_{max}$ ) and Ohm's law:

$$R1 = \frac{V_{SHUNT} - V_{BE}}{I_{max}}$$

**Figure 3. Lower bias voltage provided by R3 and D3**

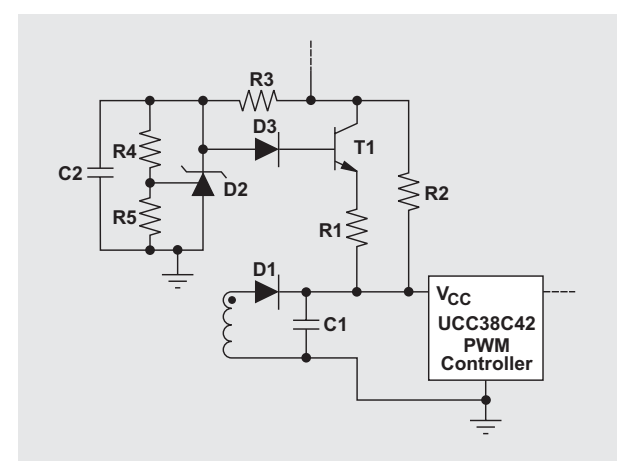

C1 is typically sized for hold-up time ( $t_{HOLDUP}$ ) and can be sized by knowing  $V_{BIAS}$  and the PWM's UVLO and operating current ( $I_{CC}$ ):

$$C1 = \frac{I_{CC} \times t_{HOLDUP}}{V_{BIAS} - UVLO}$$

C2 is a hold-up and filtering capacitor for most applications. A 1- $\mu$ F ceramic capacitor will work fine for this electrical component.

In some applications, due to efficiency requirements, the power-supply designer may want the bias voltage to run lower than the PWM integrated circuit's turn-on threshold. This would require an extra resistor and diode (see Figure 3). R2 is a trickle-charge resistor used for bootstrapping the PWM. It allows capacitor C1 to charge up to the PWM's turn-on threshold voltage. Diode D3 is required to ensure that T1's maximum reverse base-to-emitter voltage is not exceeded. It is also worth mentioning that the shunt voltage would have to be adjusted to accommodate the forward voltage drop of D3.

## Related Web sites

[analog.ti.com](http://analog.ti.com)

[www.ti.com/sc/device/UCC38C42](http://www.ti.com/sc/device/UCC38C42)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

## TI Worldwide Technical Support

### Internet

**TI Semiconductor Product Information Center Home Page**  
[support.ti.com](http://support.ti.com)

**TI Semiconductor KnowledgeBase Home Page**  
[support.ti.com/sc/knowledgebase](http://support.ti.com/sc/knowledgebase)

### Product Information Centers

#### Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>		

#### Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>		

#### Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>		
Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>		

#### Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>		<a href="mailto:ti-china@ti.com">ti-china@ti.com</a>

C011905

**Safe Harbor Statement:** This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

**Trademarks:** All other trademarks are the property of their respective owners.

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated

SLY077