

The IBIS model, Part 2: Determining the total quality of an IBIS model

By Bonnie C. Baker

Senior Applications Engineer

This article is Part 2 of a three-part series. Part 1 (see Reference 1) discussed the fundamental elements of digital input/output buffer information specification (IBIS) simulation models and how they are generated in the SPICE environment. This article, Part 2, investigates IBIS-model validation. Part 3, which will appear in a future issue of the *Analog Applications Journal*, will show how IBIS users investigate signal-integrity issues and problems during the development phase of a printed circuit board (PCB).

IBIS models can be generated from the SPICE deck of an integrated circuit (IC) or in the lab. In both cases, the modeling engineer collects DC data to generate the power-clamp, ground-clamp, pull-up, and/or pull-down data for the various digital buffers on the chip. Following this, data is collected on the output buffer's transient or on the AC rise and fall times. See Reference 1 for more information on these data-collection processes. The IBIS model's transient data replicates the time behavior of output buffers. The modeling engineer acquires the model data with an array of power-supply conditions and junction temperatures. Further enhancements include the addition of the IC's package characteristics, buffer-input chip capacitance, and surrounding documentation. Once the IBIS model exists, the engineer reviews it to verify several quality stages and then produces a validation report that correlates the IBIS model to SPICE simulations or bench data.

Historically, IBIS models have had a reputation of poor quality because many IBIS users have received incorrect models from vendors. The errors range from simple format errors to the model not really portraying the behavior of the buffers in the IC at all. Texas Instruments (TI) is committed to generating quality, reliable IBIS models for customers' signal-integrity investigations.

The IBIS Open Forum's Quality Task Group and Model Review Task Group have formulated a quality-control (QC) process using four QC stages, which are described in the "IBIS Quality Specification," Version 2.0 (Reference 2).

The IBIS task groups are subcommittees of TechAmerica's Systems, Standards & Technology Council. Other model users and model makers across the industry have also contributed to this QC process. The four QC stages are:

- Stage 0: An automated quality check using an IBIS parser
- Stage 1: A manual and visual quality check of the model
- Stage 2: Correlation to SPICE or hardware test data
- Stage 3: Correlation to both SPICE and hardware test data

TI performs stages 0, 1, and 2 for its IBIS models, correlating them with SPICE for stage 2. This article will describe the nuances of performing stages 0, 1, and 2 (with SPICE correlation only).

Stage 0: IBIS parsers

The first stage of QC for an IBIS model begins with an IBIS parser program. This computer program provides an essential first-stage model check, inspecting the IBIS file for the validity of the IBIS model data and for syntax errors. This type of program can create "Error," "Warning," and/or "Note" messages in relation to the IBIS model under test, but creating an IBIS model that is free of these messages is possible.

For instance, the parser program IBISCHK4 looks for illegal text types, verifies model types, insures that all proper variables are available for each model, validates end points of data, and performs other housekeeping checks. An example of the results of running an IBISCHK4 program with an IBIS model is shown in the sidebar below.

The "Error," "Warning," and "Note" messages from the parser check provide an opportunity for the IBIS-model designer to identify errors and easily correct them. Running a parser with an IBIS model is essential at the beginning of the quality check; however, the parser does not provide an exhaustive list of IBIS-model errors and does not necessarily guarantee a good model.


Example IBISCHK4 results

```

ERROR (line 137) - Invalid Model_type ("InputX")
WARNING (line 154) - Vinl should not be specified for model type (null)
WARNING (line 155) - Vinh should not be specified for model type (null)
ERROR - Model 'sdi_3p3': Ramp Not Defined

Errors : 2
Warnings: 2

File Failed
  
```

 Figure 1. Pull-down I-V test circuit for three-state buffer

Parser freeware programs are available for dos32, hp_111, Linux®, and Sun® platforms at the IBIS Open Forum's Web site (<http://www.eda.org/ibis>). To date there are four parsers available: IBISCHK2, IBISCHK3, IBISCHK4, and IBISCHK5. The level number of each parser program corresponds respectively to the version number of the documented IBIS specification. For example, the most recent parser program, IBISCHK5, corresponds to Version 5.0 of the IBIS specification (Reference 3). TI uses IBISCHK4 and IBISCHK5 to validate its IBIS models.

Stage 1: Visual check

A visual QC check of an IBIS model consists of a manual review of its text and waveforms. During this visual review, the modeling engineer verifies that the header section of the IBIS model contains accurate information. For instance, the header must have the proper products within the

product families listed and must have appropriate modeling comments and notes. Following the header, the model must have reasonable package parasitics and well-defined selector entries and must map directly to parameters in the product data sheet, including buffer types, load conditions, input-buffer thresholds, and operating or specified temperature range.

Additionally, the DC and transient waveforms must comply with IBIS standards. The measurement voltage span of the DC waveforms ranges from $-V_{DD}$ to $+2 \times V_{DD}$ (where V_{DD} is the power-supply voltage to the buffer). Across this range, the input and output current must not exceed 2 A. Notes in the comments section in the IBIS model header explain the reason for any excessive currents beyond 2 A. Figure 1 shows the pull-down test configuration for an output buffer, and Figure 2 shows a sample of a pull-down curve from an IBIS model.

 
Figure 2. Pull-down IBIS graph for DAC7718 output buffer

 
Figure 3. Falling-edge V-t test circuit for an output buffer

Figure 3 shows the proper test-circuit configuration for the transient falling edge of an output buffer. The resistor following the pad is usually $50\ \Omega$; however, it can be a different value depending on the IC's requirements as stated in the product data sheet.

Figure 4 shows typical falling-edge data for an IBIS model. In this graph, the initial output voltage remains constant for at least two points in time. The data completes its migration to the final value within approximately two-thirds of the total x-axis time.

The text and graphics checks of the IBIS model can be found in Reference 2, where they are described in detail.

Stage 2: Correlation to SPICE or hardware test data

A primary use for IBIS models is to simulate timing and signal integrity, including over/undershoot or crosstalk behavior on an IC's PCB. For stage 2 QC, the modeling engineer compares the performance of an IBIS model in this environment to the device's IC SPICE simulation or test data. The engineer selects appropriate models for a typical board's transmission lines for the specific product under test and compares the test results graphically and with a figure of merit.

 
Figure 4. DAC7718 input-buffer fall-time analysis

Figure 5 shows an example of a validation test circuit for a SPICE-deck output buffer. This circuit includes the resistive, inductive, and capacitive package parasitics (R_{pkg} , L_{pkg} , and C_{pkg} , respectively) at the output of the SPICE buffer. Following these parasitics is a model of a PCB transmission line, T1. The SPICE simulation collects data at the far end of the transmission line, $V_{(\text{SPICE})}$.

Figure 6 shows an example of an output-buffer IBIS circuit. Notice that the package parasitics do not appear in the circuit, as they are embedded in the IBIS model. This IBIS simulation circuit has the same model of a PCB transmission line (T1) as that in the SPICE-deck simulation circuit.

Figure 7 provides a simulation rise-time comparison between the SPICE and IBIS models based on TI's ADS8319. The outputs were compared at the $V_{(\text{SPICE})}$ node in Figure 5 and the $V_{(\text{IBIS})}$ node in Figure 6. Simulated model conditions were based on a nominal or 1.8-V power supply, a junction temperature of 27°C, and a typical process corner.

Figure 5. Example circuit for SPICE test of an output buffer

 


Figure 6. Example circuit for IBIS-model test of an output buffer

 


Figure 7. Comparison of output rise times for SPICE and IBIS models

 


Figure 8. Comparison of output fall times for SPICE and IBIS models

 


Figure 8 shows a similar fall-time comparison between the SPICE and IBIS models, also based on the ADS8319. Simulated model conditions were based on a 5-V power supply, a junction temperature of 25°C, and a typical process corner.

It is common to calculate a figure of merit (FOM) when curves like those in Figures 7 and 8 are compared. The FOM calculation is

$$FOM = 100 \times \left[1 - \frac{\sum_{i=1}^N |X_i(\text{golden}) - X_i(\text{DUT})|}{\Delta X \times N} \right],$$

where $X_i(\text{golden})$ is a time sample of the SPICE-deck curve, $X_i(\text{DUT})$ is the matching time sample of the IBIS-model curve, ΔX is the range of data points, and N is the number of samples. The FOM formula compares the two waveforms by summing the absolute value of the x-axis differences between two data points. This sum is divided by the range of the data points as well as by the number of data points. A preliminary numerical task must map each set of data points to a common x-y grid by interpolation. The FOM for the curves in Figures 7 and 8 combined is 0.68%.

Conclusion

In the past, IBIS models have been known to be of poor quality. This lack of quality can be rectified by using the IBIS Open Forum's QC process. At stage 0 in this process, an IBIS parser software finds errors in syntax and in the IBIS model's format. Stage 1 IBIS QC is implemented with a visual inspection of the text and graphics. At stage 2, the IBIS model is mapped back to the product's data sheet. Finally, as the modeling engineer generates IBIS models for SPICE decks, it is important to complete the loop by validating that the IBIS model does match the SPICE-deck performance in a PCB environment. Using stages 0, 1, and

2 to validate the IBIS model insures reliable simulations with signal integrity.

References

For more information related to this article, you can download an Acrobat® Reader® file at www.ti.com/lit/litnumber and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Bonnie Baker, "The IBIS model: A conduit into signal-integrity analysis, Part 1," <i>Analog Applications Journal</i> (4Q 2010)	slyt390
2. The IBIS Open Forum. (2009, Oct. 30). "IBIS Quality Specification," Version 2.0 [Online]. Available: http://www.eda.org/ibis/quality_ver2.0	—
3. The IBIS Open Forum. (2008, Aug. 29). "IBIS (I/O Buffer Information Specification)," Version 5.0 [Online]. Available: http://www.eda.org/ibis/ver5.0	—
4. The IBIS Open Forum. (2000, Apr. 20). "I/O Buffer Accuracy Handbook," Rev. 2.0 [Online]. Available: http://www.eda.org/ibis/accuracy/handbook.pdf	—
5. The IBIS Open Forum. (2000, Sept. 11). "I/O Buffer Accuracy Report," Rev. 2.1 [Online]. Available: http://www.eda.org/ibis/accuracy/report.pdf	—

Related Web sites

dataconverter.ti.com
www.ti.com/sc/device/ADS8319
www.ti.com/sc/device/DAC7718
www.eda.org/ibis

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center

Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas Phone +1(972) 644-5580

Brazil Phone 0800-891-2616

Mexico Phone 0800-670-7544

Fax +1(972) 927-6377

Internet/Email support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone

European Free Call 00800-ASK-TEXAS
(00800 275 83927)

International +49 (0) 8161 80 2121

Russian Support +7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +49 (0) 8161 80 2045

Internet support.ti.com/sc/pic/euro.htm

Direct Email asktexas@ti.com

Japan

Phone Domestic 0120-92-3326

Fax International +81-3-3344-5317

Domestic 0120-81-0036

Internet/Email International support.ti.com/sc/pic/japan.htm

Domestic www.tij.co.jp/pic

Asia

Phone

International +91-80-41381665

Domestic [Toll-Free Number](#)

Note: Toll-free numbers do not support mobile and IP phones.

Australia 1-800-999-084

China 800-820-8682

Hong Kong 800-96-5941

India 1-800-425-7888

Indonesia 001-803-8861-1006

Korea 080-551-2804

Malaysia 1-800-80-3973

New Zealand 0800-446-934

Philippines 1-800-765-7404

Singapore 800-886-1028

Taiwan 0800-006800

Thailand 001-800-886-0010

Fax +8621-23073686

Email tiasia@ti.com or ti-china@ti.com

Internet support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A122010

E2E is a trademark of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. Linux is a registered trademark of Linus Torvalds. Sun is a registered trademark of Sun Microsystems Inc. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video
Wireless	www.ti.com/wireless-apps

[TI E2E Community Home Page](#)

[e2e.ti.com](#)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated