# TI Developer Conference March 7-9, 2007 • Dallas, TX

### Minds in Motion

**TEXAS INSTRUMENTS** 

### **Real World Analog Solutions for Your Processor Applications**

ADC: Delta-Sigma, SAR vs. Pipeline ADCs -When and Where to Use Them

**Bonnie Baker Senior Applications Engineer, DAP** bonnie@ti.com


### Agenda

- What Are the Signal Frequencies
  - Analog classes of applications
  - Frequency ranges of ADCs
- Nuts and Bolts of Delta-Sigma Converters
  - $\Delta\Sigma$  converter core and auxiliary  $\Delta\Sigma$  functions
  - Applications for the  $\Delta\Sigma$  converter
- The SAR ADC
  - Input stage dynamics
  - Applications for the SAR converter
- The High-speed Pipeline Topology
  - Driving the capacitive input stage
  - Applications for the pipeline converter
- Conclusion

Minds in Motion

🦆 Texas Instruments

### Real World vs. Bandwidth

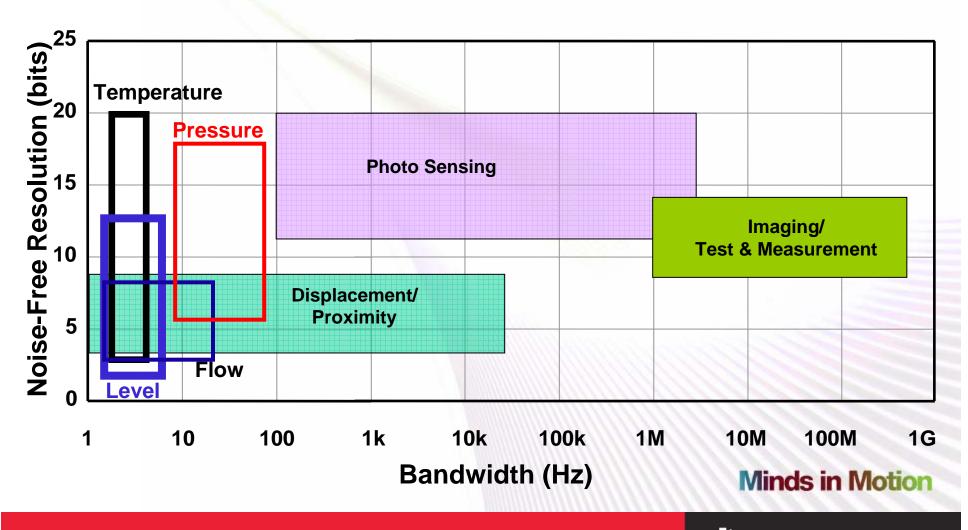



# **ADC** Architectures


- There are many different ADC architectures
  - Successive approximation (SAR)
  - Sigma delta ( $\Sigma\Delta$ )
  - Slope or dual slope
  - Pipeline
  - Flash ... as in quick, not memory
- Delta-sigma converters determine the digital world by:
  - Oversampling
  - Applying digital filtering
- SARs determine the digital world by:
  - Sampling the input signal
  - Using an iterative process
- Pipeline converters determine the digital world by:
  - Undersampling
  - With sample/gain algorithm topology
  - Multiple stages/larger cycle-latency

**Minds in Motion** 

🖑 Texas Instruments

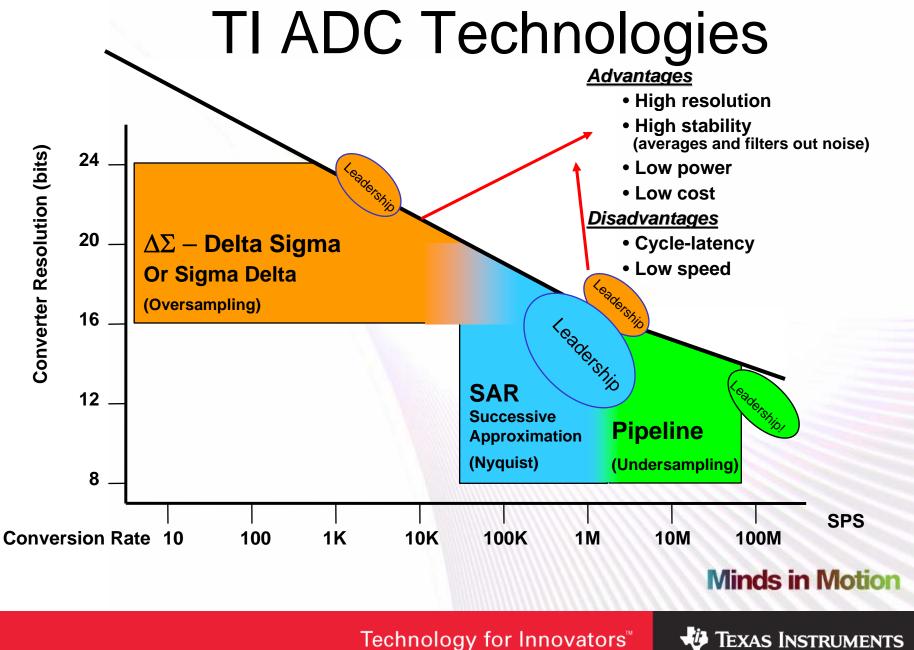


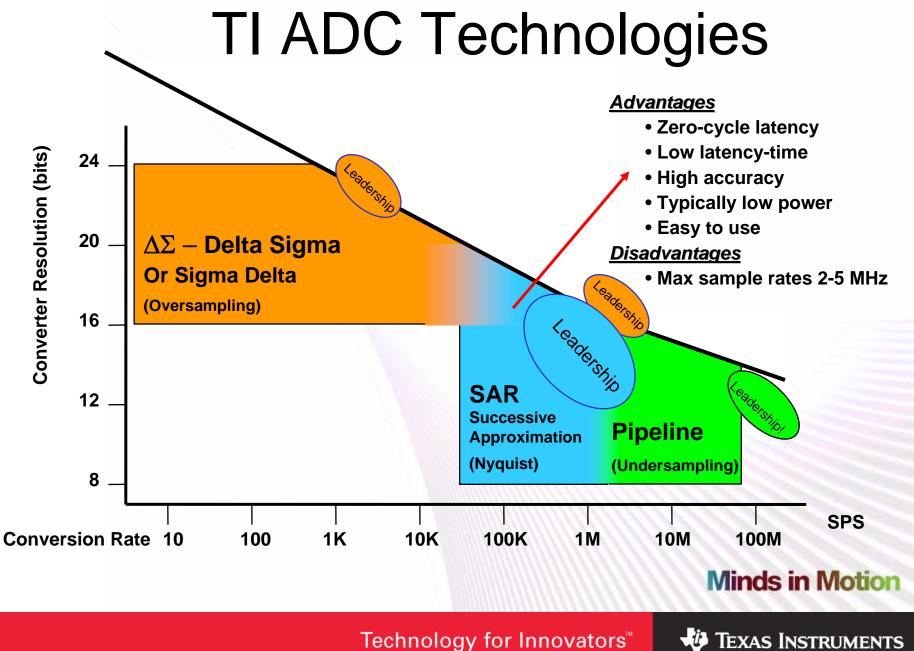

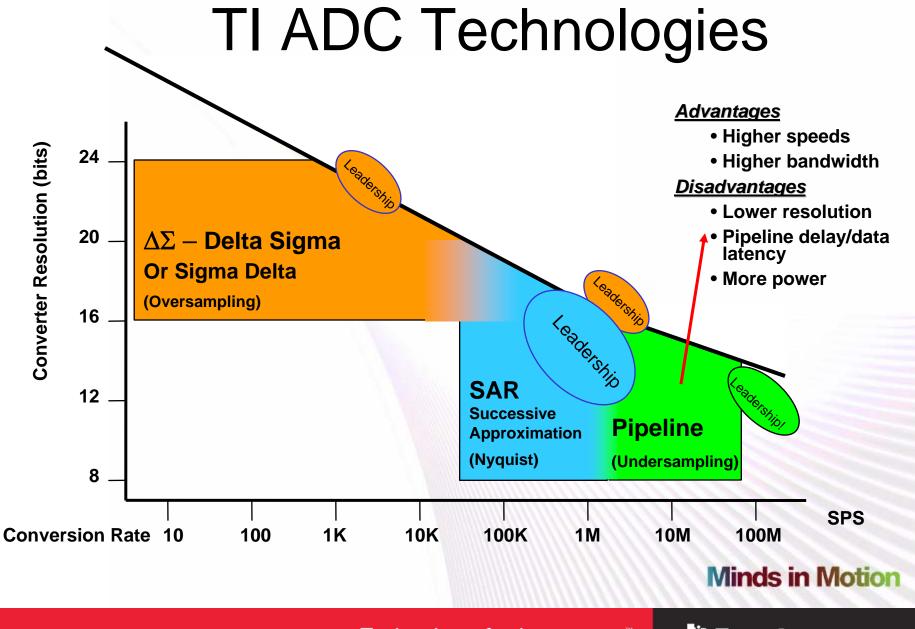


Technology for Innovators<sup>™</sup>

🕂 Texas Instru<u>ments</u>

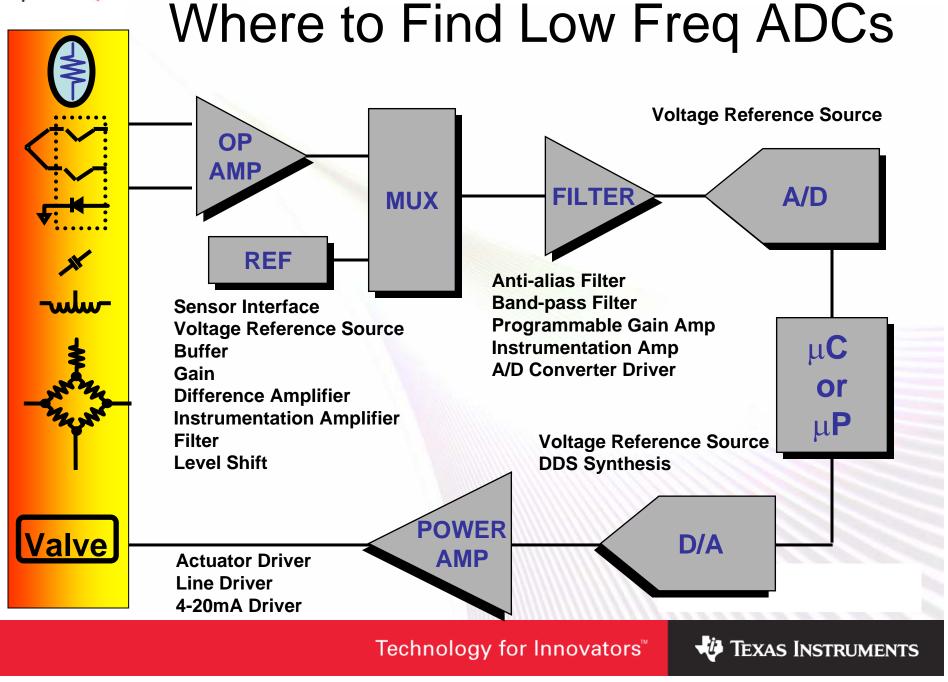



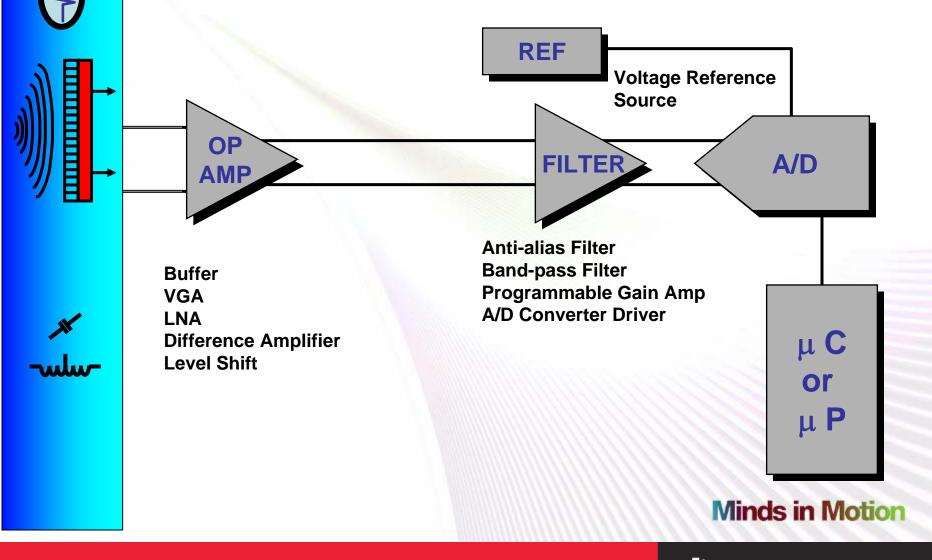

Technology for Innovators<sup>™</sup>

🐺 Texas Instruments

## Agenda

- What Are the Signal Frequencies
  - Analog classes of applications
  - Frequency ranges of ADCs
- Nuts and Bolts of Delta-Sigma Converters
  - $\Delta\Sigma$  converter core and auxiliary  $\Delta\Sigma$  functions
  - Applications for the  $\Delta\Sigma$  converter
- The SAR ADC
  - Input stage dynamics
  - Applications for the SAR converter
- The High-speed Pipeline Topology
  - Driving the capacitive input stage
  - Applications for the pipeline converter
- Conclusion


## Nuts and Bolts of $\Delta\Sigma$ ADCs

- The system versus  $\Delta\Sigma$  (delta-sigma)
- $\Delta\Sigma$  analog-to-digital converter core
  - Programmable gain amplifier (PGA)
  - Analog modulator
  - Digital filter
  - Decimation filter
- Other features and options
- Typical applications



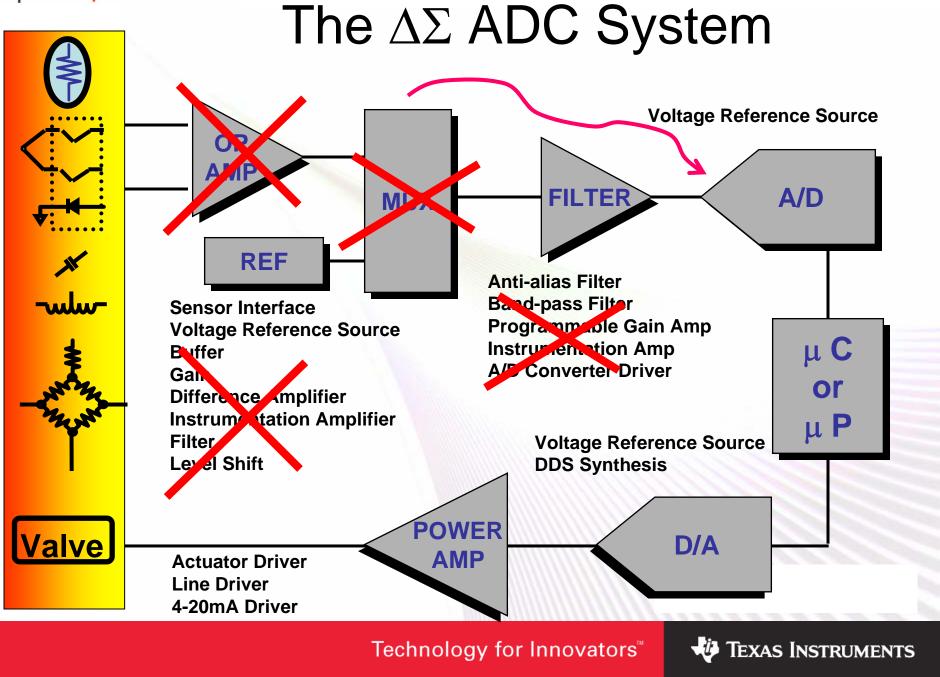
# Applications for $\Delta\Sigma$ Converters


- Signal Level: System Clock Range ~ 0.5 to 40 MHz
  - Has an internal digital low-pass filter
    - Uses an integrator
  - Accurate near DC
  - High resolution: Up to 24 bits
- Audio: System Clock Range ~ 20 to 40 MHz
  - Has an internal digital low-pass filter
  - Optimized noise performance
  - Optimized filter in audio frequency for flatness
- High Speed
  - Has an internal digital band-pass filter
    - Uses a band-pass topology instead of integrator




## **Delta-Sigma ADC Core**

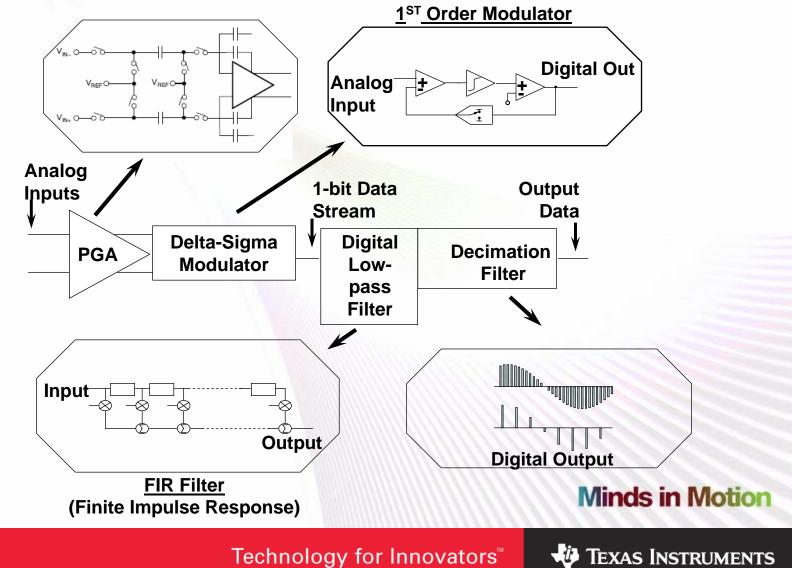


### Programmable Gain Amp

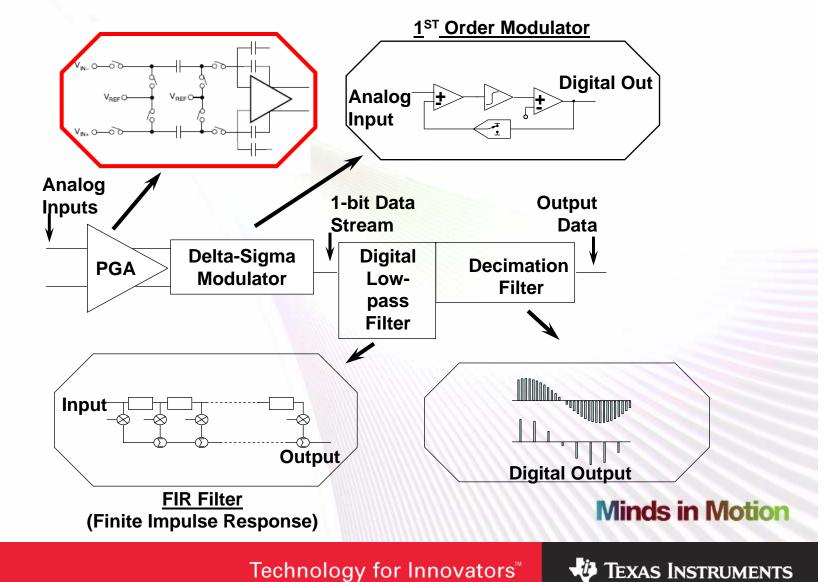


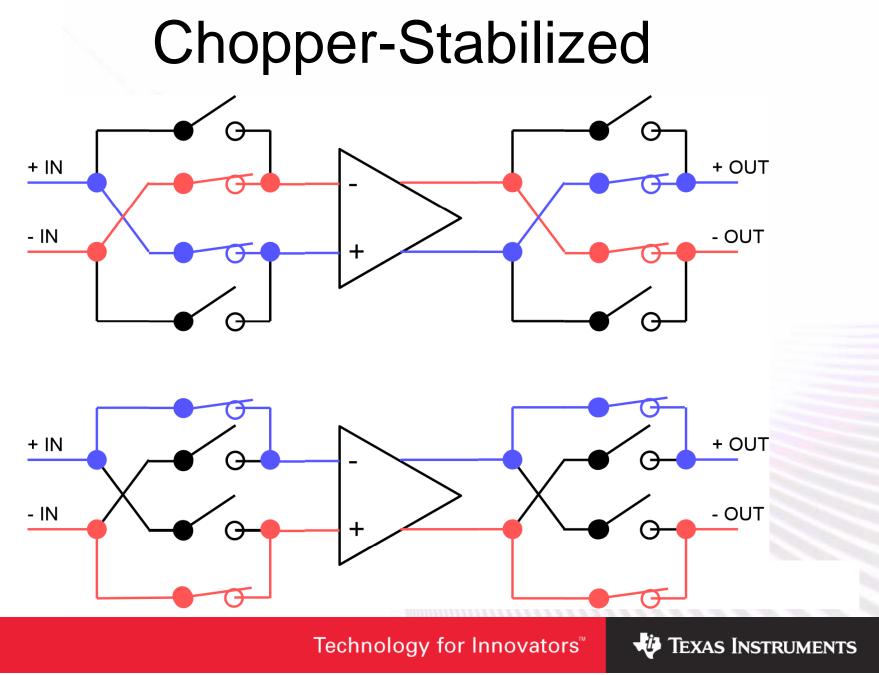


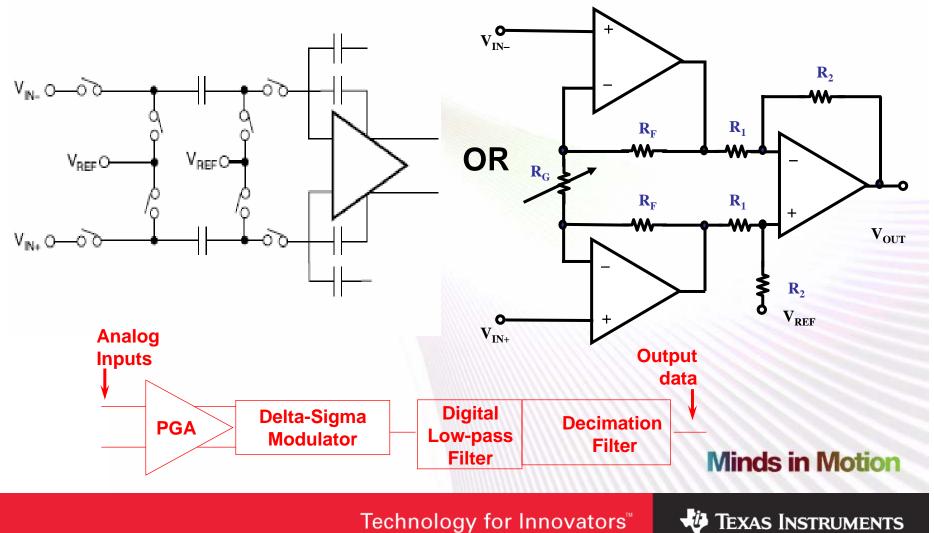
### **Programmable Gain Amplifier** (PGA)




## **Delta-Sigma ADC Core**

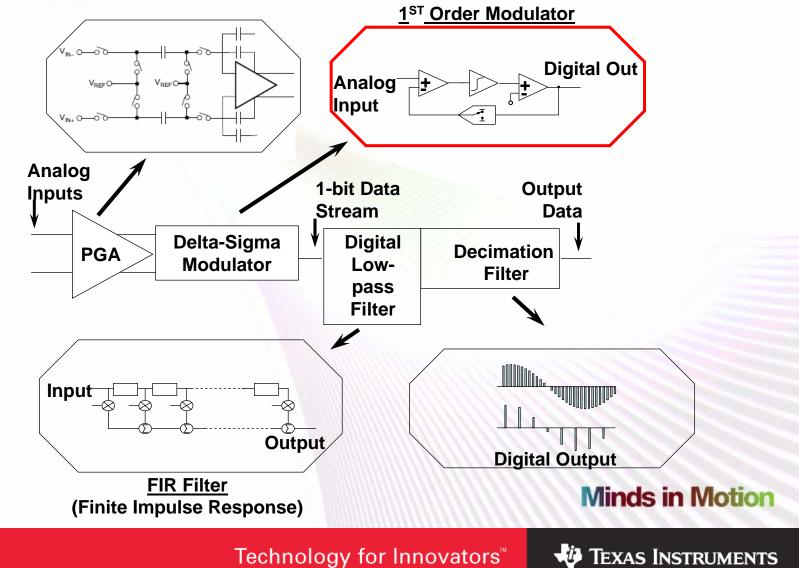


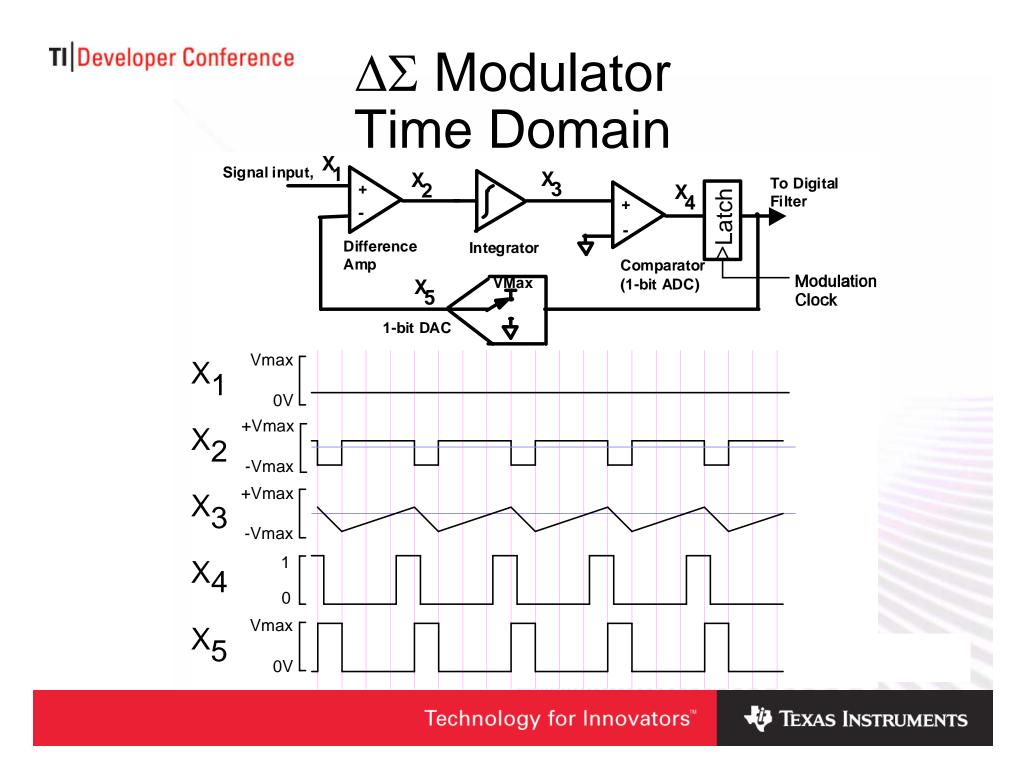


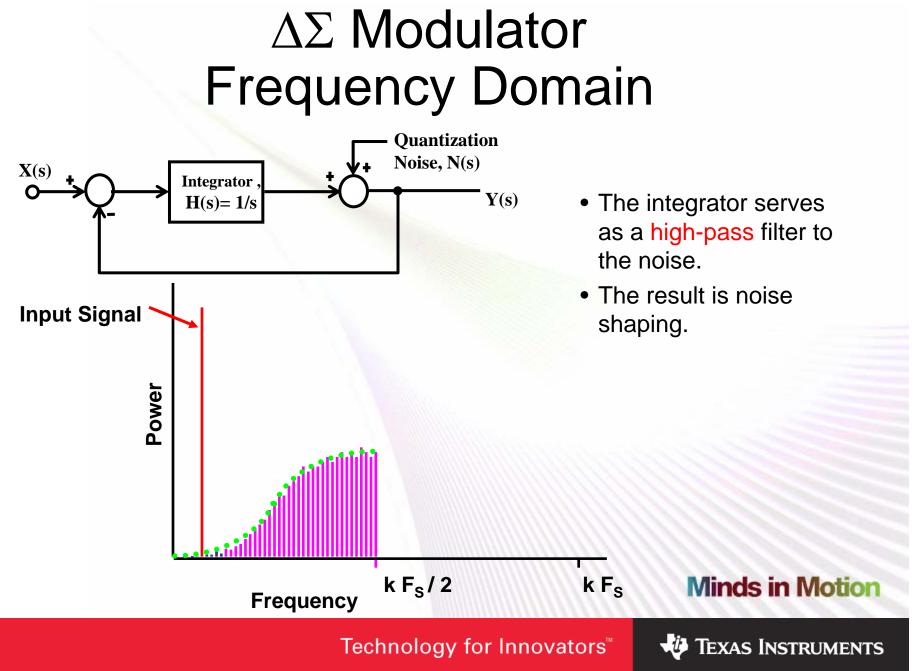


### **Delta-Sigma ADC Core**

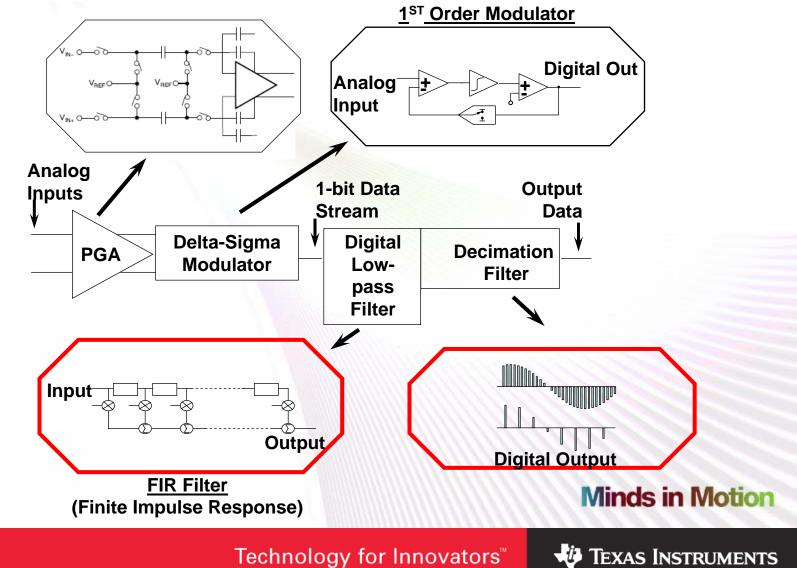

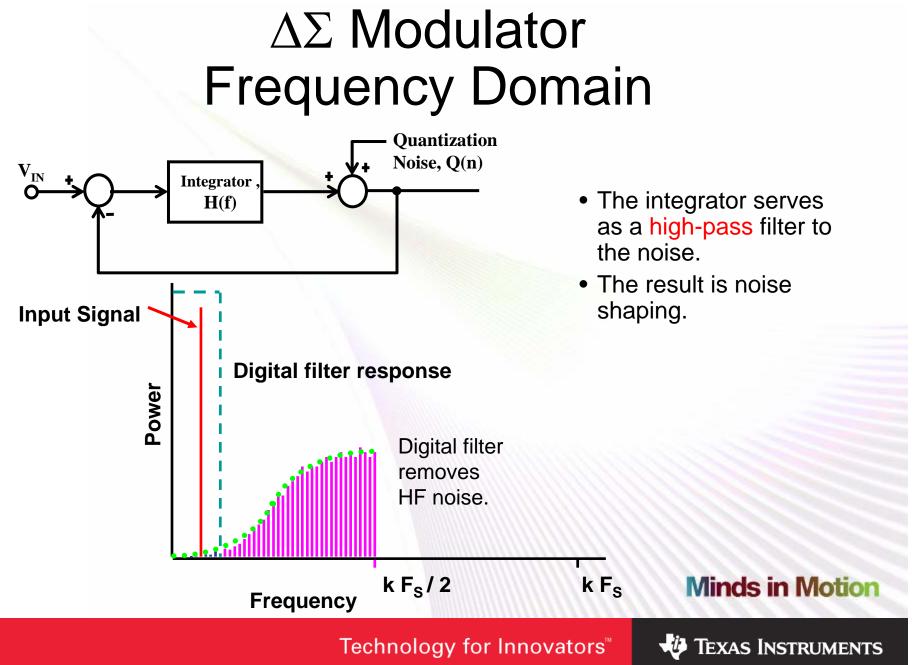

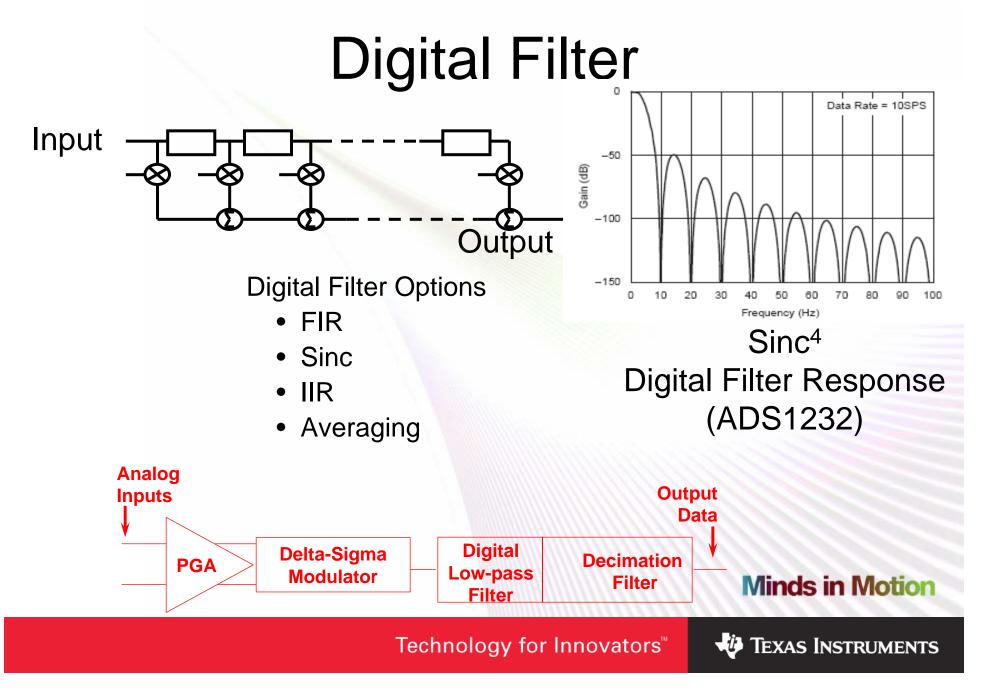

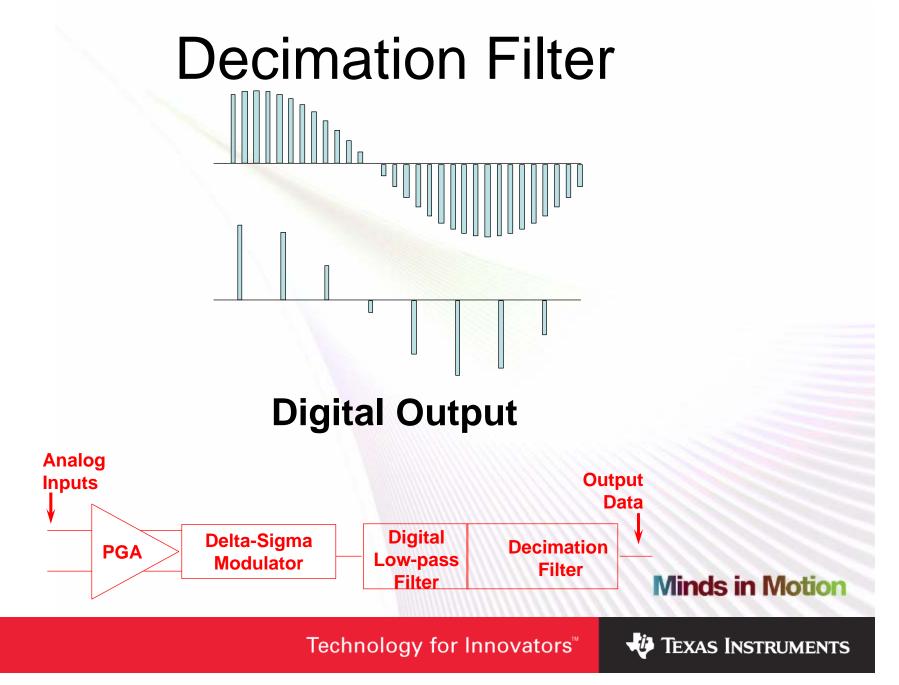

### Other Analog Features and Options

### Analog

- Features
  - Internal voltage or current reference(s)
  - AC excitation capable
  - DAC for TARE offset adjust
  - Transducer burn-out sensor
- Input Interface
  - Differential and/or multichannel Inputs
  - Buffer input
  - Negative input

#### Minds in Motion

**TEXAS INSTRUMENTS** 

### **Other Digital Features and Options**


### Digital


- Features
  - Single-cycle conversion (zero-cycle latency)
  - Programmable digital filter
  - Calibration: Offset, gain, self, system
  - Sleep mode, BOR, memory, digital latches
- Interface
  - Slave/master
  - Clock polarity
  - Daisy chain


#### Minds in Motion

**TEXAS INSTRUMENTS** 

**Zero-Latency in MUX Applications** 

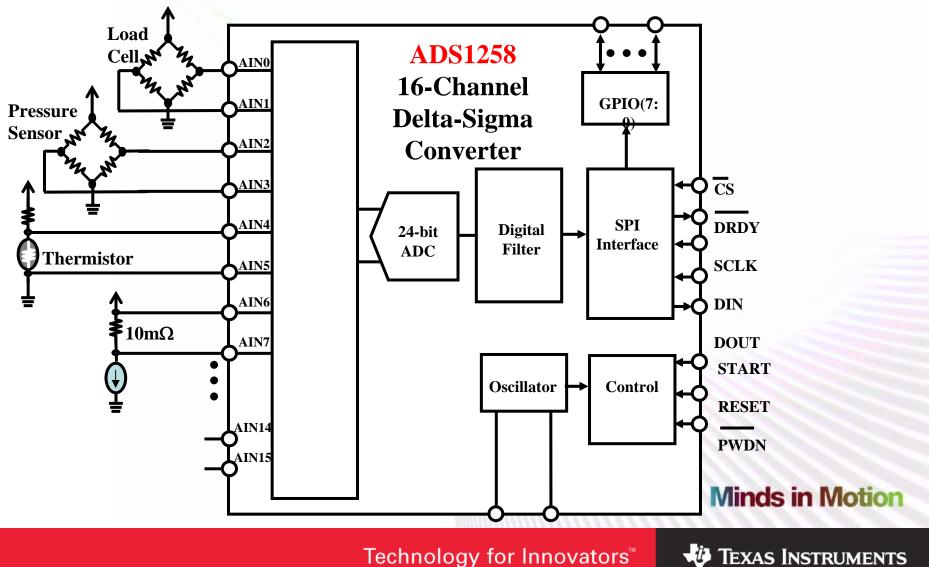

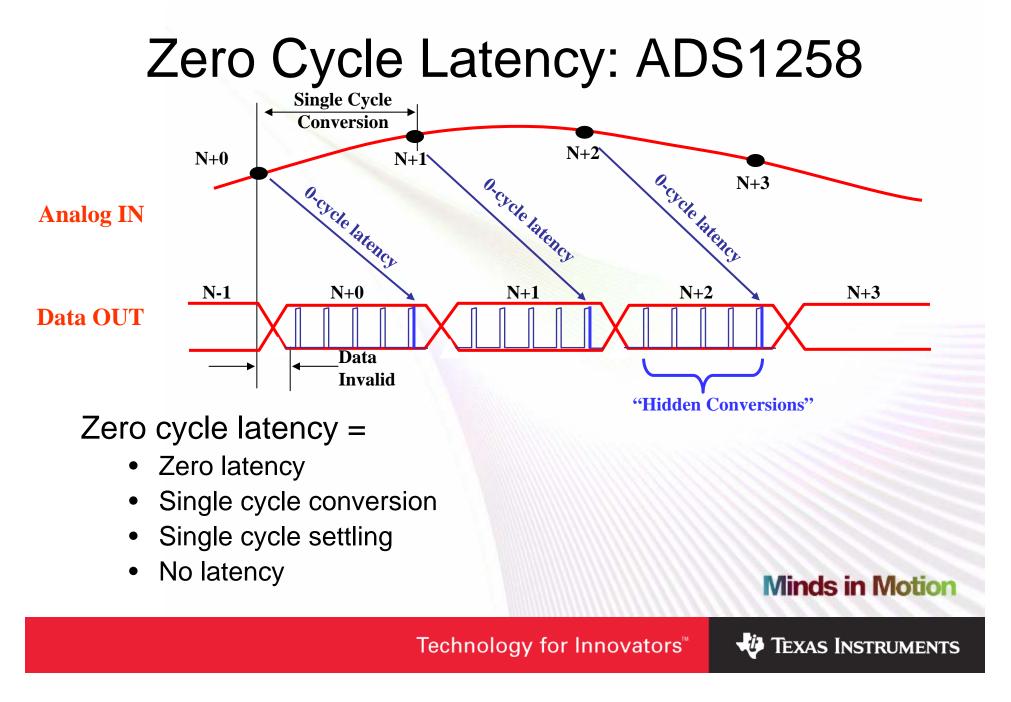

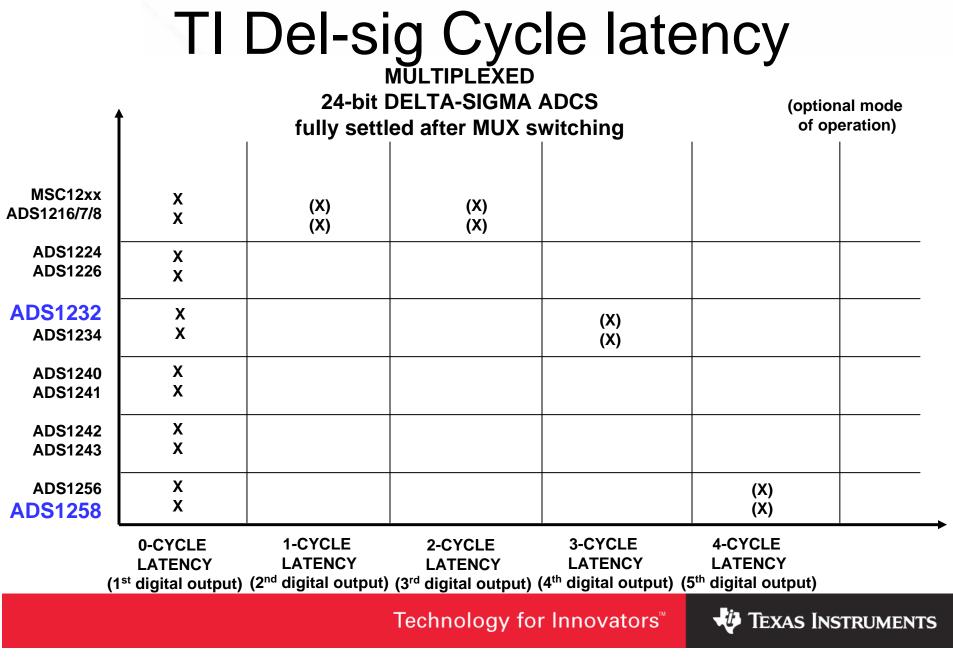

### Agenda

- What Are the Signal Frequencies
  - Analog classes of applications
  - Frequency ranges of ADCs
- Nuts and Bolts of Delta-Sigma Converters
  - $\Delta\Sigma$  converter core and auxiliary  $\Delta\Sigma$  functions
  - Applications for the  $\Delta\Sigma$  converter
- The SAR ADC
  - Input stage dynamics
  - Applications for the SAR converter
- The High-speed Pipeline Topology
  - Driving the capacitive input stage
  - Applications for the pipeline converter
- Conclusion

## The SAR ADC

- Most serial ADCs are SARs or Del-Sigs.
- SARs are best for general-purpose apps.
  - Data loggers
  - Temp sensors
  - Bridge sensors
  - General purpose
- In the market SARs:



- Speed range: >10 ksps to < 5 Msps</p>
- SARs found as
  - Standalone
  - Peripheral in microcontrollers, processors


**Minds in Motion** 


SAR


**Digital** 

Analog-to-

Converter

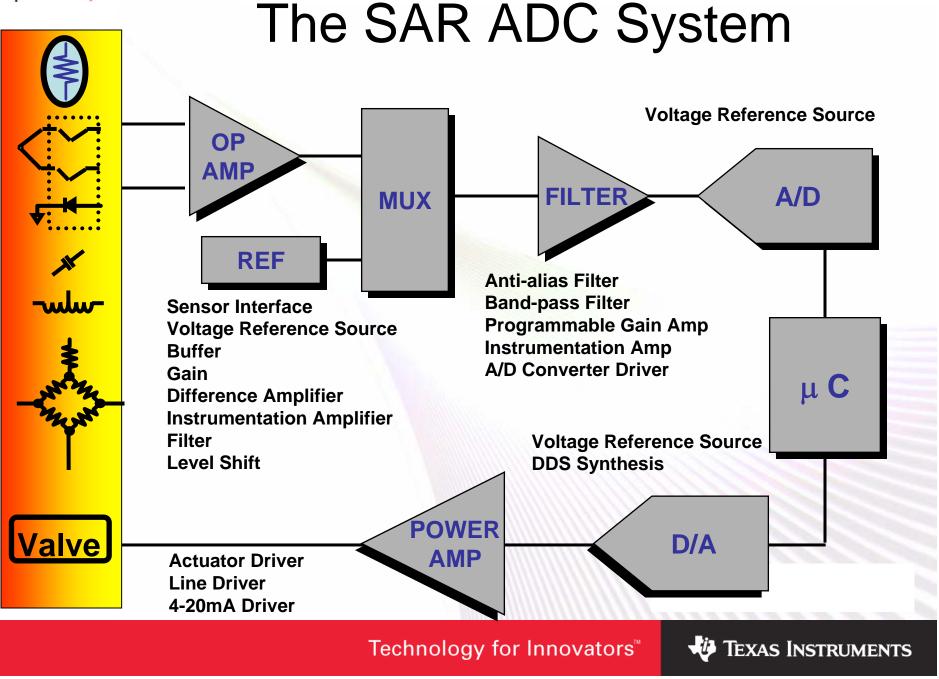


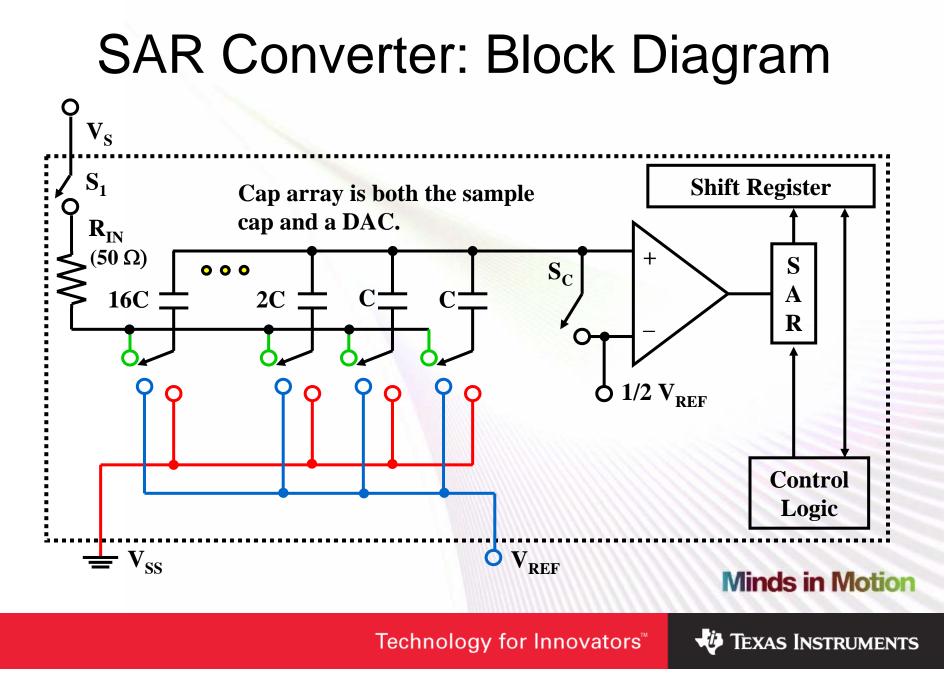

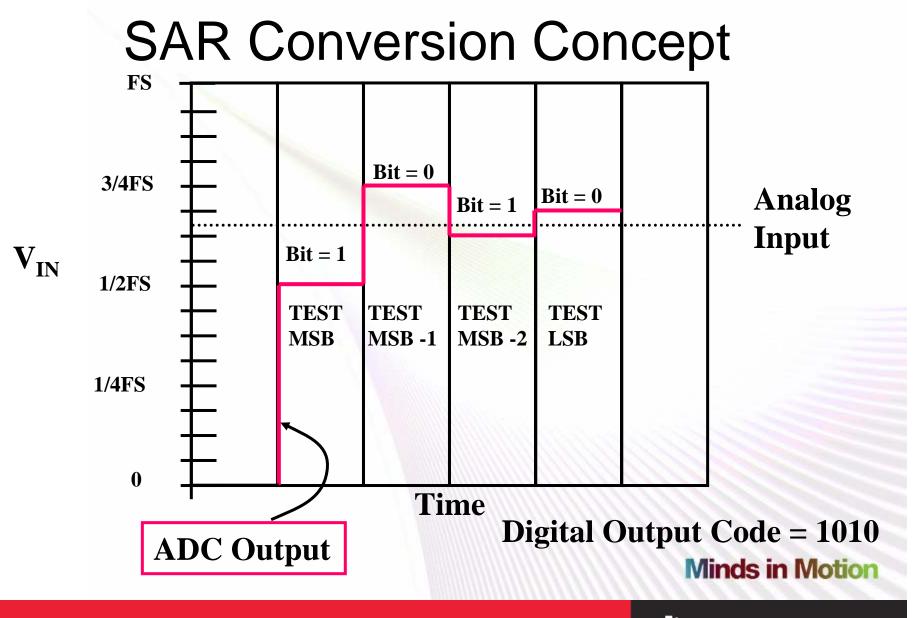

Technology for Innovators<sup>™</sup>

IEXAS INSTRUMENTS

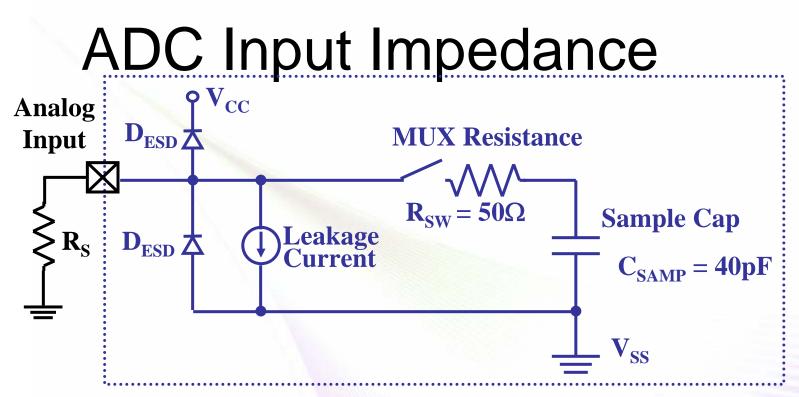


- Input internal impedance is relatively low.
- A high-impedance source increases sample cap charging time.
- Rise time of voltage on


$$C_{SW} \sim (R_S + R_{SAMP}) * C_{SW}$$

#### Minds in Motion


**TEXAS INSTRUMENTS** 

# Sample Cap Charging Time

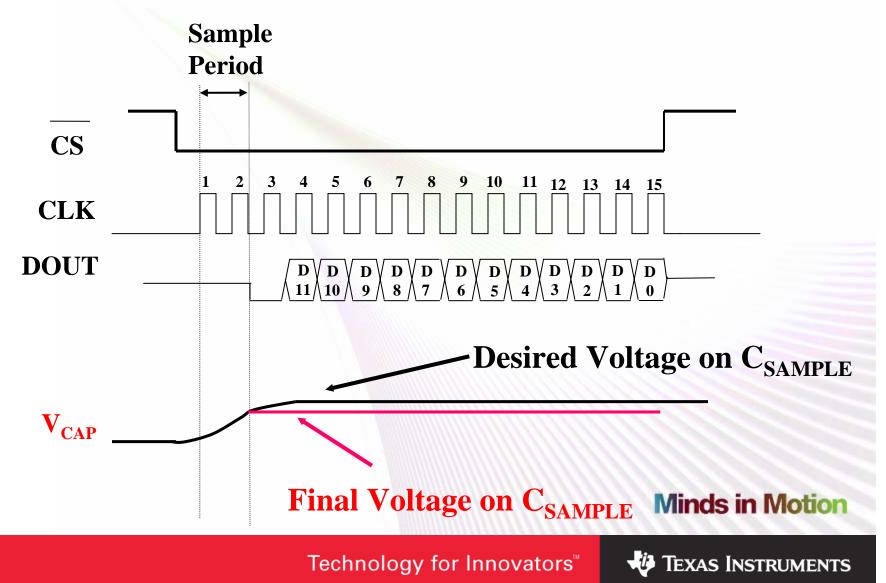

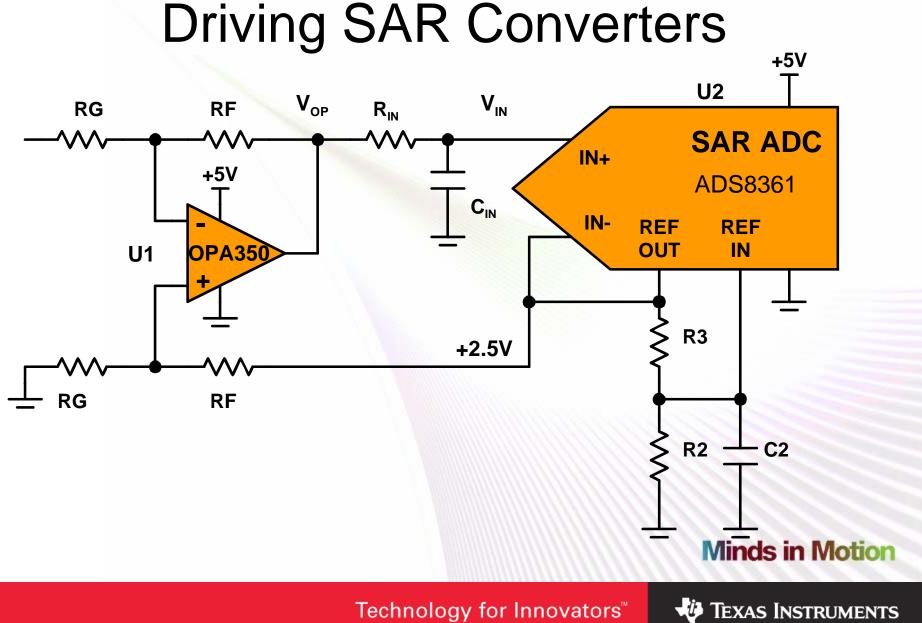


Technology for Innovators<sup>™</sup>

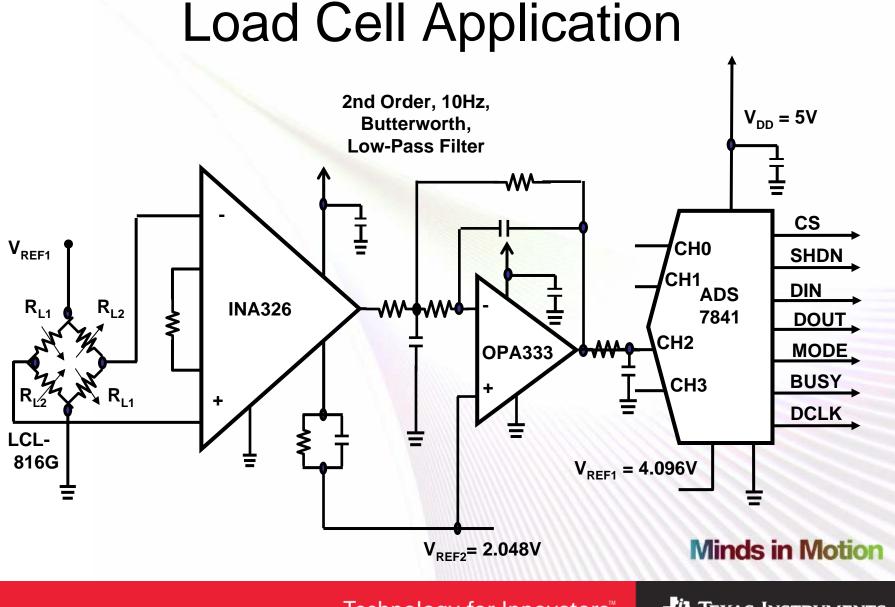

Technology for Innovators<sup>™</sup>

🐺 Texas Instruments

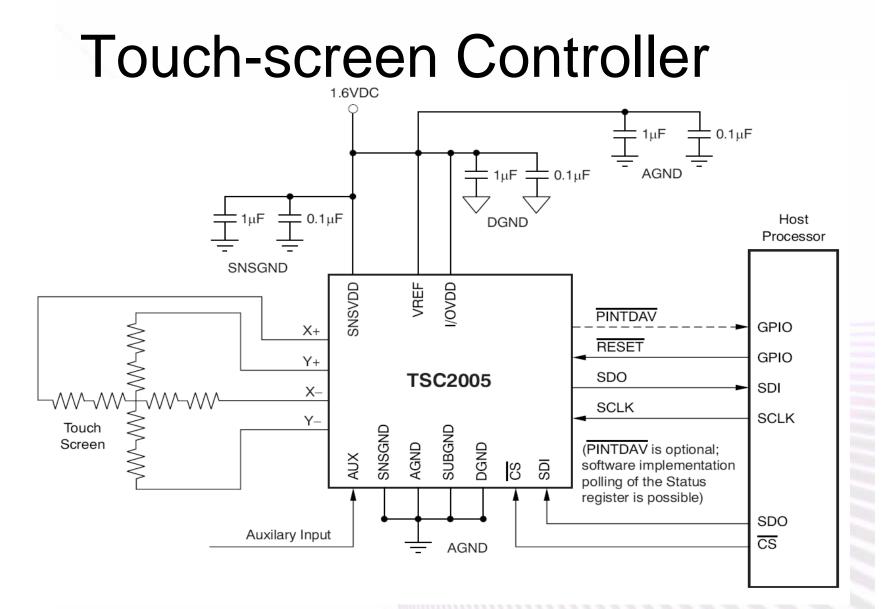

Technology for Innovators<sup>™</sup>

# Agenda

- What Are the Signal Frequencies
  - Analog classes of applications
  - Frequency ranges of ADCs
- Nuts and Bolts of Delta-Sigma Converters
  - $\Delta\Sigma$  converter core and auxiliary  $\Delta\Sigma$  functions
  - Applications for the  $\Delta\Sigma$  converter
- The SAR ADC
  - Input stage dynamics
  - Applications for the SAR converter
- The High-speed Pipeline Topology
  - Driving the capacitive input stage
  - Applications for the pipeline converter
- Conclusion

Technology for Innovators<sup>™</sup>

🤃 Texas Instruments


Minds in Motion

# High Speed: Pipeline Topology

- Pipeline converters fit high-speed applications (5 MHz to 100+MHz).
- Applications where you typically find pipeline converters are:
  - Test and measurement instrumentation
  - Medical imaging
  - Radar systems
  - Data acquisition

Minds in Motion

**TEXAS INSTRUMENTS** 

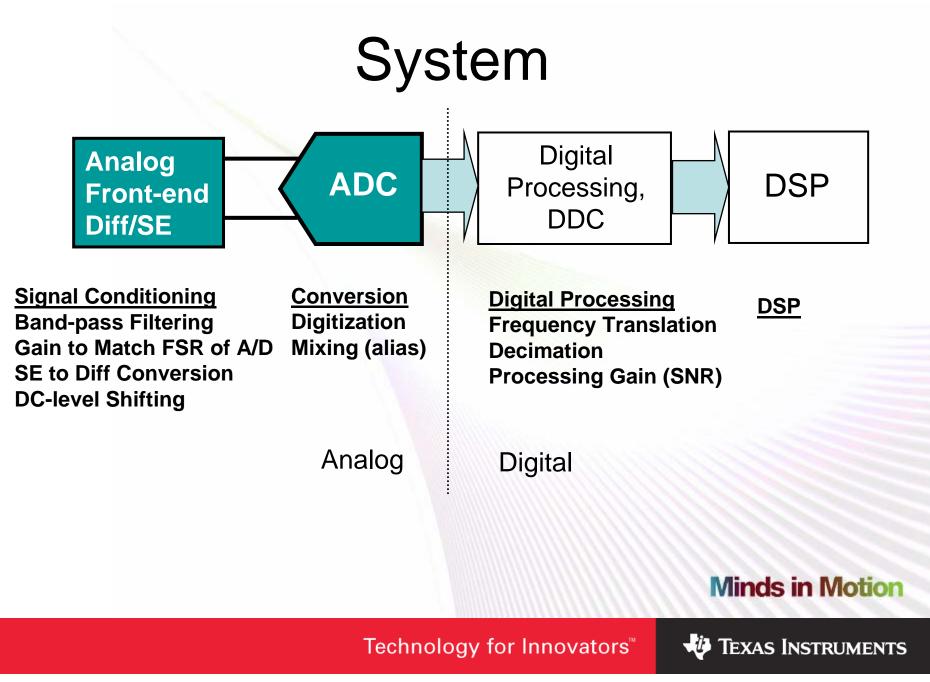

# What's the Application/EE ?

### Time Domain


- Imaging (CCD)
  - Camcorders
  - Digital cameras
  - Scanners
  - RGB/comp. video
  - Test instrumentation
  - Medical
- Important Specs
  - SNR
  - Slew-rate/ tset
  - DNL
  - DC-accuracy/drift

### **Frequency Domain**

- Communications
  - Set-top boxes
  - Cable modems
  - Base stations
  - IF digitizers
  - GPS
  - Frequency synthesizers
- Important Specs
  - SFDR
  - ENOB
  - Analog input bandwith
  - Jitter

#### Minds in Motion
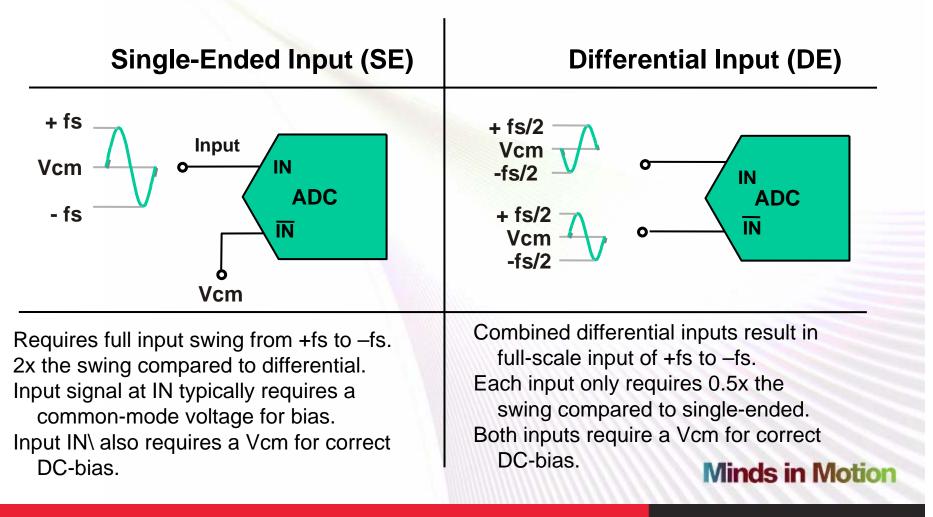
### ADC Interface Solutions Principle Configuration Choices



Technology for Innovators<sup>™</sup>


🦆 Texas Instruments

# SE vs. DE Issues

- Single-ended Inputs (SEs)
  - Degraded dynamic performance (larger FSR).
  - Common-mode voltage and op amp headroom may limit use for DC-coupling.
  - Best suited for **time-domain** applications.
- Differential (DE)
  - Optimized performance due to lower FSR, reduction of even-order and common-mode components.
  - Best for higher input frequencies (IFs).
  - More complex driver circuitry (consider diff-amps).
  - Best suited for frequency-domain applications.

Minds in Motion


# **HS-ADC Simplified Input Circuit**

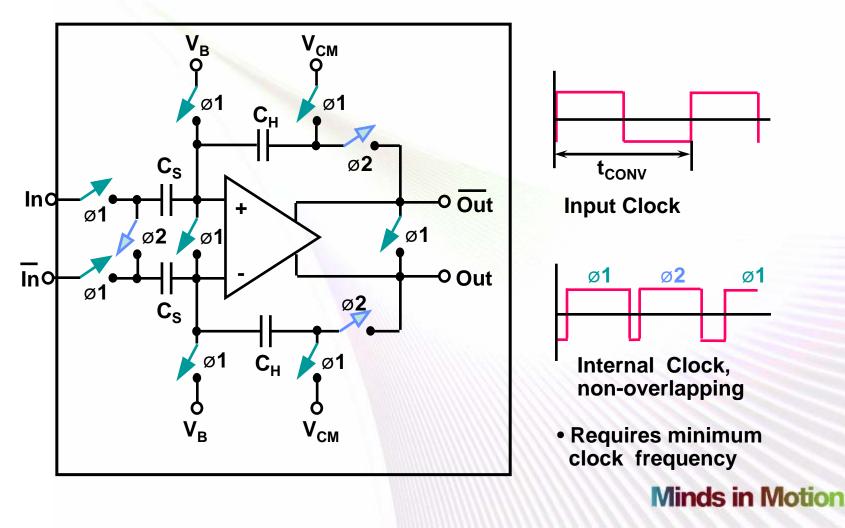

Technology for Innovators<sup>™</sup>

🜵 Texas Instruments

# **Driving Capacitive Input ADCs**

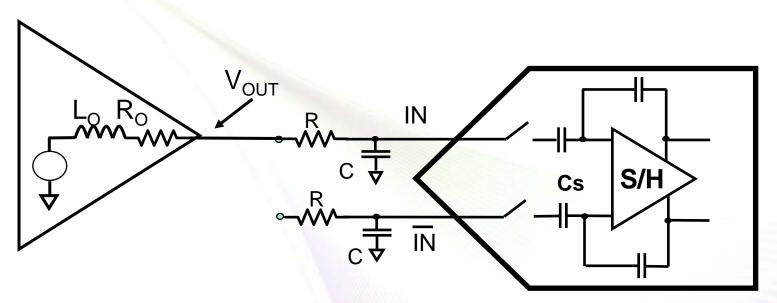


- Due to Op amp's finite (R<sub>O</sub>) output impedance, V<sub>OUT</sub> will drop momentarily when cap load is switched.
- As the output recovers, ringing may occur, which results in increased settling time.
- Use external R: Isolates op amp output from capacitive load and improves settling.
  Minds in Motion

Technology for Innovators<sup>™</sup>

Texas Instruments
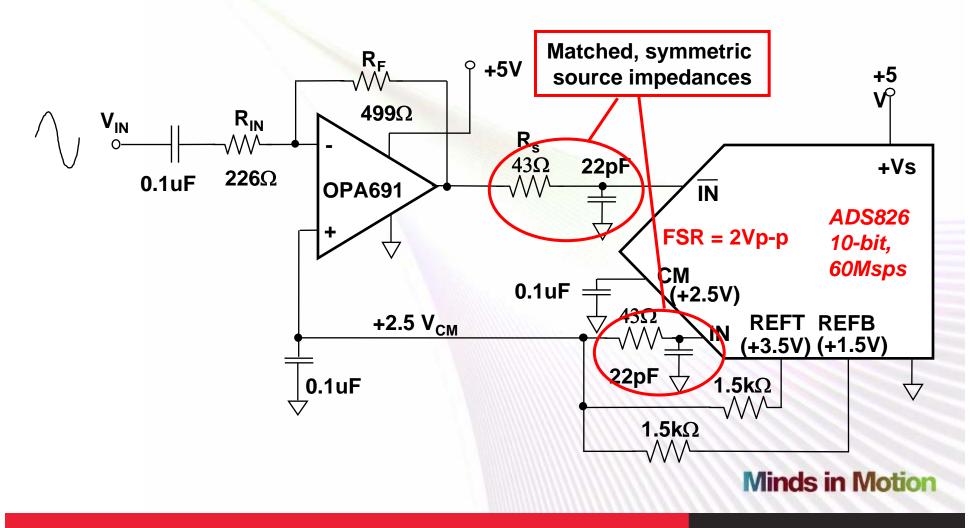
## SE: Interface


Single-ended, AC-coupled driver for single supply operation



Technology for Innovators<sup>™</sup>

🐺 Texas Instruments

# **Differential ADC Driver**

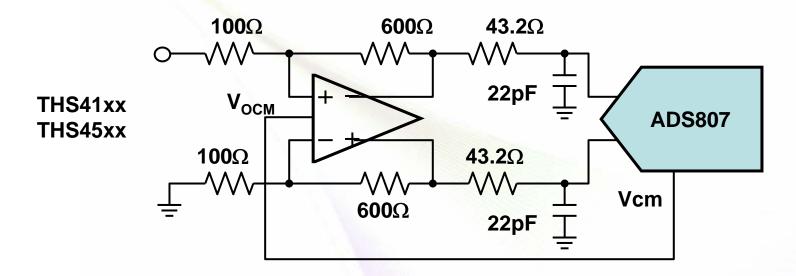


#### **Ideal Baseband Driver Solution**

- No transformer
- VCM matched to ADC
- Good even-order harmonic rejection
- Easily configured for gain and low-pass filter

**Minds in Motion** 

**TEXAS INSTRUMENTS** 

# **Ultra-Sound Receive Chain**

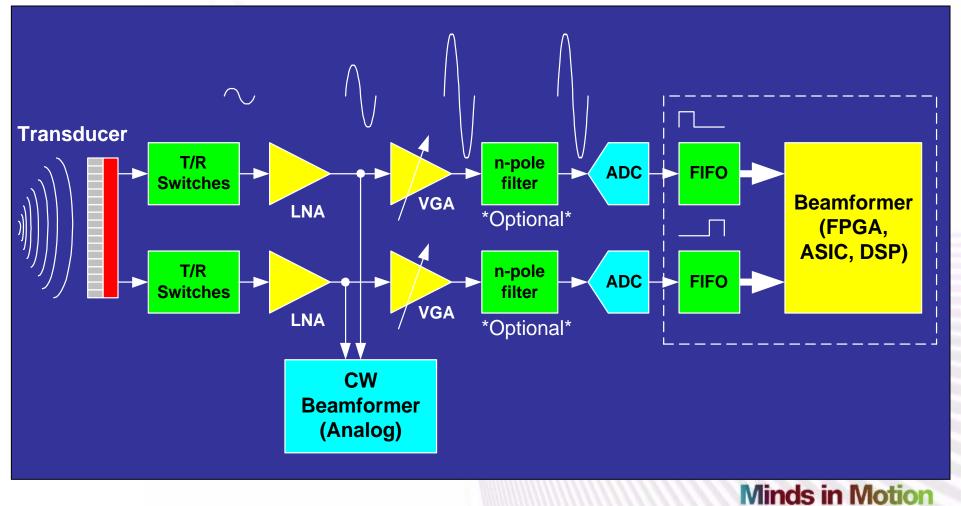

Technology for Innovators<sup>™</sup>

🜵 Texas Instruments

# Conclusion Delta-sigma, SAR, Pipeline ADCs

- Commonalities
  - Input stage
  - Input driving amplifier
- Differences
  - Sampling frequencies
- Appropriate Applications
  - Delta-Sigma: DC up to 30 ksps
  - SAR: 10 ksps up to 5 Msps
  - Pipeline: 1 Msps up to 500 Msps

Minds in Motion

**TEXAS INSTRUMENTS** 

# TI Developer Conference March 7-9, 2007 • Dallas, TX

## Minds in Motion

**TEXAS INSTRUMENTS** 

### **Real World Analog Solutions for Your Processor Applications**

ADC: Delta-Sigma, SAR vs. Pipeline ADCs -When and Where to Use Them

**Bonnie Baker Senior Applications Engineer, DAP** bonnie@ti.com

Technology for Innovators<sup>™</sup>