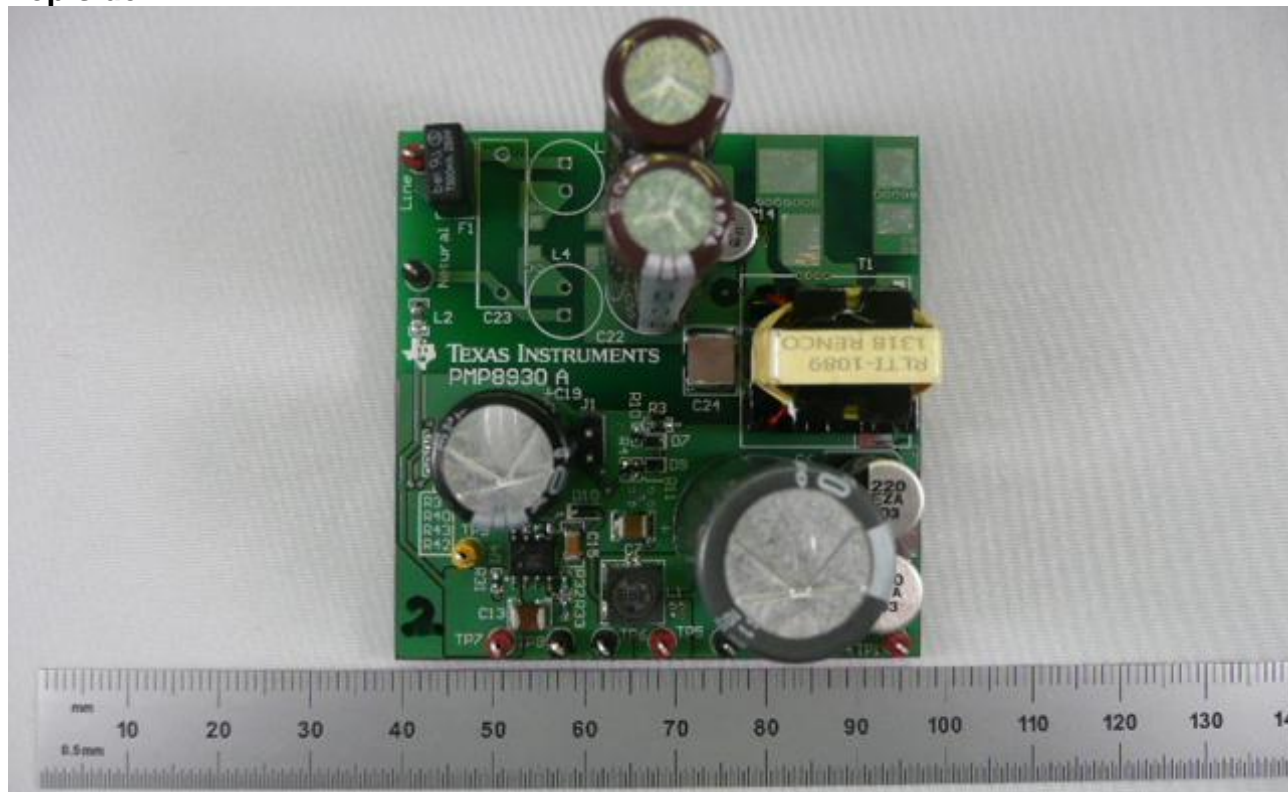



## 1 Photo

The photographs below show the PMP8930 Rev A assembly. This circuit was built on a PMP8930 Rev A PCB.

### Top side




### Bottom side

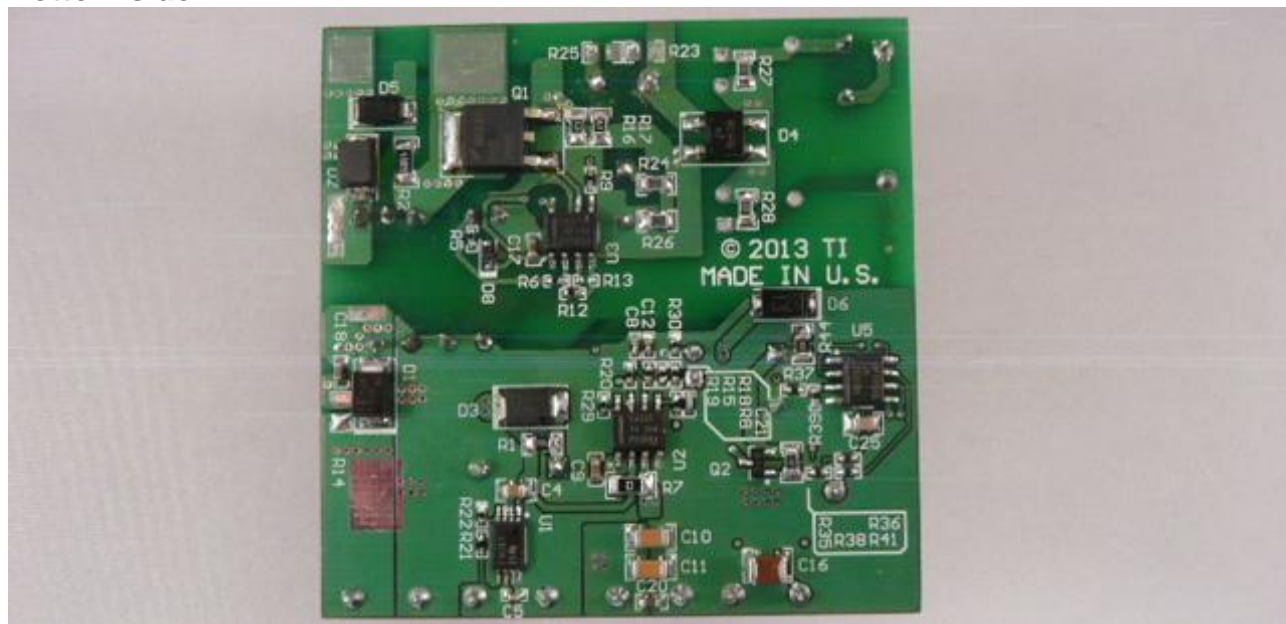

## 2 Efficiency
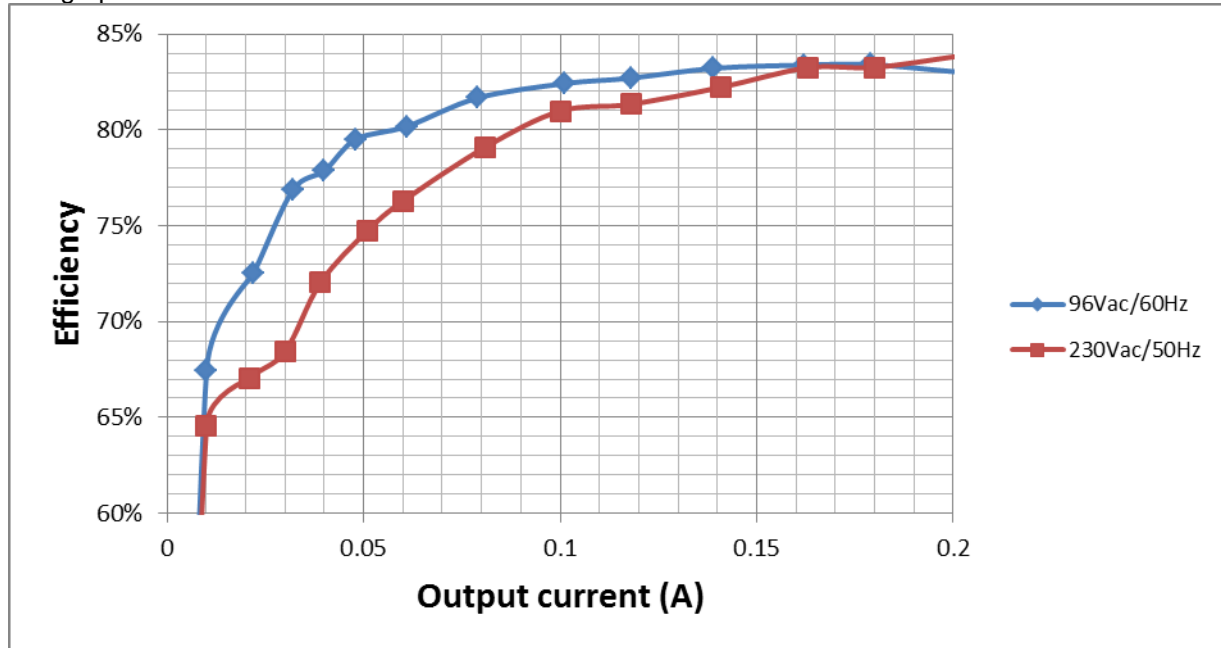
### 2.1 Flyback Converter Efficiency

Flyback converter efficiency was tested by disable U1, U2 and D6. The efficiency data is shown in the tables and graph below.



$V_{in}=96V_{AC}/60Hz$


Vin(V)	Iin(A)	Pin(W)	Vout(V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
96.08	0.1093	4.958	20.48	0.201	4.11648	0.84152	83.03%
96.08	0.09876	4.395	20.48	0.179	3.66592	0.72908	83.41%
96.08	0.0909	3.979	20.48	0.162	3.31776	0.66124	83.38%
96.08	0.08054	3.421	20.48	0.139	2.84672	0.57428	83.21%
96.08	0.07104	2.922	20.48	0.118	2.41664	0.50536	82.70%
96.08	0.06257	2.511	20.49	0.101	2.06949	0.44151	82.42%
96.08	0.05176	1.983	20.5	0.079	1.6195	0.3635	81.67%
96.08	0.0423	1.561	20.52	0.061	1.25172	0.30928	80.19%
96.08	0.03492	1.24	20.54	0.048	0.98592	0.25408	79.51%
96.08	0.0305	1.056	20.56	0.04	0.8224	0.2336	77.88%
96.08	0.02556	0.8571	20.59	0.032	0.65888	0.19822	76.87%
96.08	0.019525	0.626	20.64	0.022	0.45408	0.17192	72.54%
96.08	0.01044	0.306	20.64	0.01	0.2064	0.0996	67.45%
96.08	0.00245	0.06388	20.71	0	0	0.06388	0.00%

**Vin=230V<sub>AC</sub>/50Hz**

Vin(V)	Iin(A)	Pin(W)	Vout(V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
230	0.06336	4.905	20.46	0.201	4.11246	0.79254	83.84%
230	0.05824	4.423	20.46	0.18	3.6828	0.7402	83.26%
230	0.0537	4.006	20.46	0.163	3.33498	0.67102	83.25%
230	0.048	3.51	20.47	0.141	2.88627	0.62373	82.23%
230	0.04195	2.971	20.48	0.118	2.41664	0.55436	81.34%
230	0.03669	2.529	20.48	0.1	2.048	0.481	80.98%
230	0.0313	2.099	20.5	0.081	1.6605	0.4385	79.11%
230	0.02507	1.613	20.51	0.06	1.2306	0.3824	76.29%
230	0.02191	1.4	20.52	0.051	1.04652	0.35348	74.75%
230	0.018349	1.112	20.54	0.039	0.80106	0.31094	72.04%
230	0.015537	0.902	20.58	0.03	0.6174	0.2846	68.45%
230	0.011724	0.645	20.59	0.021	0.43239	0.21261	67.04%
230	0.00674	0.319	20.6	0.01	0.206	0.113	64.58%
230	0.0015	0.069	20.65	0	0	0.069	0.00%
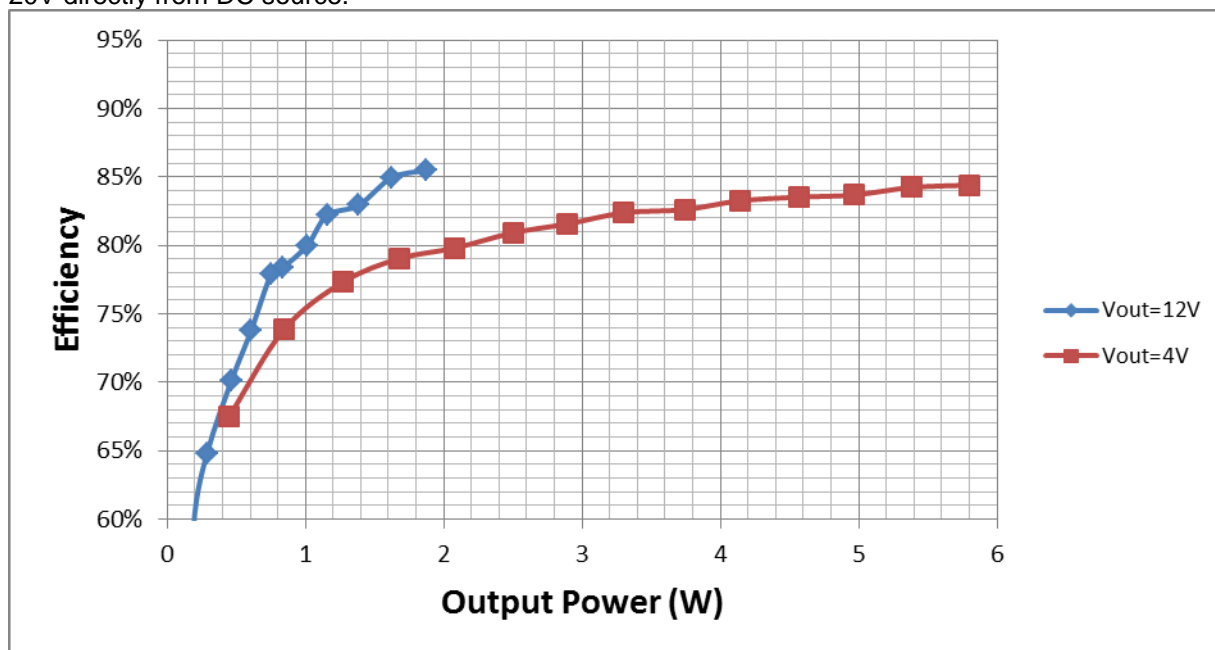
## 2.2 Synchronous Buck Converter Efficiency

The efficiency of the synchronous buck converter (TPS54335 and its related circuit) was tested by applying a 20V directly from DC source.



### $V_{out}=4V_{DC}$ (J1 open)

Vin(V)	Iin(A)	Pin(W)	Vout(V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
20.03	0.343	6.87029	4.13	1.404	5.79852	1.07177	84.40%
20.04	0.319	6.39276	4.13	1.304	5.38552	1.00724	84.24%
20.04	0.296	5.93184	4.13	1.202	4.96426	0.96758	83.69%
20.03	0.273	5.46819	4.13	1.106	4.56778	0.90041	83.53%
20.04	0.248	4.96992	4.13	1.002	4.13826	0.83166	83.27%
20.04	0.226	4.52904	4.13	0.906	3.74178	0.78726	82.62%
20.05	0.2	4.01	4.13	0.8	3.304	0.706	82.39%
20.05	0.177	3.54885	4.13	0.701	2.89513	0.65372	81.58%
20.05	0.154	3.0877	4.13	0.605	2.49865	0.58905	80.92%
20.06	0.13	2.6078	4.13	0.504	2.08152	0.52628	79.82%
20.06	0.106	2.12636	4.13	0.407	1.68091	0.44545	79.05%
20.06	0.082	1.64492	4.13	0.308	1.27204	0.37288	77.33%
20.06	0.057	1.14342	4.14	0.204	0.84456	0.29886	73.86%
20.07	0.033	0.66231	4.14	0.108	0.44712	0.21519	67.51%


**V<sub>out</sub>=12V<sub>DC</sub> (J1 shorted)**

Vin(V)	Iin(A)	Pin(W)	Vout(V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
20.08	0.109	2.18872	11.92	0.157	1.87144	0.31728	85.50%
20.09	0.095	1.90855	11.92	0.136	1.62112	0.28743	84.94%
20.09	0.083	1.66747	11.92	0.116	1.38272	0.28475	82.92%
20.09	0.07	1.4063	11.92	0.097	1.15624	0.25006	82.22%
20.1	0.063	1.2663	11.92	0.085	1.0132	0.2531	80.01%
20.1	0.053	1.0653	11.93	0.07	0.8351	0.2302	78.39%
20.1	0.048	0.9648	11.93	0.063	0.75159	0.21321	77.90%
20.1	0.041	0.8241	11.93	0.051	0.60843	0.21567	73.83%
20.1	0.033	0.6633	11.93	0.039	0.46527	0.19803	70.14%
20.1	0.022	0.4422	11.93	0.024	0.28632	0.15588	64.75%
20.11	0.016	0.32176	11.93	0.016	0.19088	0.13088	59.32%
20.11	0.004	0.08044	11.93	0	0	0.08044	0.00%


### 3 Thermal Images

The thermal images below show a top view and bottom view of the board with 96V<sub>ao</sub>/60Hz input ( $P_{in}=10W$ ). The ambient temperature was 20°C with no forced air flow. The output was at full load: 20V/50mA, 5V/10mA, 4V/1.4A, and 3.3V/50mA.

#### Top Side

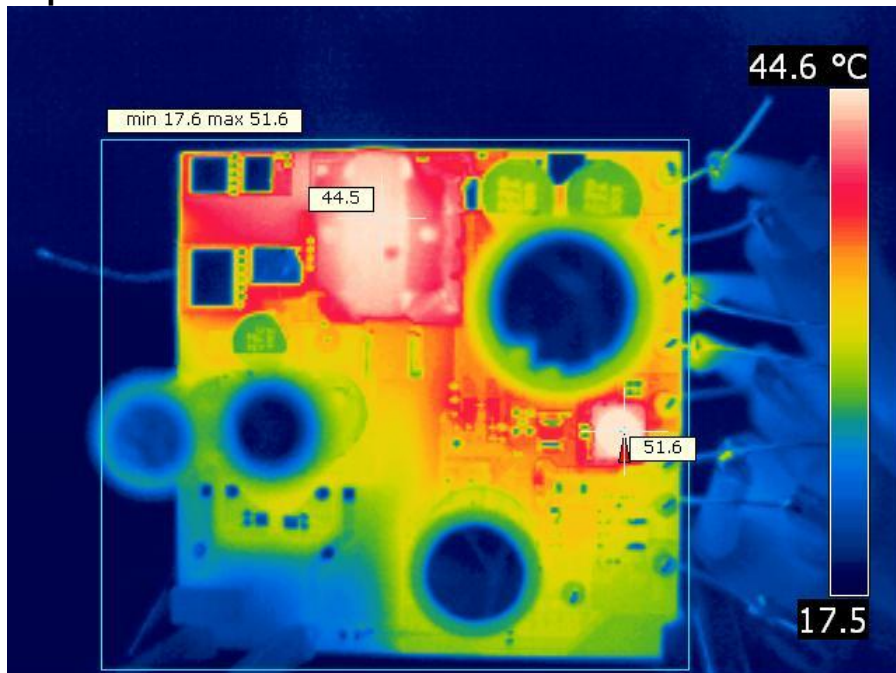

#### Bottom Side

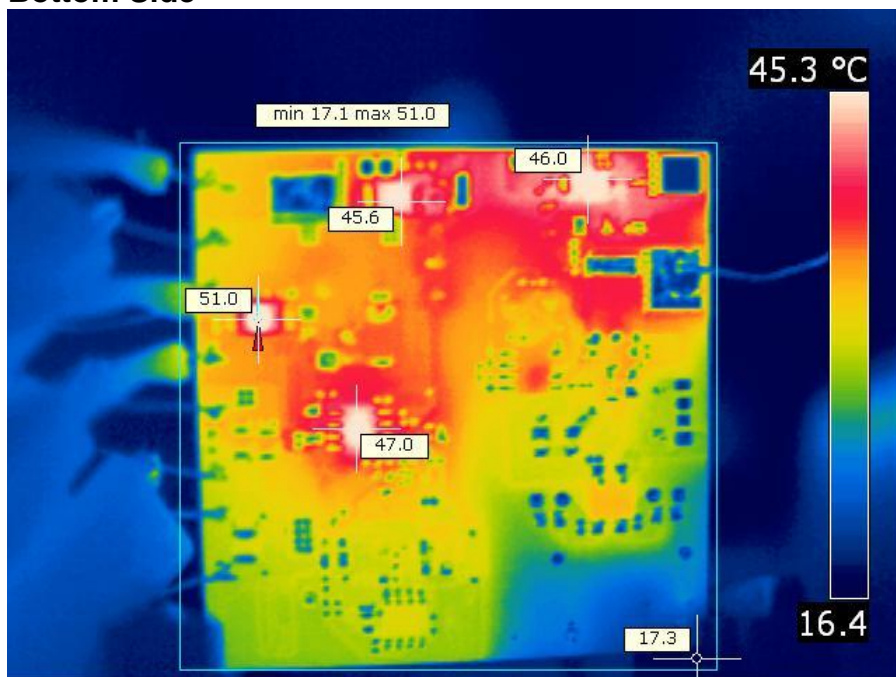




## 4 Startup

The output voltage at startup is shown in the images below. Channel 1: 3.3V, Channel 2: 4V or 12V, Channel 3: 5V, Channel 4: 20V.

### 4.1 Start Up @ 96V<sub>ac</sub>: 20V/50mA, 5V/10mA, 4V/1.4A, and 3.3V/50mA.


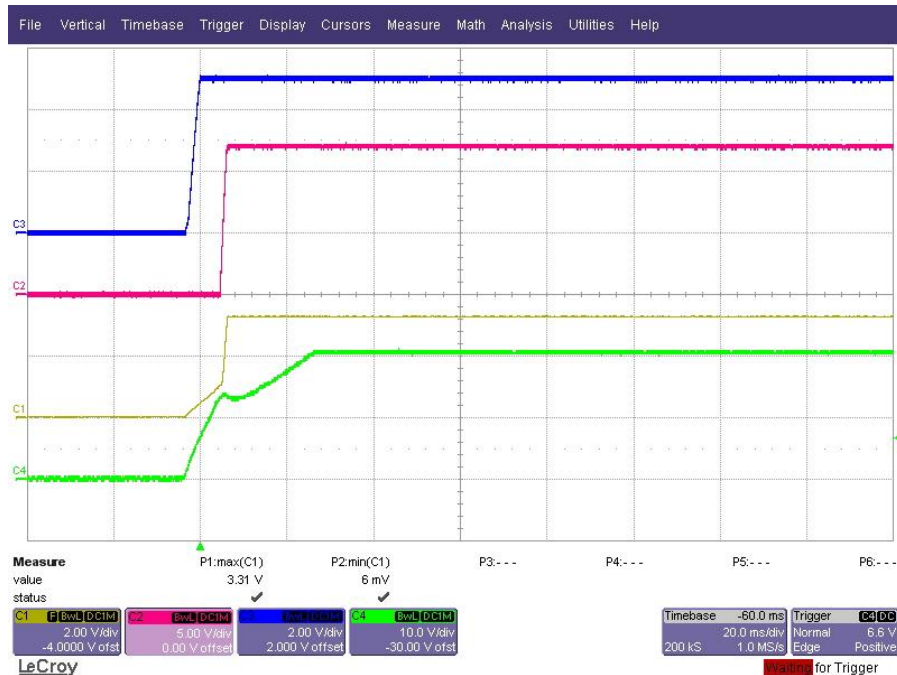
### 4.2 Start Up @ 96V<sub>ac</sub>: 20V/50mA, 5V/10mA, 12V/150mA, and 3.3V/50mA.



### 4.3 Start Up @ 275V<sub>ac</sub>: 20V/50mA, 5V/10mA, 4V/1.4A, and 3.3V/50mA.




### 4.4 Start Up @ 275V<sub>ac</sub>: 20V/50mA, 5V/10mA, 12V/150mA, and 3.3V/50mA.




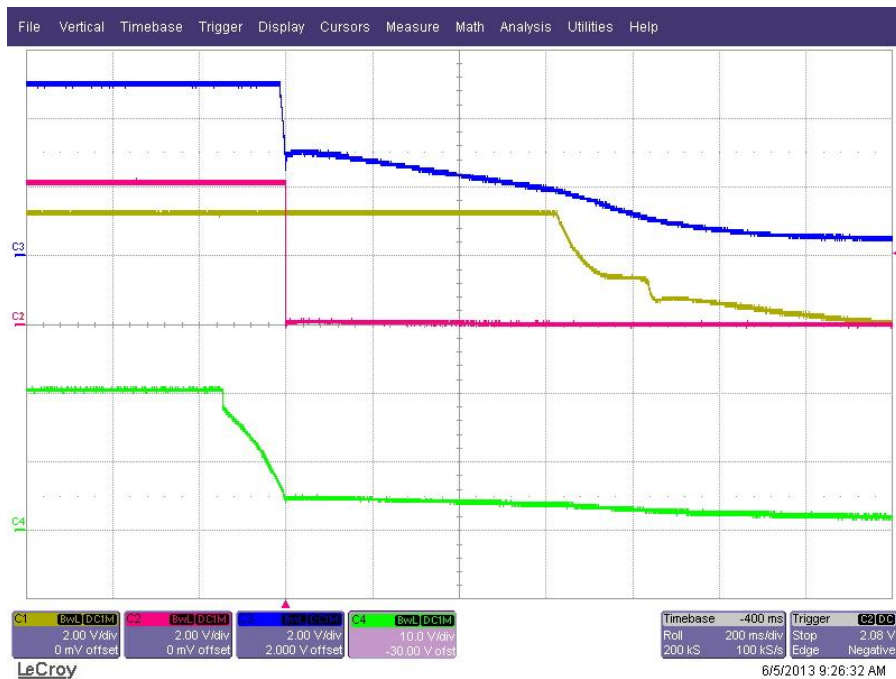
## 5 Turn off


The output voltage at turn off transient is shown in the images below at full load (20V/50mA, 5V/10mA, 12V/150mA, and 3.3V/50mA) and 96V<sub>ac</sub>/60Hz input. Channel 1: 3.3V, Channel 2: 4V or 12V, Channel 3: 5V, Channel 4: 20V.




## 6 Output Ripple Voltages - Full Load



The output ripple voltages are shown in the plots below with 96V<sub>ac</sub> input voltage.

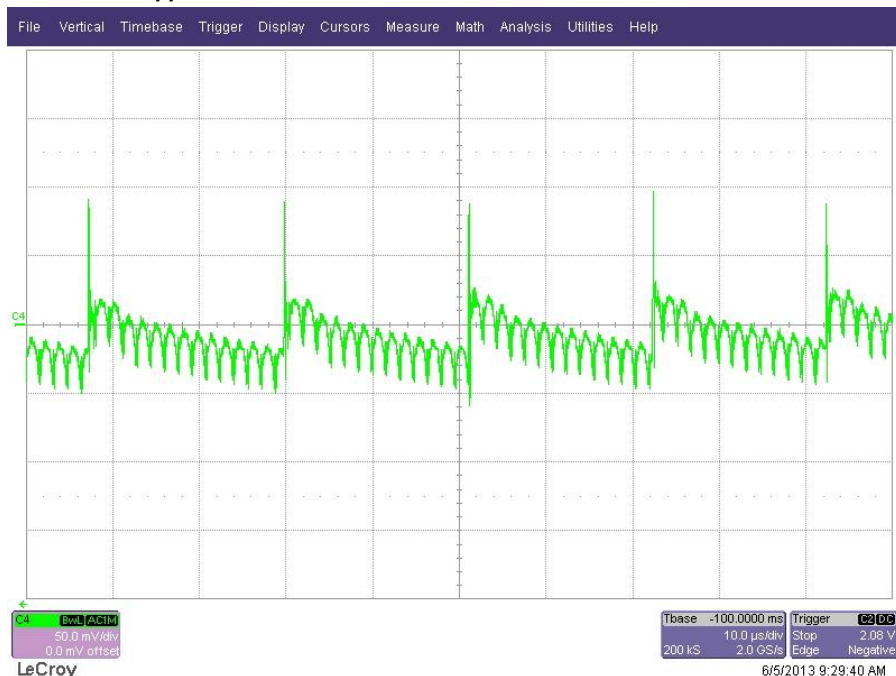
### 6.1 20V<sub>ripple</sub> with loads 20V/50mA, 5V/10mA, 4V/1.4A, and 3.3V/50mA:


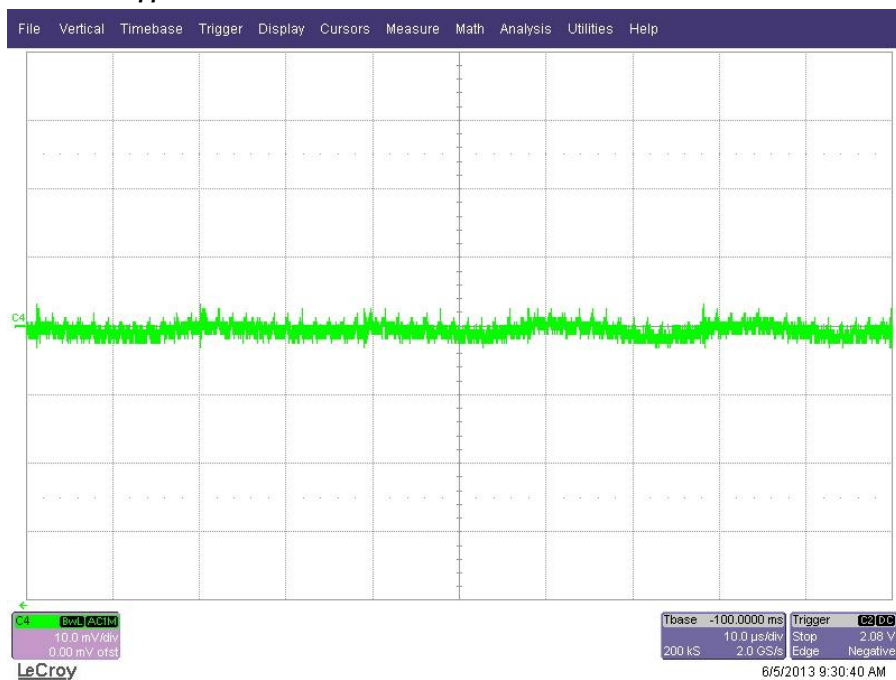
### 6.2 5V<sub>ripple</sub> with loads 20V/50mA, 5V/10mA, 4V/1.4A, and 3.3V/50mA:




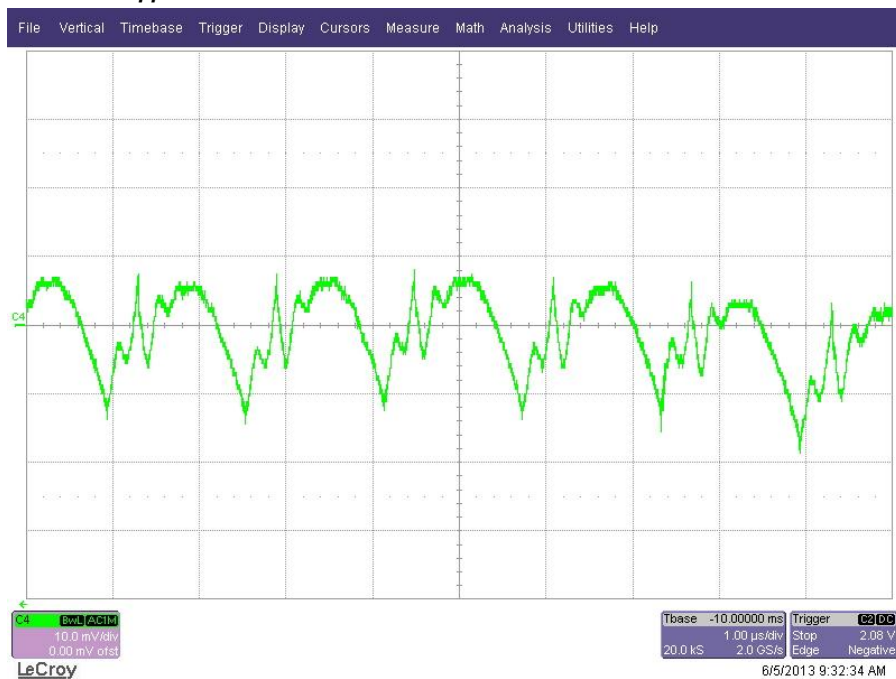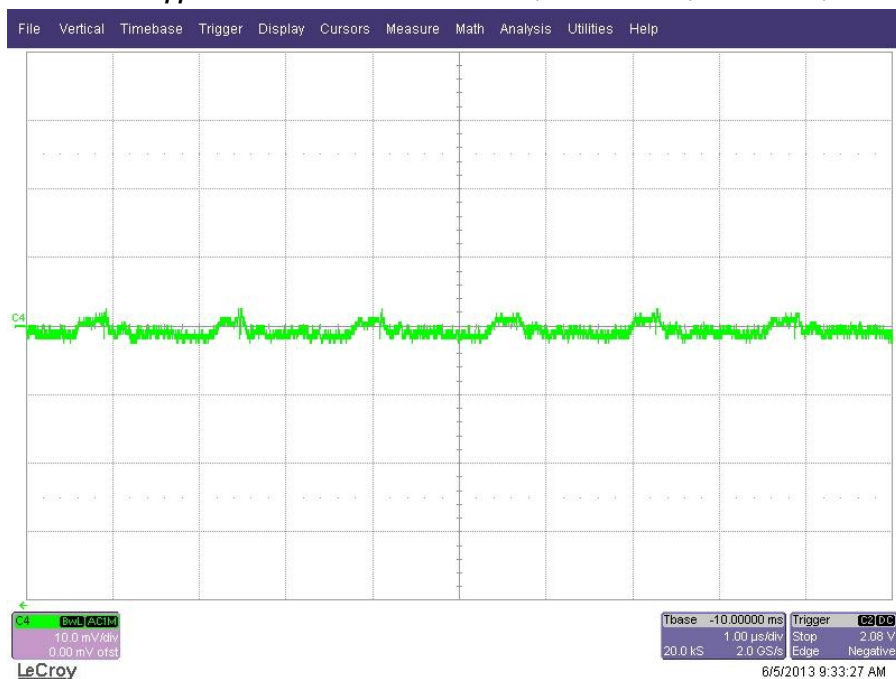**6.3 4V<sub>ripple</sub> with loads 20V/50mA, 5V/10mA, 4V/1.4A, and 3.3V/50mA:****6.4 3.3V<sub>ripple</sub> with loads 20V/50mA, 5V/10mA, 4V/1.4A, and 3.3V/50mA:**

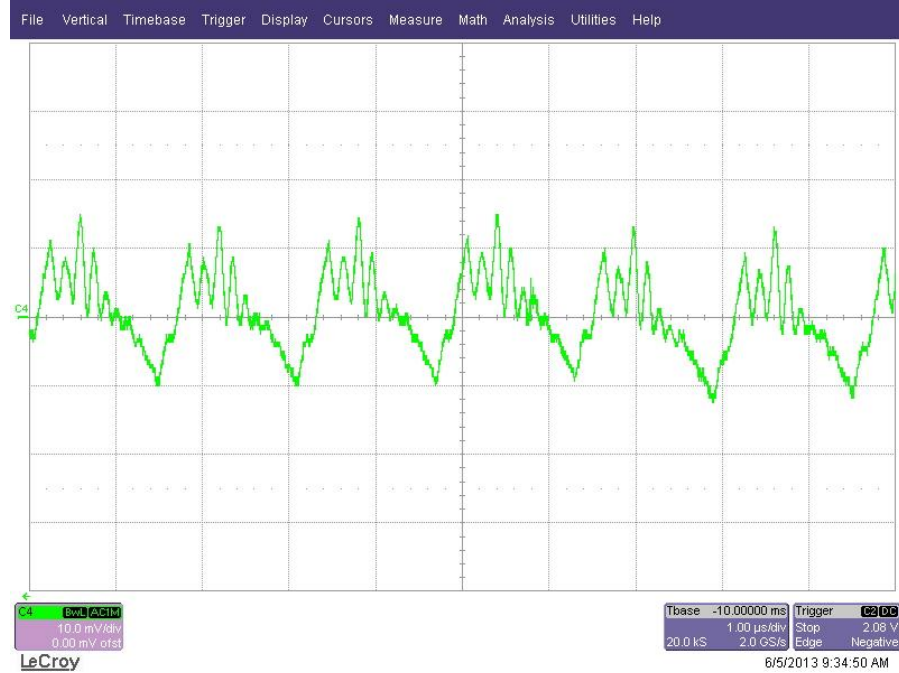**6.5  $12V_{ripple}$  with loads 20V/50mA, 5V/10mA, 12V/150mA, and 3.3V/50mA:**

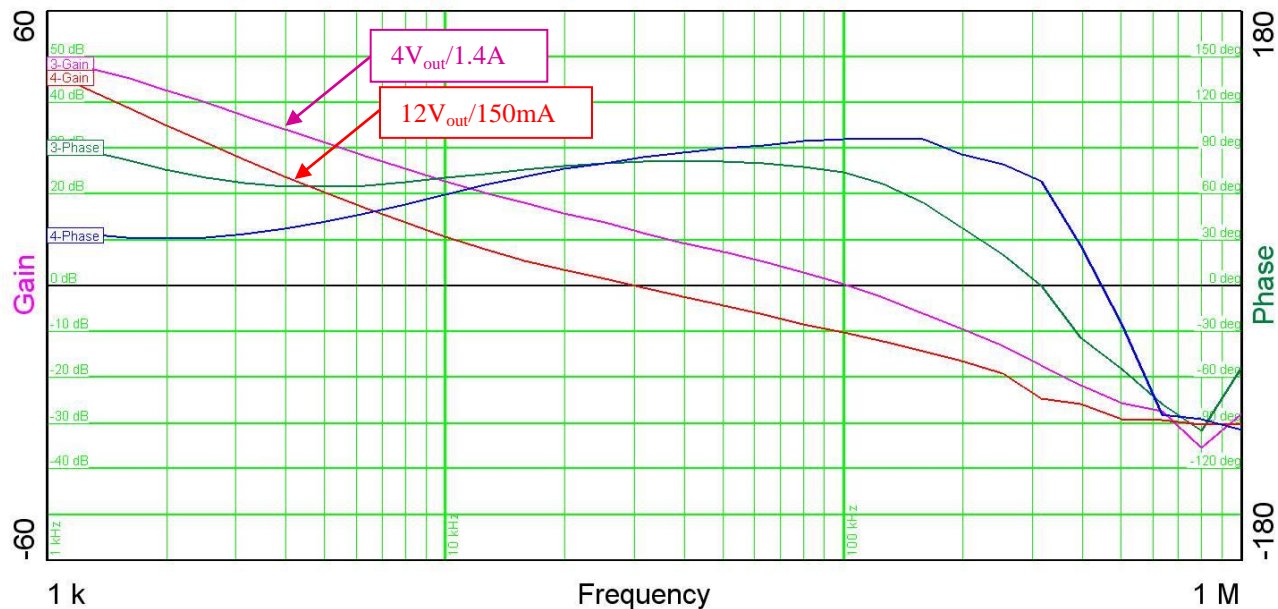
## 7 Synchronous Buck Converter Loop Response

The plot below shows the frequency response of the feedback loop. The input voltage was 20V.


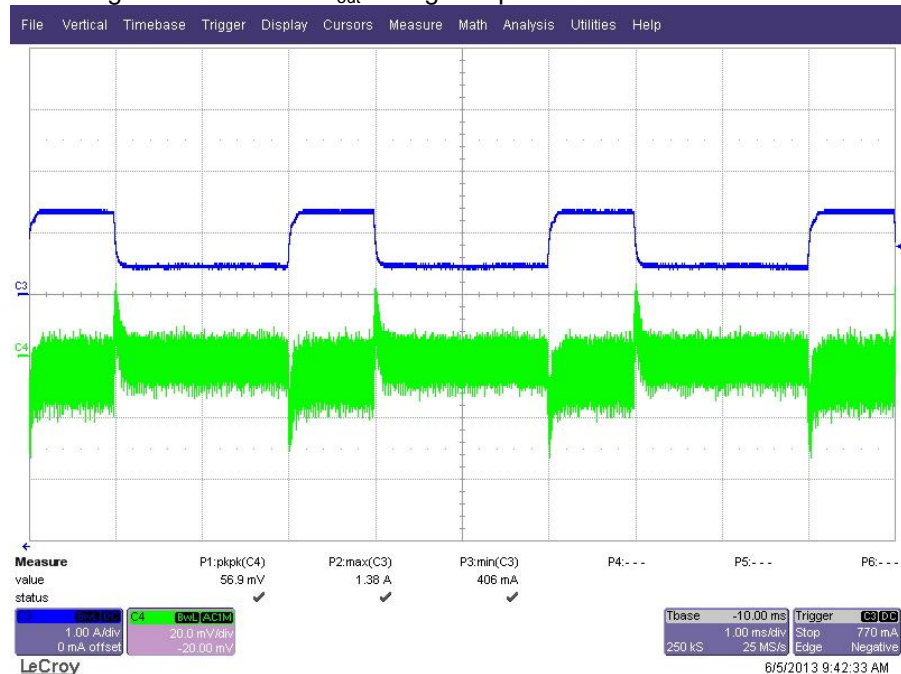
## 8 Load Transients


The image below shows  $4V_{out}$  voltage response to a **0.5A** to **1.4A** load transient.




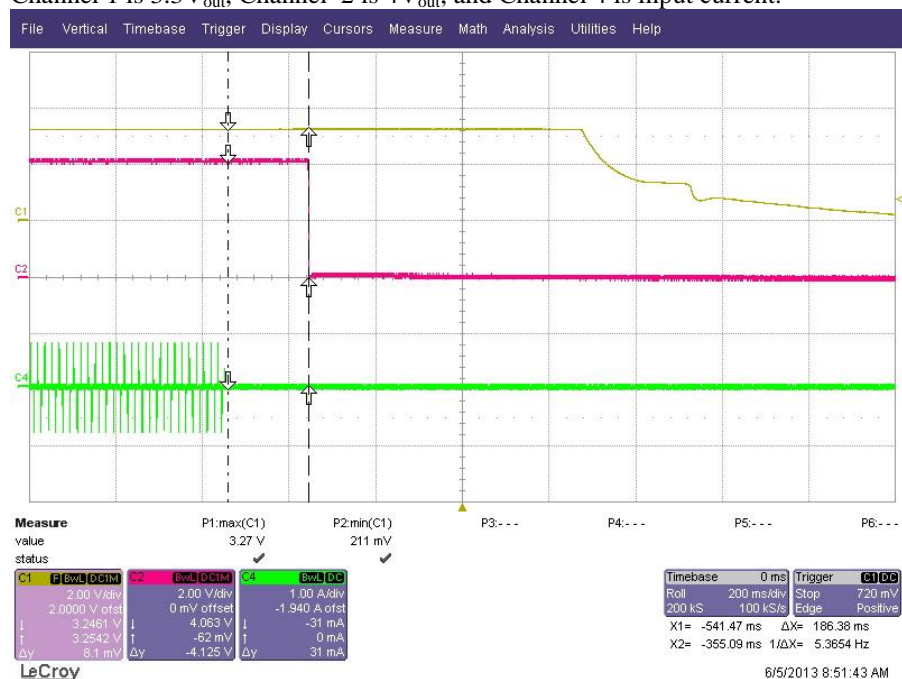
## 9 Hold-up Time


The image below shows the hold-up time with full load (20V/50mA, 5V/10mA, 12V/150mA, and 3.3V/50mA) applied. Channel 1 is 3.3V<sub>out</sub>, Channel 2 is 4V<sub>out</sub>, and Channel 4 is input current.




## 10 Switching Waveforms

The image below shows key switching waveforms of PMP8930RevA. The waveforms are measured with full load (20V/50mA, 5V/10mA, 12V/150mA, and 3.3V/50mA).

### 10.1 Primary MOSFET Q1 @ 96V/60Hz

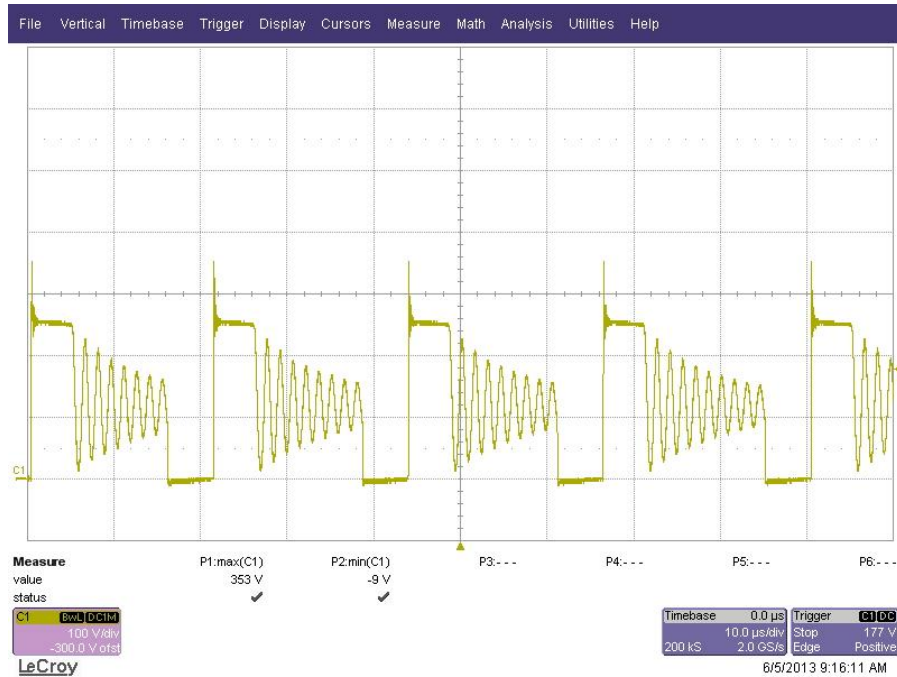

### 10.2 Primary MOSFET Q1 @ 275V/50Hz

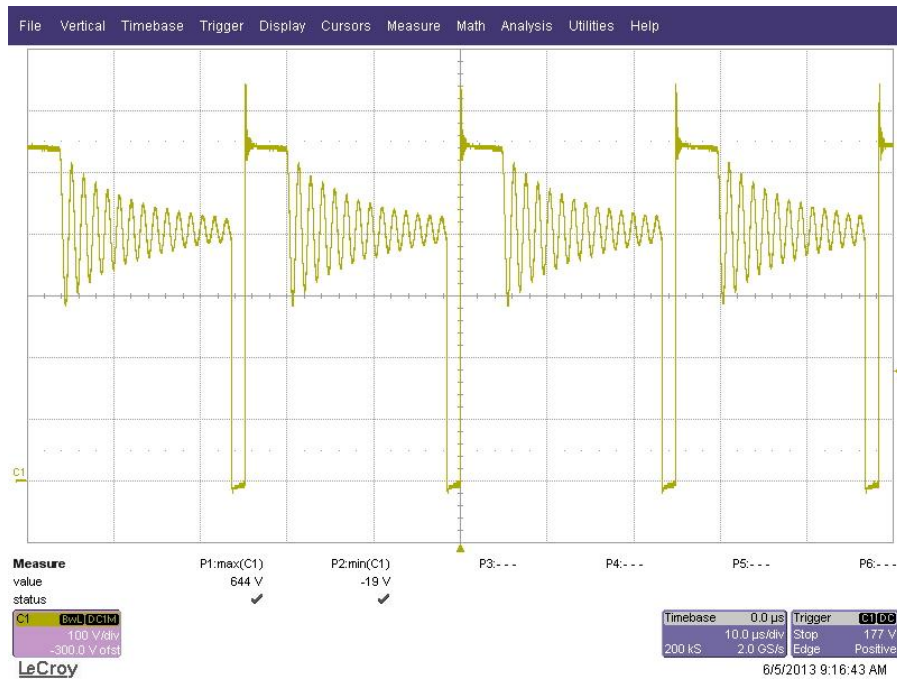

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated