

Reducing Output Ripple Voltage of TPS61070 During PFM-Mode Operation

S.K. Loo

PMP Portable Power

ABSTRACT

This application report presents a possible solution to reduce the output ripple voltage of the TPS61070 during PFM-mode operation, and primarily focuses on modifying the feedback loop response and how that affects the output ripple voltage for Bluetooth™ headset application with a single-cell alkaline battery.

Contents

1	Introduction	2
2	Experiment	3
3	Summary	10

List of Figures

1	High Ripple Voltage Causes the Bluetooth Chipset to Draw Excessive Current During Sniff-Mode Operation.....	2
2	Test Circuit of TPS61070 for Single-Cell Alkaline Battery to 1.8-V Output	3
3	Output Ripple Voltage During PFM-Mode Operation With Original EVM Setup of 4.7- μ H Inductor and 2 \times 4.7- μ F Output Capacitors (Note the change of voltage scale on the right to accommodate the waveforms.)	3
4	Output Ripple Voltage During PFM-Mode Operation With Additional 22- μ F Output Capacitor (C5)	4
5	Output Ripple Voltage During PFM-Mode Operation With Additional 120- μ F Output Capacitor (C5)	4
6	Output Ripple Voltage During PFM-Mode Operation With 10- μ H Inductance, 2 \times 4.7- μ F Output Capacitor (Note the change of voltage scale on the right to accommodate the waveforms.)	5
7	Output Ripple Voltage During PFM-Mode Operation With 10- μ H Inductance, 2 \times 4.7- μ F + Additional 22- μ F (C5) Output Capacitor	5
8	Output Ripple Voltage During PFM-Mode Operation With 10- μ H Inductance, 2 \times 4.7- μ F + Additional 120- μ F(C5) Output Capacitor	5
9	Output Ripple Voltage During PFM-Mode Operation With 22- μ H Inductance, 2 \times 4.7- μ F + 22- μ F (C5) Output Capacitor.....	6
10	Output Ripple Voltage During PFM-Mode Operation With 22- μ H Inductance, 2 \times 4.7- μ F + 120- μ F (C5) Output Capacitor	6
11	Output Ripple Voltage During PFM-Mode Operation With 1-nF Feedforward Capacitor (Cff), 4.7- μ H Inductor, and With Different Output Capacitors	7
12	Output Ripple Voltage During PFM-Mode Operation With 10-nF Feedforward Capacitor (Cff), 4.7- μ H Inductor, and With Different Output Capacitors	7
13	Output Ripple Voltage During PFM-Mode Operation With 100-nF Feedforward Capacitor (Cff), 4.7- μ H Inductor, and With Different Output Capacitors	7
14	Output Ripple Voltage During PFM-Mode Operation With 1-nF Feedforward Capacitor (Cff), 10- μ H Inductor, and With Different Output Capacitors	8
15	Output Ripple Voltage During PFM-Mode Operation With 10-nF Feedforward Capacitor (Cff), 10- μ H Inductor, and With Different Output Capacitors	8
16	Output Ripple Voltage During PFM-Mode Operation With 100-nF Feedforward	

	Capacitor (Cff), 10- μ H Inductor, and With Different Output Capacitors	9
17	Output Ripple Voltage During PFM-Mode Operation With 1-nF Feedforward Capacitor (Cff), 22- μ H Inductor, and With Different Output Capacitors	9
18	Output Ripple Voltage During PFM-Mode Operation With 10-nF Feedforward Capacitor (Cff), 22- μ H Inductor, and With Different Output Capacitors.....	10
19	Output Ripple Voltage During PFM-Mode Operation With 100-nF Feedforward Capacitor (Cff), 22- μ H Inductor, and With Different Output Capacitors.....	10
20	Output Ripple Voltage and Current Waveform From TPS61070 During Sniff-Mode Operation of Bluetooth Headset With 1-nF Feedforward Capacitor (Cff) and With 2 \times 22- μ F Output Capacitors.....	11
21	Output Ripple Voltage and Current Waveform From TPS61070 During Sniff-Mode Operation of Bluetooth Headset With 10-nF Feedforward Capacitor (Cff) and With 2 \times 22- μ F Output Capacitors.....	11

1 Introduction

The battery life for Bluetooth™ headset primarily depends on the power consumption of the Bluetooth chipset, as well as the efficiency of the dc/dc converter. Due to the unique current pulses drawing from the Bluetooth chipset at a different operating mode, it places a stringent requirement on the dc/dc converter to achieve high efficiency throughout the operating conditions.

Achieving high converter efficiency (>85%) during talk mode is not difficult as the average current drawn is between 20 mA and ~30 mA. However, during sniff-mode (or standby-mode) operation, the system draws low current (μ A) most of the time, with repetitive current pulses of 20 mA to ~ 30 mA periodically. In order to achieve high converter efficiency, power safe-mode (or pulse frequency modulation) operation is required to improve the converter efficiency to greater than 75%.

During power safe-mode operation, the converter only operates when the output voltage trips below a lower set threshold voltage, ramping up the output voltage with several pulses until the output voltage exceeds the upper set threshold voltage, and the converter enters the power safe-mode operation again. The output ripple voltage of this power safe-mode operation, therefore, is much higher than fixed frequency operation, and could easily exceed 50 mV. This violates the ripple voltage requirement of the Bluetooth chipset and might cause abnormal current drawn by the chipset.

Figure 1 shows this phenomenon in the actual circuit with our TPS61070 converter boosting from a single-cell alkaline battery to 1.8 V during sniff-mode operation. The pulse-frequency modulation (PFM) ripple voltage of > 40 mV causes the system to draw extra current.

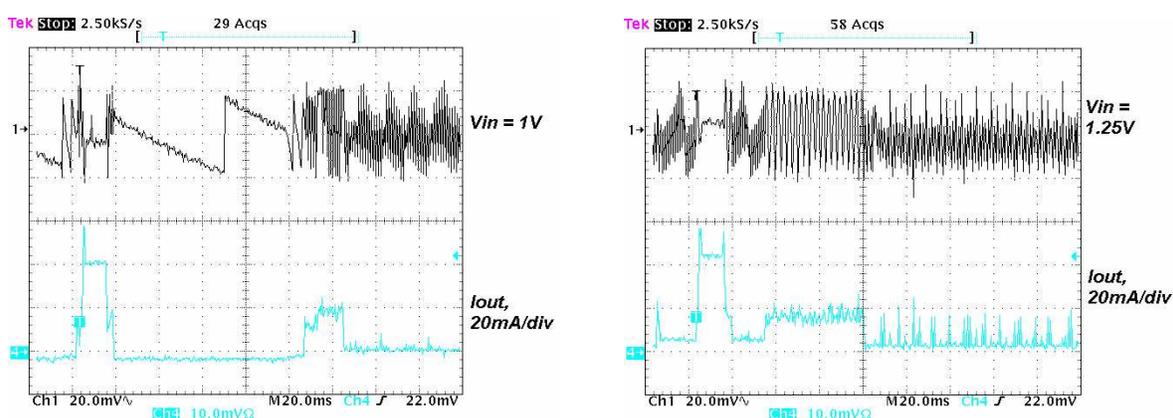


Figure 1. High Ripple Voltage Causes the Bluetooth Chipset to Draw Excessive Current During Sniff-Mode Operation

Bluetooth is a trademark of Bluetooth SIG, Inc..

2 Experiment

TPS61070EVM evaluation module (EVM) was used in this experiment with slight modification to find a practical solution of reducing the PFM ripple voltage for such an application. Figure 2 shows the schematic for this evaluation. Figure 3 shows the screen captures of the output ripple voltage before any modification of the EVM, with inductor value of 4.7 μH and output capacitor of $2 \times 4.7 \mu\text{F}$. The left image of Figure 3 shows the ripple voltage when no load is connected at the output, and the right image of Figure 3 shows the ripple voltage when periodic current pulses are drawn to the load to simulate the sniff-mode operation of a Bluetooth headset.

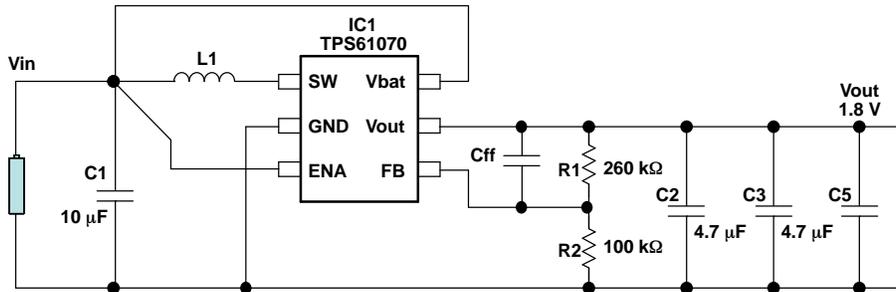


Figure 2. Test Circuit of TPS61070 for Single-Cell Alkaline Battery to 1.8-V Output

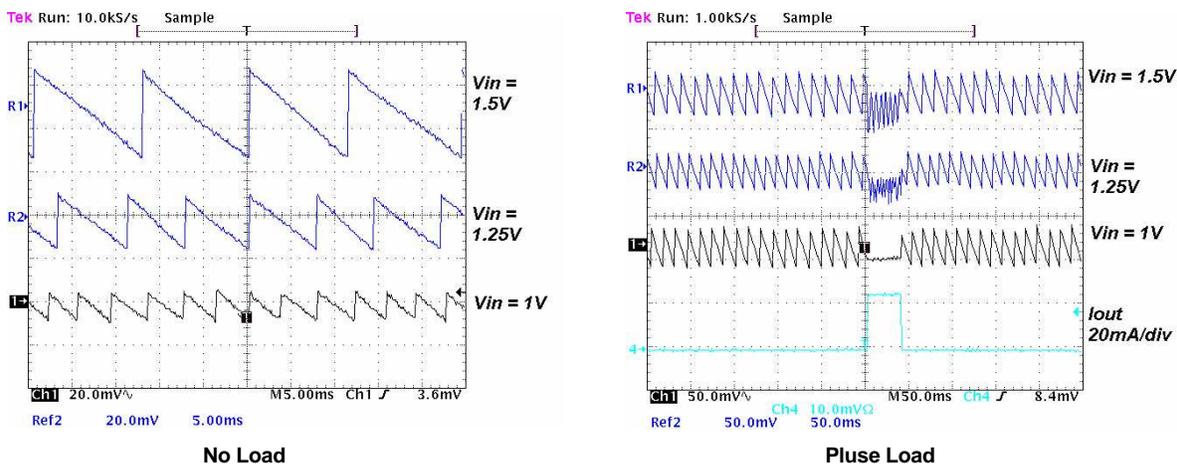


Figure 3. Output Ripple Voltage During PFM-Mode Operation With Original EVM Setup of 4.7- μH Inductor and $2 \times 4.7\text{-}\mu\text{F}$ Output Capacitors (Note the change of voltage scale on the right to accommodate the waveforms.)

Although adding an output capacitor to the circuit improved the ripple voltage at no-load steady state, it did not improve the ripple voltage during periodic pulse current-mode operation (simulated sniff-mode operation). Figure 4 and Figure 5 show the ripple voltage after adding a 22- μF output capacitor and 120- μF output capacitor, respectively.

Experiment

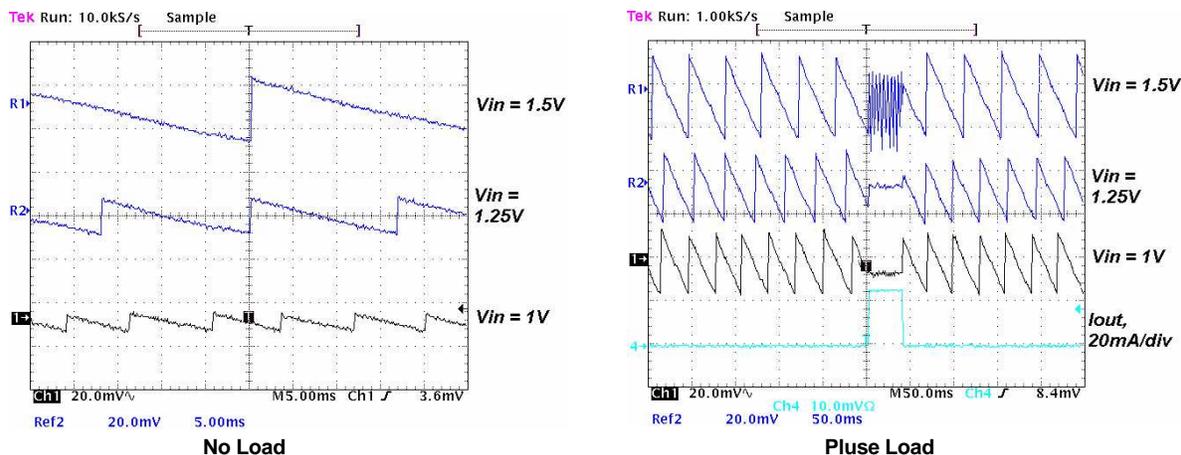


Figure 4. Output Ripple Voltage During PFM-Mode Operation With Additional 22- μ F Output Capacitor (C5)

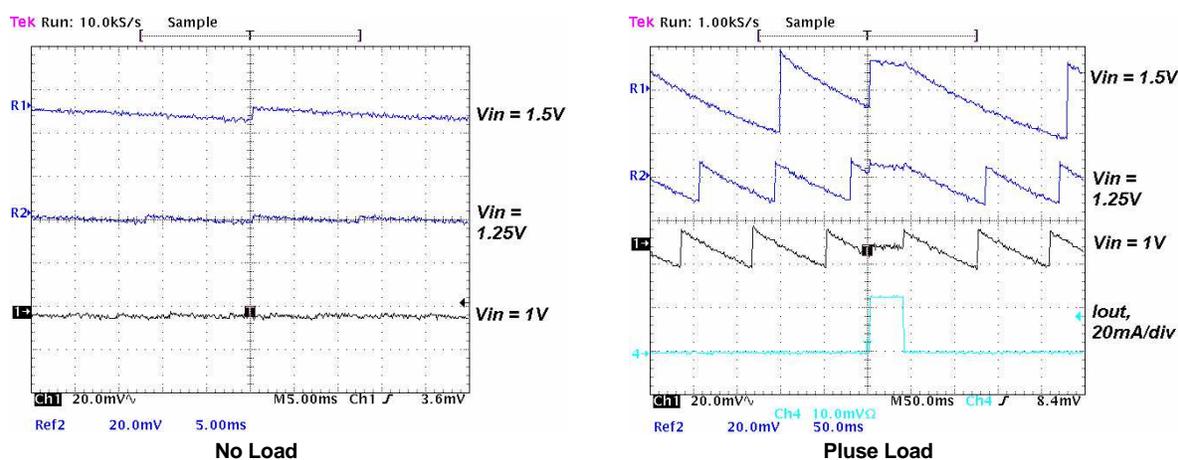


Figure 5. Output Ripple Voltage During PFM-Mode Operation With Additional 120- μ F Output Capacitor (C5)

Increasing the inductance from 4.7 μ H to 10 μ H also did not improve the ripple voltage during the pulse load. Figure 6 shows the output ripple voltage with $2 \times 4.7\text{-}\mu\text{F}$ output capacitors. Figure 7 and Figure 8 show the ripple voltage with the addition of 22- μ F and 120- μ F output capacitors, respectively

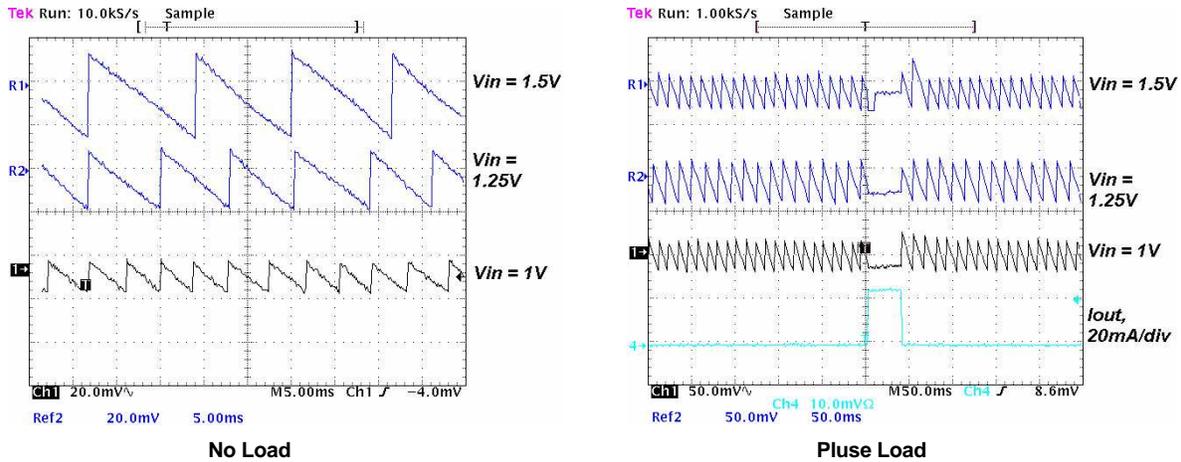


Figure 6. Output Ripple Voltage During PFM-Mode Operation With 10- μ H Inductance, 2 \times 4.7- μ F Output Capacitor (Note the change of voltage scale on the right to accommodate the waveforms.)

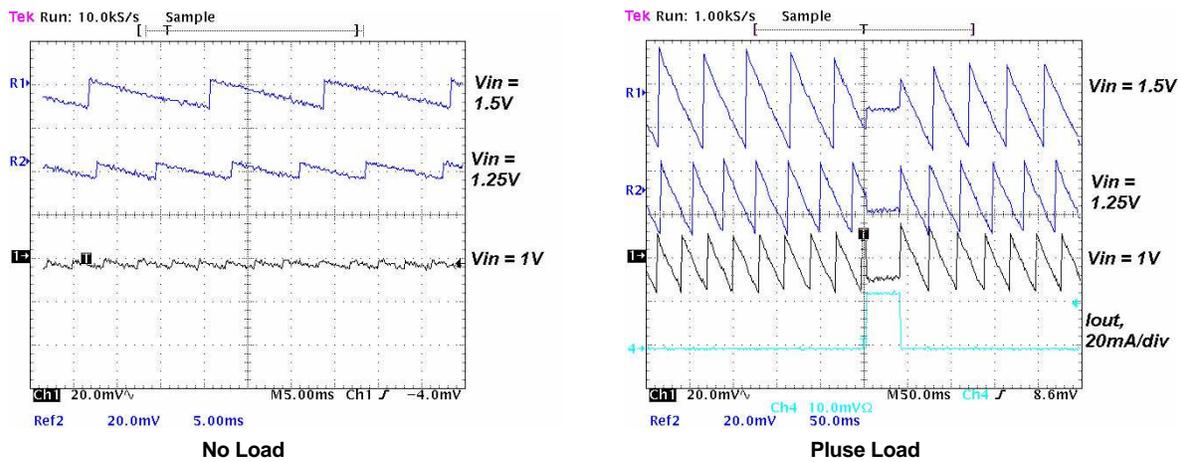


Figure 7. Output Ripple Voltage During PFM-Mode Operation With 10- μ H Inductance, 2 \times 4.7- μ F + Additional 22- μ F (C5) Output Capacitor

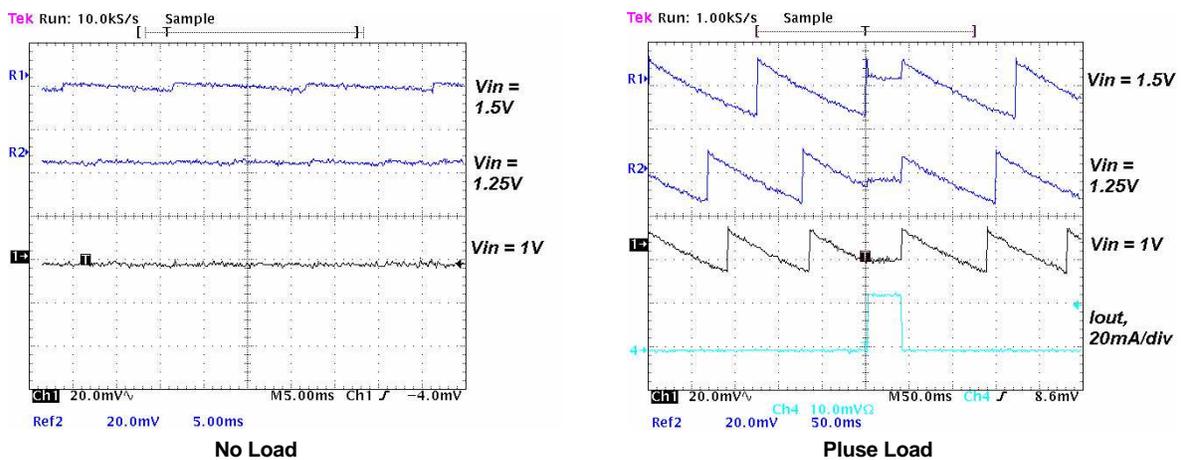


Figure 8. Output Ripple Voltage During PFM-Mode Operation With 10- μ H Inductance, 2 \times 4.7- μ F + Additional 120- μ F(C5) Output Capacitor

Experiment

Increasing the inductance to 22 μH did not improve the ripple voltage at pulse load operation. It actually caused increases of output ripple voltage, especially at lower input, as shown in [Figure 9](#) and [Figure 10](#).

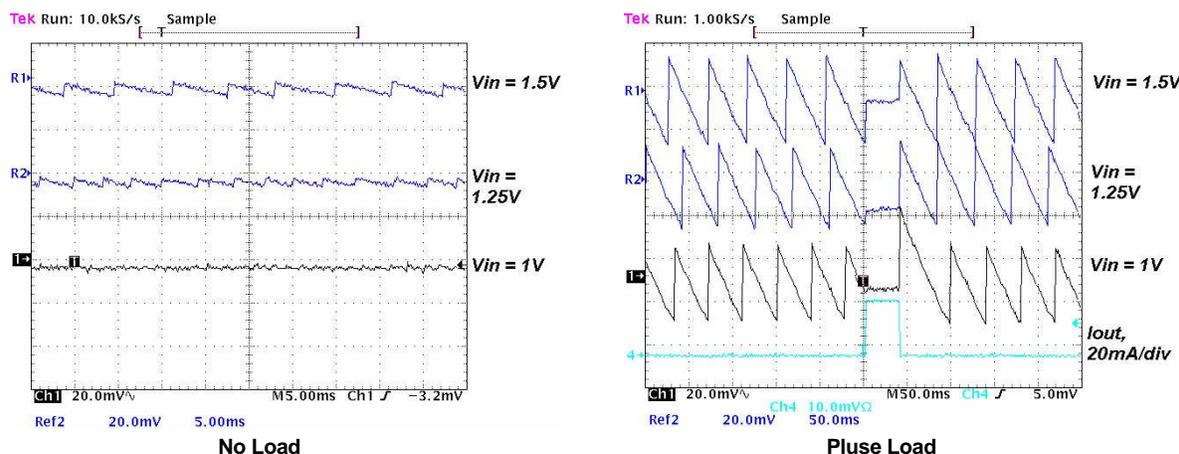


Figure 9. Output Ripple Voltage During PFM-Mode Operation With 22- μH Inductance, $2 \times 4.7\text{-}\mu\text{F} + 22\text{-}\mu\text{F}$ (C5) Output Capacitor

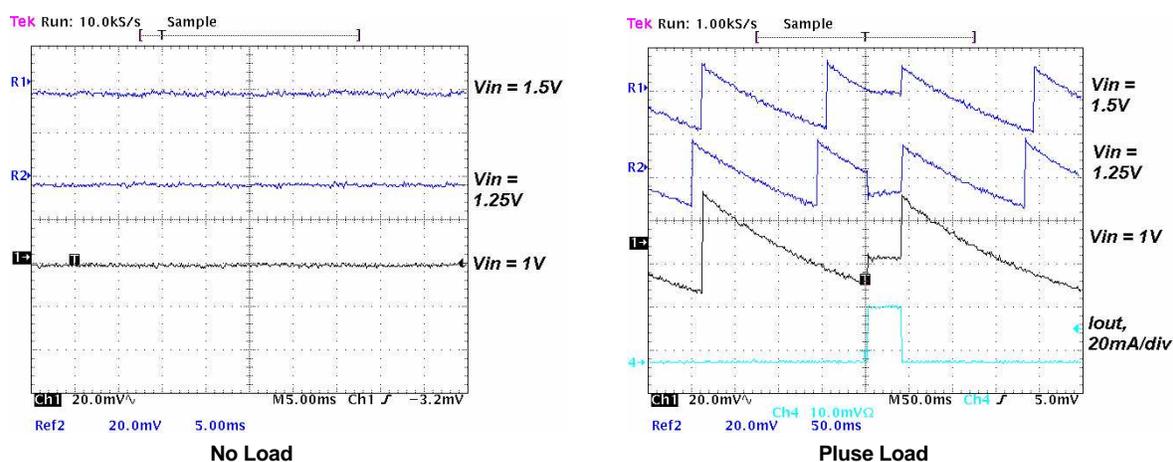


Figure 10. Output Ripple Voltage During PFM-Mode Operation With 22- μH Inductance, $2 \times 4.7\text{-}\mu\text{F} + 120\text{-}\mu\text{F}$ (C5) Output Capacitor

The preceding test results show that simply increasing the inductance or output capacitance could not improve the output ripple voltage significantly during pulse load operation (unless one increased the output capacitance to the range of few thousand microfarads, which is impractical in this application).

At light- to no-load operation, when the inductor current reduces to zero, power safe-mode (PFM) operation occurs, and the output voltage is monitored and regulated by the comparator. The trip point of the comparator and the rate of voltage change at the FB pin determine the output PFM ripple voltage. Adding a feedforward capacitor (C_{ff}) at the feedback path allows more high-frequency content to be coupled into the FB pin and also increases the rate of voltage change. This should reduce the PFM ripple voltage.

With the addition of a 1-nF feedforward capacitor (C_{ff}), the output ripple voltage has improved significantly. [Figure 11](#) shows the screen captured with 4.7- μH inductance with different output capacitance. [Figure 12](#) and [Figure 13](#) show the output ripple voltage with 10-nF and 100-nF feedforward capacitors, respectively.

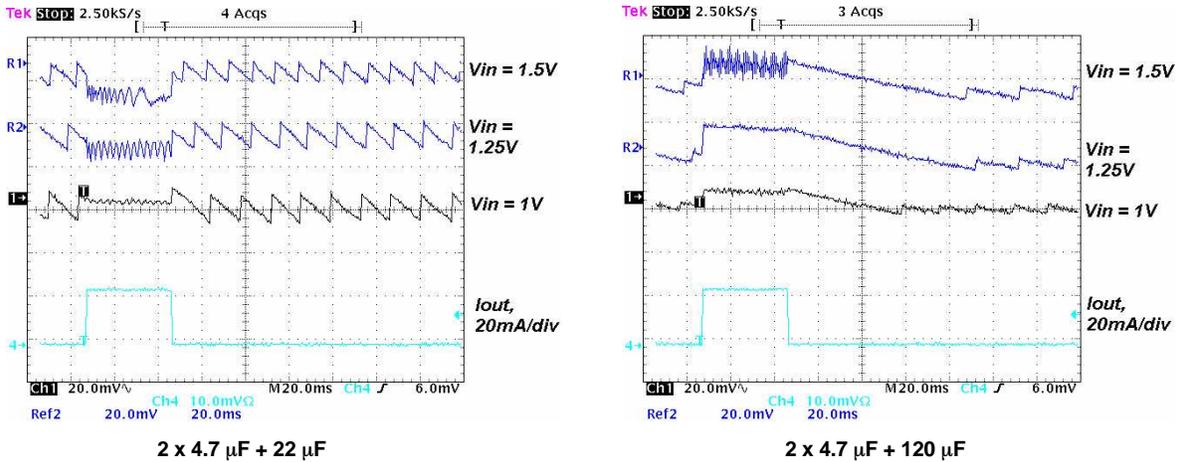


Figure 11. Output Ripple Voltage During PFM-Mode Operation With 1-nF Feedforward Capacitor (Cff), 4.7- μ H Inductor, and With Different Output Capacitors

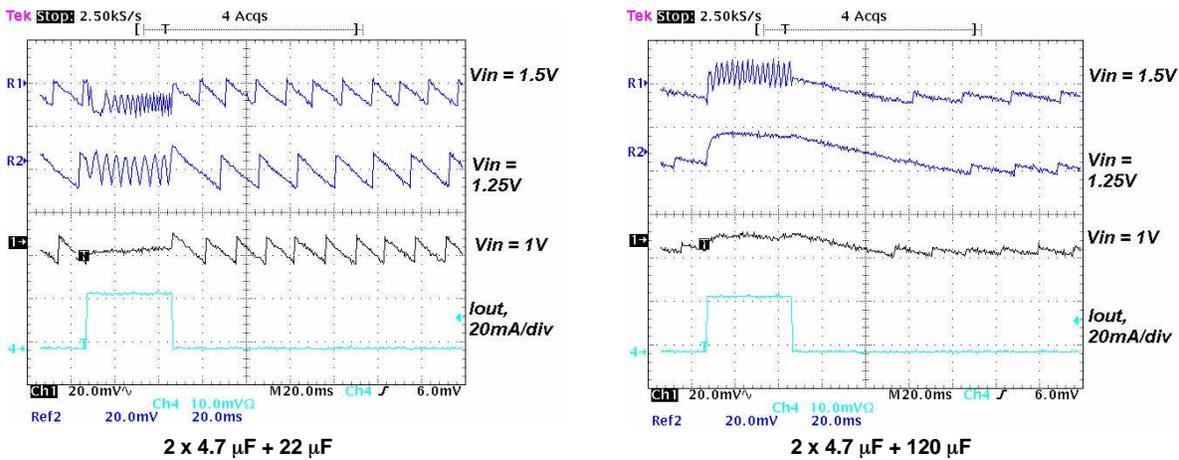


Figure 12. Output Ripple Voltage During PFM-Mode Operation With 10-nF Feedforward Capacitor (Cff), 4.7- μ H Inductor, and With Different Output Capacitors

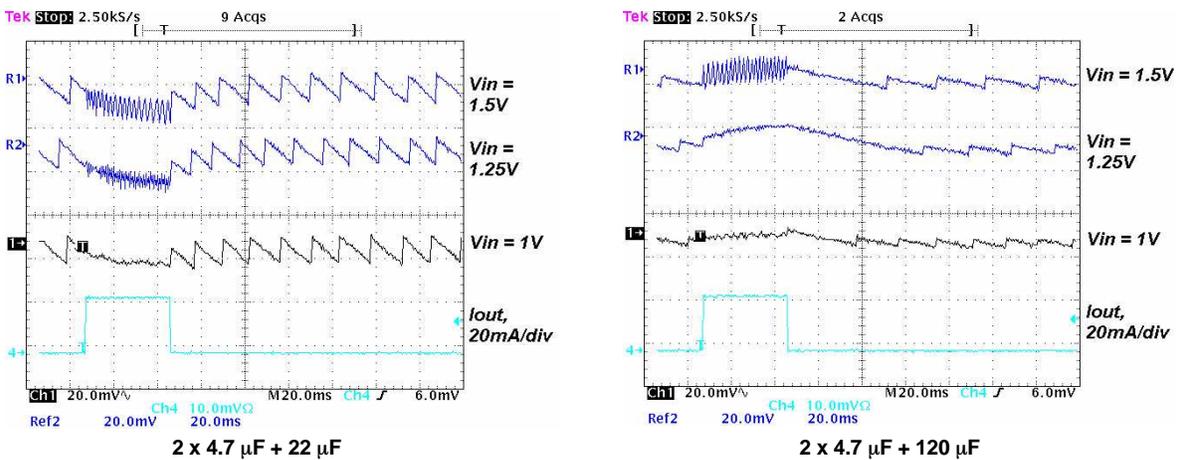


Figure 13. Output Ripple Voltage During PFM-Mode Operation With 100-nF Feedforward Capacitor (Cff), 4.7- μ H Inductor, and With Different Output Capacitors

Experiment

Increasing the inductance from 4.7 μH to 10 μH did not show much improvement on the ripple voltage. Figure 14 to Figure 16 show the screens captured with 1-nF, 10-nF, and 100-nF feedforward capacitors, respectively.

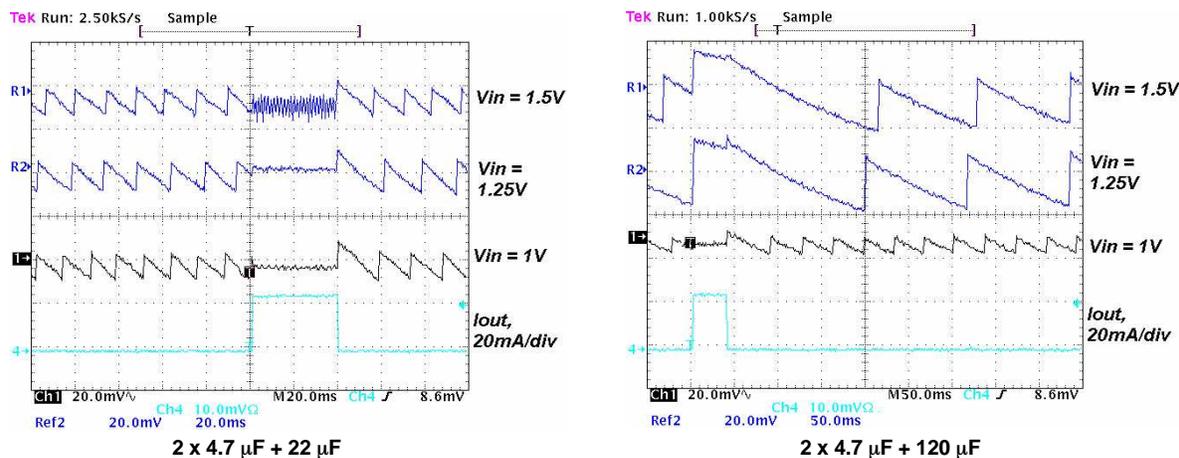


Figure 14. Output Ripple Voltage During PFM-Mode Operation With 1-nF Feedforward Capacitor (C_{ff}), 10- μH Inductor, and With Different Output Capacitors

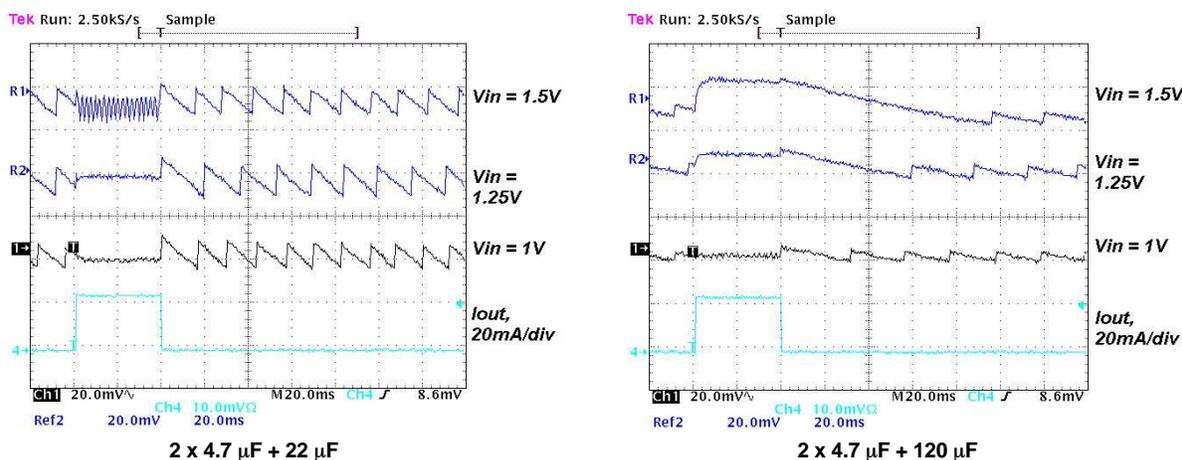


Figure 15. Output Ripple Voltage During PFM-Mode Operation With 10-nF Feedforward Capacitor (C_{ff}), 10- μH Inductor, and With Different Output Capacitors

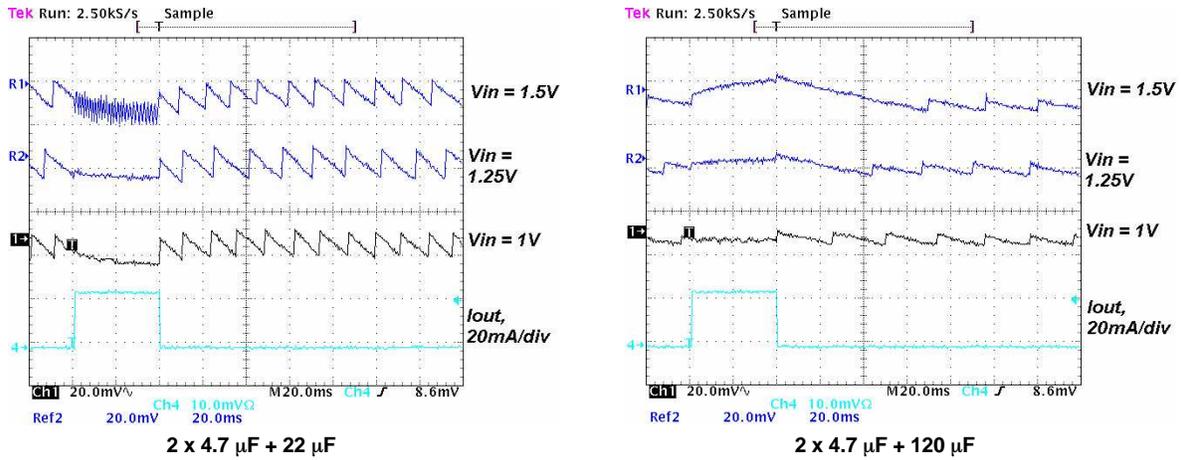


Figure 16. Output Ripple Voltage During PFM-Mode Operation With 100-nF Feedforward Capacitor (Cff), 10-µH Inductor, and With Different Output Capacitors

Increasing the inductance to 22 µH causes the ripple voltage during the transition from pulse load to no load to increase significantly. Figure 17 to Figure 19 show the screen captured with 1-nF, 10-nF, and 100-nF feedforward capacitors, respectively.

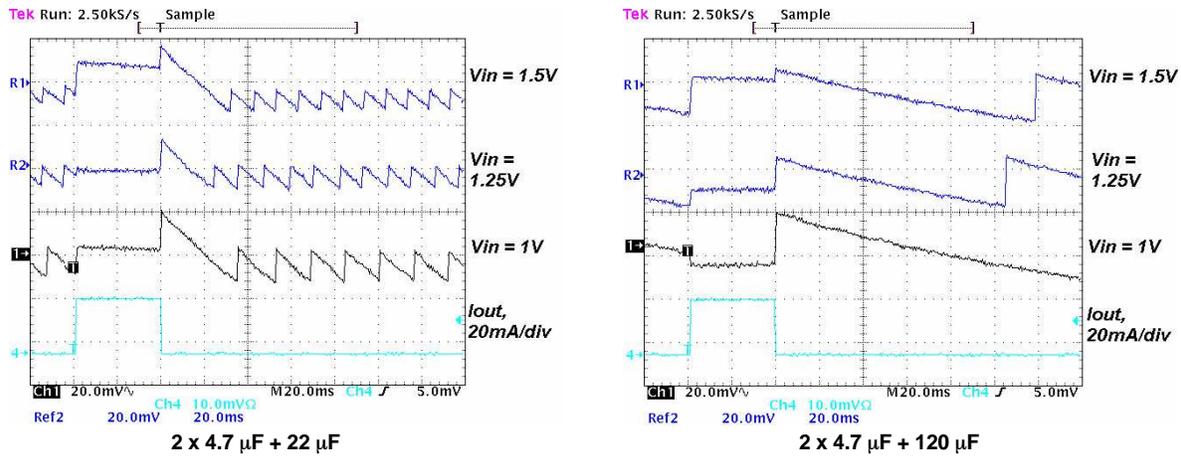


Figure 17. Output Ripple Voltage During PFM-Mode Operation With 1-nF Feedforward Capacitor (Cff), 22-µH Inductor, and With Different Output Capacitors

Summary

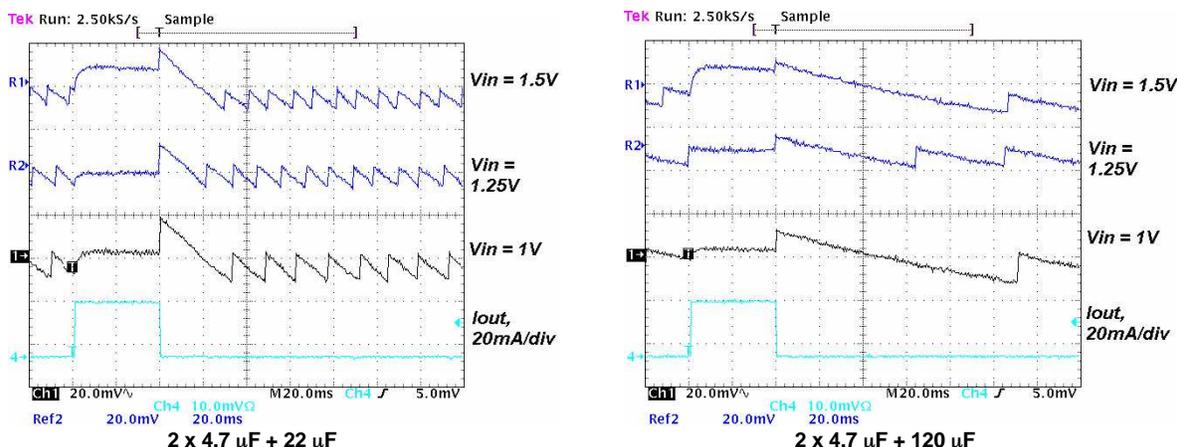


Figure 18. Output Ripple Voltage During PFM-Mode Operation With 10-nF Feedforward Capacitor (Cff), 22-μH Inductor, and With Different Output Capacitors

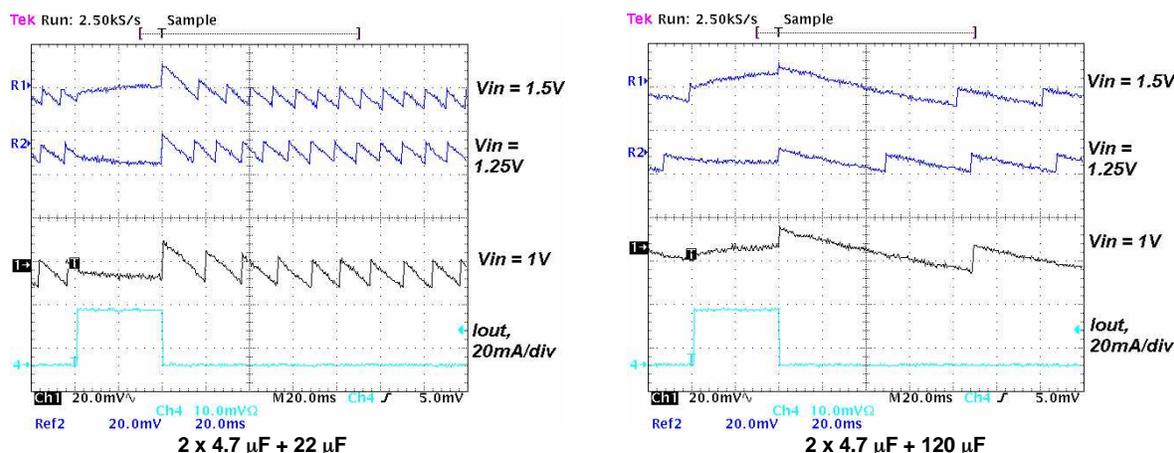


Figure 19. Output Ripple Voltage During PFM-Mode Operation With 100-nF Feedforward Capacitor (Cff), 22-μH Inductor, and With Different Output Capacitors

3 Summary

From the preceding test results, with a reasonable output capacitor value (greater than 22 μF) and inductance value of 4.7 μH to 10 μH, adding a feedforward capacitor from 1 nF to 100 nF could significantly reduce the output ripple voltage.

Figure 20 and Figure 21 show the screen capture of the ripple voltage and current waveform from the actual Bluetooth headset during sniff-mode operation. It confirms that this is a practical solution to reduce the output ripple voltage in the Bluetooth headset by adding the feedforward capacitor at the feedback loop.

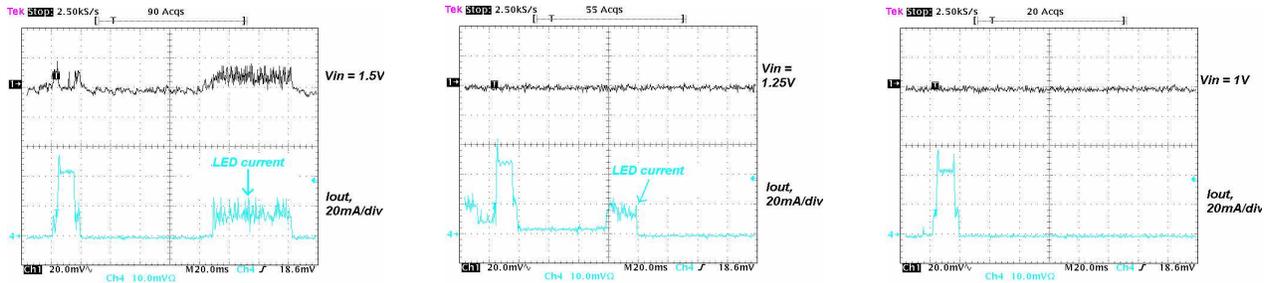


Figure 20. Output Ripple Voltage and Current Waveform From TPS61070 During Sniff-Mode Operation of Bluetooth Headset With 1-nF Feedforward Capacitor (C_{ff}) and With 2 × 22-μF Output Capacitors

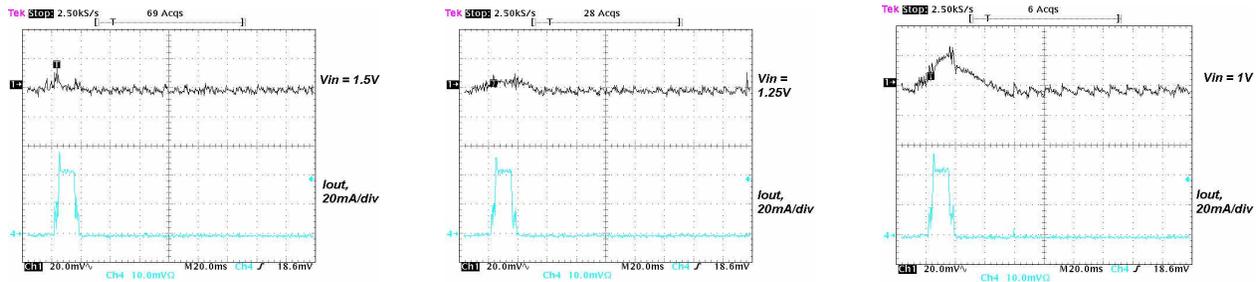


Figure 21. Output Ripple Voltage and Current Waveform From TPS61070 During Sniff-Mode Operation of Bluetooth Headset With 10-nF Feedforward Capacitor (C_{ff}) and With 2 × 22-μF Output Capacitors

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265