



Dan Harmon

In [previous installments of this series](#), I discussed implementation alternatives and how those decisions affect and are affected by device parameters. In this post, I'll explain how device parameters as well as system factors can affect the achievable accuracy.

To understand how accurate a measurement we can achieve, we first need to understand the sources of potential errors. Here is a list of two types of error sources – note that this is not an exhaustive list, but rather highlights some of the main sources:

Amplifier-related Error (Noise) Sources:

- Input offset voltage (V_{OS}).
- V_{OS} drift.
- Common-mode rejection ratio (CMRR).
- Power-supply rejection ratio (PSRR).
- Gain error.
- Gain-error drift.

Nonamplifier Error Sources:

- Printed circuit board (PCB) layout.
- Shunt-resistor tolerance and drift.
- Gain-setting passives tolerance, matching and drift.

The worst-case accuracy is a simple linear summation of all error sources, e , shown in [Equation 1](#):

$$\zeta_{worst-case} = \sum_1^n e_n \tag{1}$$

It is statistically improbable that all errors are maxed at the same time, so a more probable accuracy equation would be a root-sum-square of the error sources, shown in [Equation 2](#):

$$\zeta_{rss} = \sqrt{\sum_1^n e_n^2} \tag{2}$$

First, let's consider the external error sources. The V_{SENSE} that the amplifier sees is what is across the input pins, which will be different than what a designer may experience if measuring across the resistor. Ideally $V_{SHUNT} = V_{SENSE}$, but parasitics and trace etch will cause this not to be true. A Kelvin connection will minimize the PCB parasitic-error contribution.

When it comes to shunt-resistor tolerance and drift, there will be a trade-off between the cost you are willing to pay and the required performance for the application. The shunt-resistor temperature drift is one of the main error sources over temperature, unless you choose a costly resistor. High-precision (0.1%), low-drift (50ppm/°C) resistors on catalog distribution sites cost somewhere between US\$4.00 and US\$8.00 in 1,000-unit quantities.

The error contribution of an operational amplifier's external circuitry is eliminated using a current-shunt monitor due to its integrated, matched, low-drift gain-resistor networks. The effects of these on-chip networks are factored into the error contributions of the current-sense amplifier itself.

When it comes to amplifier error sources, you will need to make similar trade-offs on precision versus cost. It is important to review the operating conditions of each of the parametric specifications listed in the datasheet and compare those to your actual operating conditions. For this discussion, I will focus on two of the main error contributors: input offset voltage and gain error.

The input offset voltage will be the dominant error source at low V_{SENSE} levels. If you simplify and assume that $V_{SENSE} = V_{SHUNT} = I_{LOAD} \times R_{SHUNT}$ (no parasitic error contribution), then the error contribution of V_{OS} is calculable using Equation 3:

$$e_{V_{OS}} = \frac{V_{OS(MAX)}}{I_{LOAD} \times R_{SHUNT}} \quad (3)$$

Let's look at two different current-shunt monitors, the [INA199](#) and [INA210](#), to see how V_{OS} will affect the error. The [INA199](#) datasheet lists the $V_{OS(MAX)}$ as $150\mu V$, while the [INA210](#) is $35\mu V$. [Table 1](#) shows the respective error contributions using a current value of $1mA$ and a 1Ω shunt resistor.

Table 1. INA199 And INA210 Current-shunt Monitor Error Contributions

	INA199	INA210
$V_{OS(MAX)}$	$150\mu V$	$35\mu V$
V_{OS} error	15.0%	3.5%

If you are measuring low current values that will result in low V_{SENSE} values, it is critical to minimize V_{OS} to minimize the error. As V_{SENSE} grows relative to $V_{OS(MAX)}$, this error contribution is minimized. If V_{SENSE} is 1,000 times the value of V_{OS} , then the error contribution is 0.1%. On the other end of the spectrum is when V_{SENSE} is much greater than V_O . The main error contribution will be the gain error. In most datasheets, this is specified as a flat percentage, and the contribution is a straightforward percentage adder.

Let's see how these two errors contribute to a total error, again assuming that they are the only two error sources. [Figure 1](#) shows how the linear sum as well as the root-sum-square method of error calculation work for the [INA199](#) and [INA210](#).

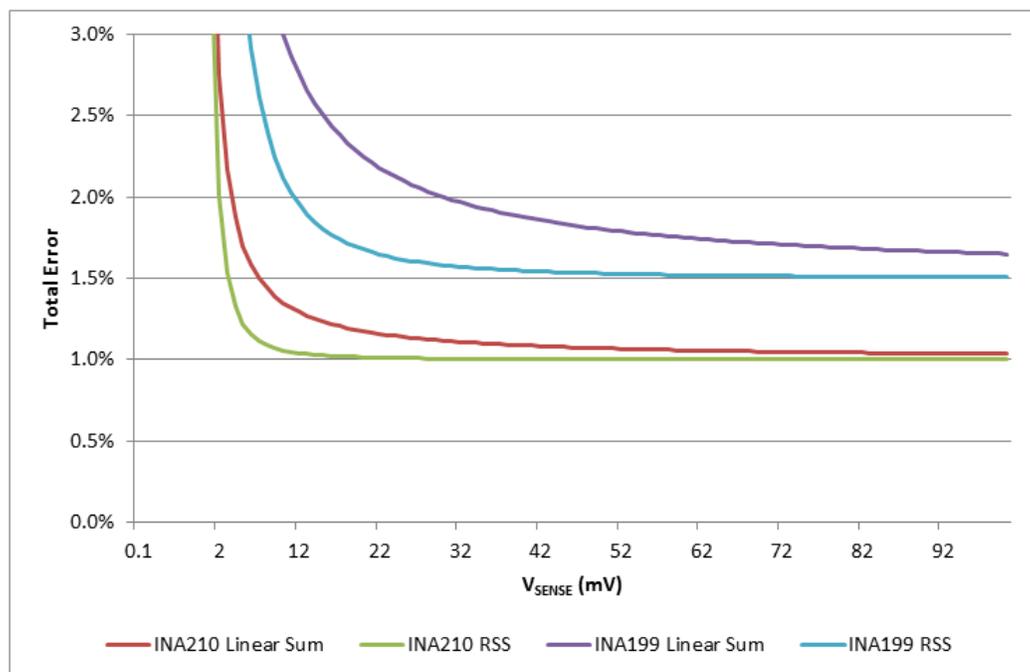


Figure 1. INA210 And INA199 Total Error

Here, the offset voltage is the major error source when V_{SENSE} is low, and gain error dominates when V_{SENSE} is high relative to V_{OS} .

My analysis has simplified the error calculations to two primary sources. However, current measurement accuracy is a very complex subject with many moving parts that need to be traded off against each other to maximize performance under specific operating conditions. One of the key elements for a more thorough analysis is temperature. The temperature drift will affect multiple specifications, including shunt-resistor value, offset voltage and gain error. Using a current-shunt monitor that has zero drift, including the [INA210](#) or [INA282](#), will help minimize the offset drift contribution.

Additional Resources

- Read the datasheets for the [INA210](#), [INA199](#) and [INA282](#) current-shunt monitors.
- Read this “Current sensing tutorial” [article series](#) on *EE Times*.
- Watch our [training series](#) on current-sense amplifiers.
- Check out related TI Designs reference designs:
 - [High-Voltage 12V-400V DC Current-Sense Reference Design](#).
 - [Current-Shunt Monitor with Transient Robustness Reference Design](#).
 - [EMC-Compliant High-Side Current-Sensing Reference Design with Overvoltage Protection](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated