

TIDA-00346 Design Considerations

Some implementations and use-cases of the TDA3x call for an inexpensive power supply without certain features that are required for other systems. This power supply design provides appropriate rails and proper sequencing for a medium use case for the TDA3x processor. In addition, this reference design contains a supply for DDR memory, a supply for a CAN transceiver and a simple switched load that can be used for testing the onboard supplies.

Each of the power supplies for the TDA3x must be sequenced during power up and power down. For this reason, any DC/DC converter that we choose must have an enable input or a switched output. All supplies must be automotive qualified and all switching frequencies should be outside of the AM band.

For the off-battery supply, a TPS54240-Q1 was chosen. This will accommodate a battery input of up to 42V. Substituting a footprint compatible TPS54260-Q1 will increase the maximum input voltage to 60V. A 340 kohm resistor sets the switching frequency at 360 kHz. Feedback resistors of 31.6k and 10.0k set the output voltage to 3.3V. This 3.3V rail will be the input to all other converters. To be able to sequence the 3.3V, it is passed through one channel of a TPS22968-Q1 analog switch.

A TPS54122-Q1 dual output supply is used for the 1.8V and 1.06V rails. The buck is used for the high current 1.06V core rail while the LDO provides the low current 1.8V rail. The 1.8V digital is utilized directly, while the 1.8V analog supply passes through the second channel of the TPS22968-Q1 analog switch (for correct sequencing).

TPS62262-Q1 was chosen for its high efficiency and the 2.2MHz switching frequency that reduces radio noise and decreases the size of external components. This is a very simple implementation utilizing the recommended 2.2uH inductor and a fixed 1.2V output.

Sequencing for the different supplies described above is achieved with a logic circuit utilizing two LM3880-Q1 sequencers and a couple of logic gates.

Power Up Sequence: When the TPS3808-Q1 power rail supervisor senses that the battery input voltage (V_{in_P}) is above 4.8V, the nRST output transitions from a low to a high. This causes the output of the OR gate to transition to a high, enabling the first sequencer (U1). This sequencer turns on three supplies in order using FLAG1, FLAG2 and FLAG3. When the last of these, FLAG3 (EN_4) goes high, the output of the AND gate transitions to a high and enables the second sequencer (U3). This enables three more supply rails and power up is complete.

Power Down Sequence: When the TPS3808-Q1 power rail supervisor senses that the battery input (V_{in_P}) voltage falls below 4.8V, the nRST output transitions from a high to a low. This causes the output of the AND gate to transition to a low, disabling the second sequencer (U3). This sequencer turns off three supplies in the reverse order using FLAG1, FLAG2 and FLAG3. When the last of these, FLAG1 (EN_5) goes low, the output of the OR gate transitions to a low and disables the first sequencer (U1). This disables three more supply rails and power down is complete.

The power down sequence requires that even though Vin_P has dropped, Vin must be held up long enough for the sequence to complete. For some loads, this may require additional capacitance be added on the Vin rail. This can be done using TP91. An alternate power down method would be to assert the master reset on the TPS3808-Q1. If a power down signal is available in the system, this would be a preferred method to initiate shutdown. The sequence would be the same, but it would not require additional capacitance. If the master reset is used, the power good threshold for the supervisor can be decreased to allow the entire system to operate down to a 4V battery input.

This concludes the design considerations for the TDA3 power supply. What follows is a description of the additional (optional) circuitry that has been included in this reference design.

For many automotive systems, a CAN transceiver is required. For this, a 5V rail has been provided. This supply is built with a TPS61071-q1 boost converter. The 5V rail is boosted off of the 3.3V rail so that the battery input can be allowed to fall below 5V.

For a design requiring DDR memory, a complete power supply and termination regulator is included. By changing the feedback resistors on the TPS79901-Q1 LDO, a VDDQ output voltage of 1.1V to 3.5V can be achieved. By configuring the input jumper for the TPS51200-Q1 termination regulator input, a VTT is made available that will accommodate multiple memories types: DDR, DDR2, DDR3, DDR3L, DDR4, LPDDR2 and LPDDR3.

To make this design easier to test, a “programmable” switched load is incorporated on the board. This circuit utilizes a TLS555-Q1 timer and a UCC27324 low-side MOSFET driver to create a repeating load pulse. The frequency of the load pulse is set to 30-40 Hz with a duty cycle of about 5%. R903, R904 and R905 are the load resistors for the 3.3V, 1.06V and 1.2V rails. Using the load resistor values shown in the schematic will result in load current pulses of 1A, 1.5A, and 120mA, respectively. Only one of these load resistors should be populated at any one time. The slope of the turn on and turn off edges of the control pulse can individually be controlled by adjusting the value of R906 and R907.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.