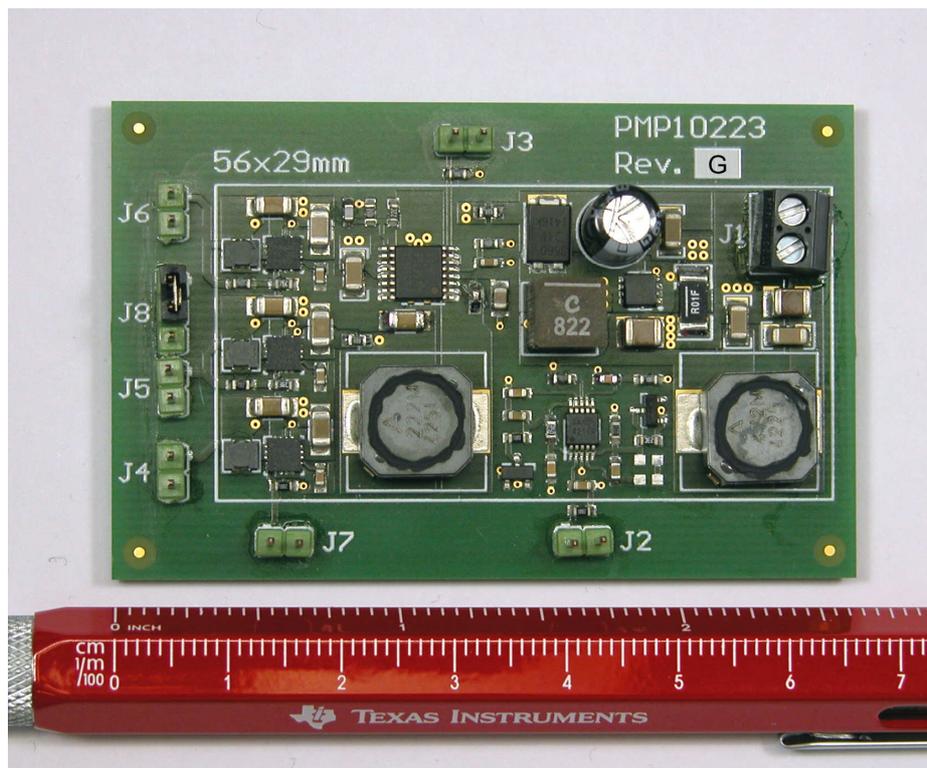


Automotive Power Supply with Pre-Boost

- Input 2.7-16V, 32V peak
- Output

Boost	9.0V @ 1.7A	TPS40210-Q1
Pre-Buck	6.0V @ 2.2A	LM53603-Q1
5V-Buck	5.0V @ 1.1A	TPS62133-Q1
3.3V-Buck	3.3V @ 0.6A	TPS62130-Q1
1.32V-Buck	1.32V @ 1.0A	TPS62130-Q1
- The output capacitor of the boost converter (Rubycon 35ZL56MEFCTA6.3X11, 405mA rms) can handle the ripple current only for a short time (cranking e.g.). For continuous operation at full load, a low ESR / high ripple current capacitor is needed (for example Nichicon PCV1V820MCL7GS or Panasonic 35SVPF82M). For a Panasonic 35SVPF82M output capacitor, no modification of the compensation network is needed (was tested).



1 +9.0V Boost Converter

1.1 Switching Node (+9.0V Boost Converter)

The switching node is shown in Figure 1.

The input voltage is set to 7.0V with a 1.7A load on the 9.0V output.

Channel C2: **Switching node**, -0.7V min, 12.1V max
2V/div, 2 μ s/div

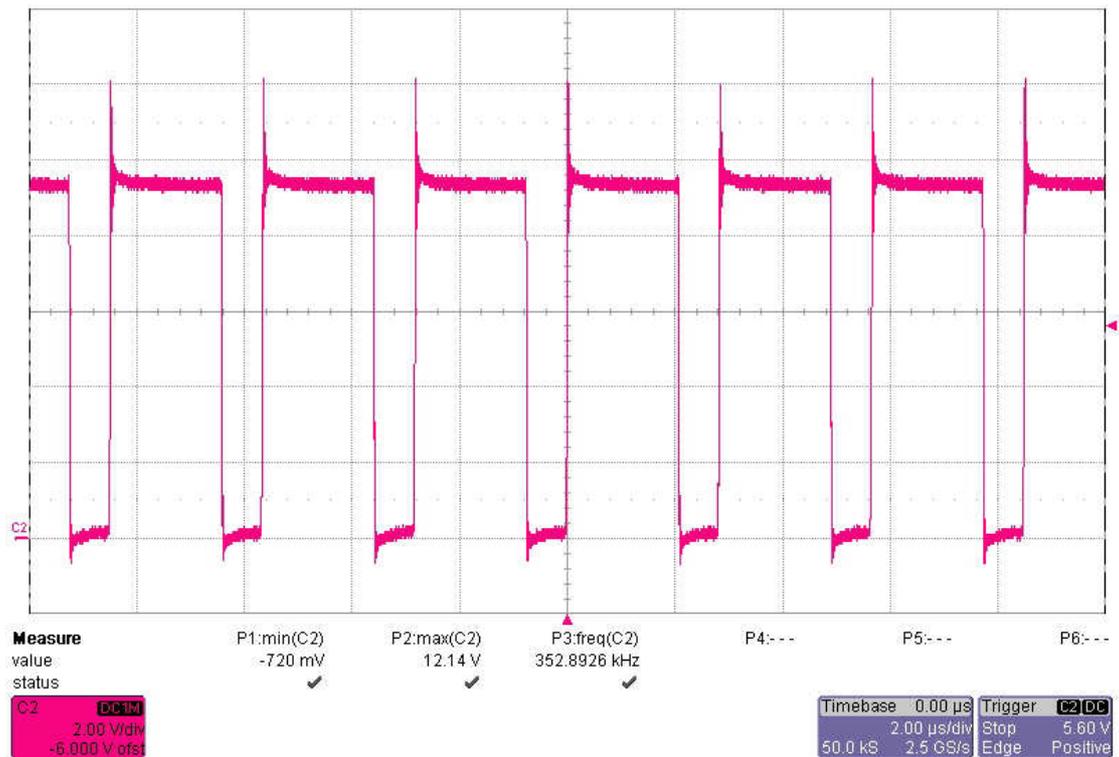


Figure 1

1.2 Transient Response (+9.0V Boost Converter)

The response to a load step is shown in Figure 2.

Channel C2: **Output voltage**, -988mV undershoot (11.0%), 1.25V overshoot (13.9%)
1V/div, 1ms/div, AC coupled

Channel C1: **Load current**, load step 0.85A to 1.7A and vice versa
1A/div, 1ms/div

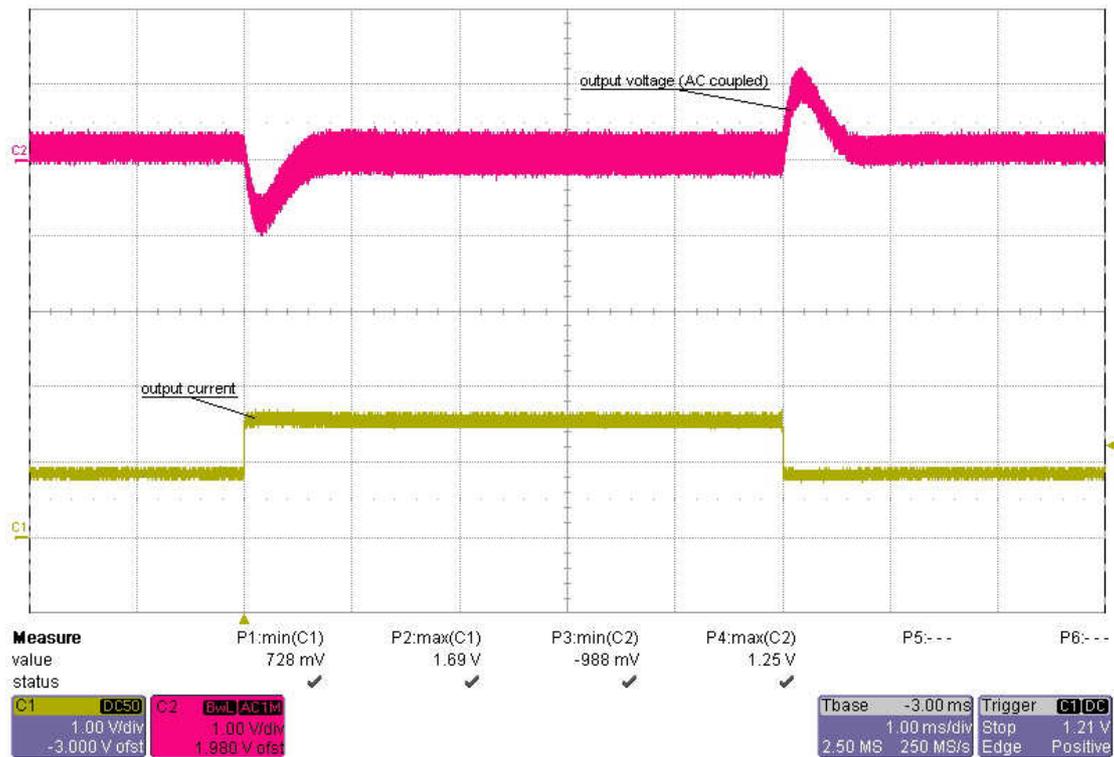


Figure 2

1.3 Frequency Response (+9.0V Boost Converter)

Figure 3 shows the loop response of the boost converter at a load of 1.7A.

2.7V input

- 62 deg phase margin @ crossover frequency of 325 Hz
- -13 db gain margin

5.0V input

- 76 deg phase margin @ crossover frequency of 517 Hz
- -22 db gain margin

7.0V input

- 78 deg phase margin @ crossover frequency of 632 Hz
- -26 dB gain margin

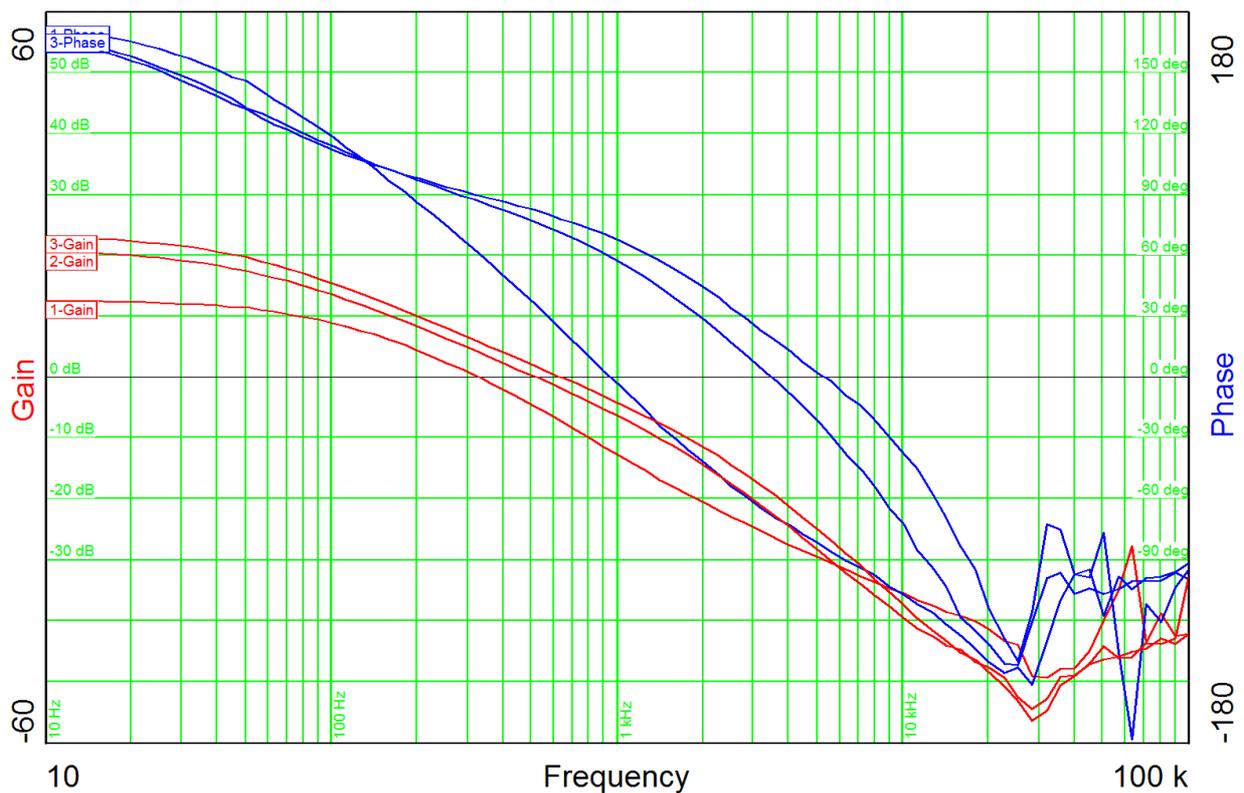


Figure 3

1.4 Efficiency (+9.0V Boost Converter)

The efficiency at 2.7V, 5.0V and 7.0V input voltage is shown in Figure 4.

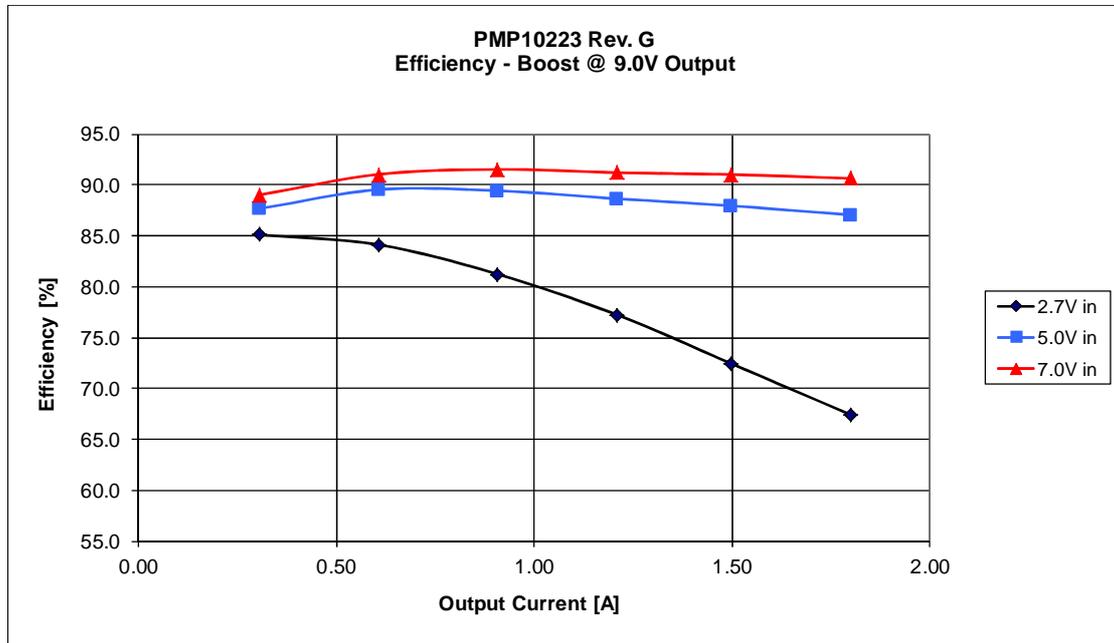


Figure 4

1.5 Load Regulation (+9.0V Boost Converter)

The load regulation of the boost converter is shown in Figure 5.

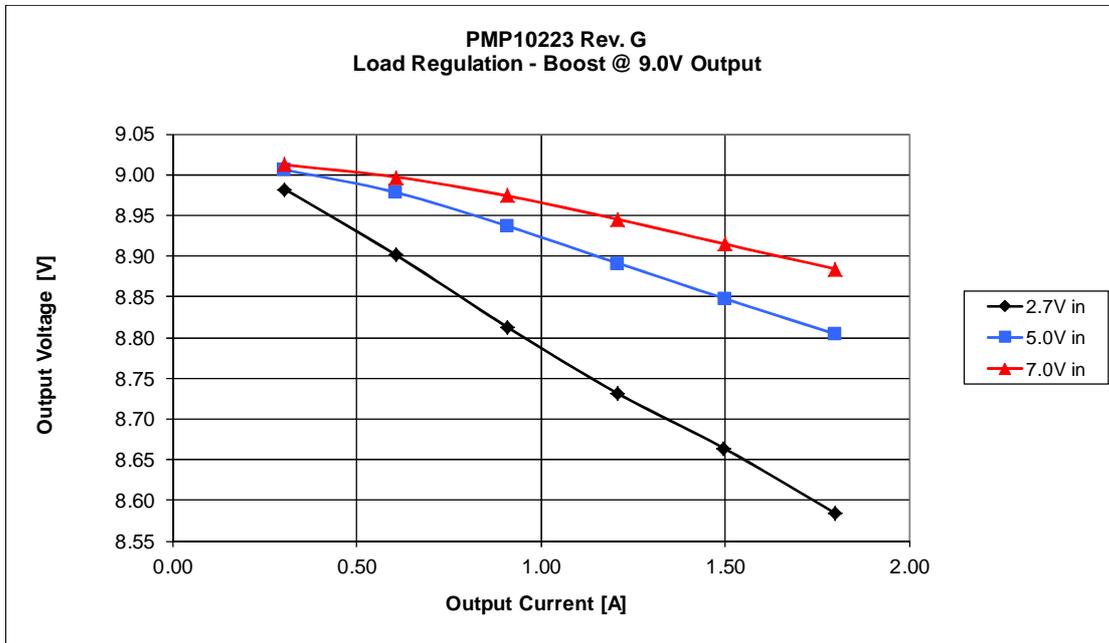


Figure 5

1.6 Output Voltage Ripple (+9.0V Boost Converter)

The output ripple of the 9.0V boost converter is shown in Figure 6.
The input voltage is set to 2.7V, 5.0V and 7.0V.

Channel M1: **2.7V input voltage**, 400mV peak-peak
300mV/div, 2us/div

Channel M2: **5.0V input voltage**, 270mV peak-peak
300mV/div, 2us/div

Channel M3: **7.0V input voltage**, 150mV peak-peak
300mV/div, 2us/div

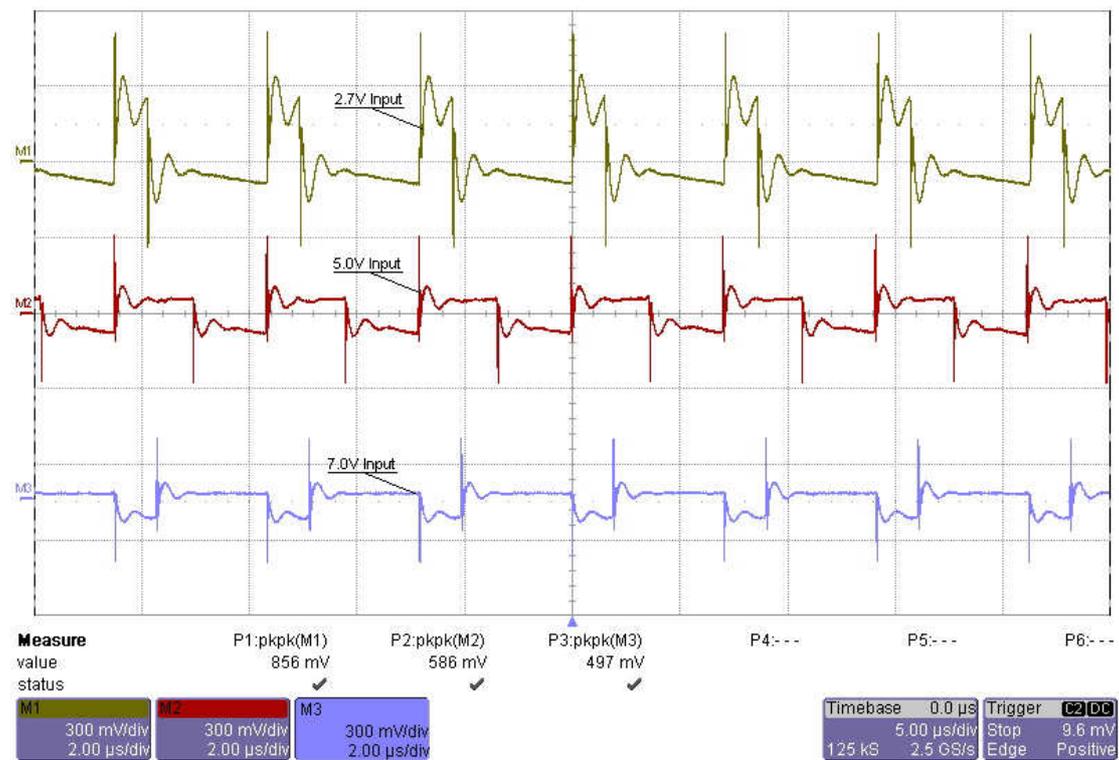


Figure 6

1.7 Input Voltage Ripple – Inductor Side (+9.0V Boost Converter)

The output ripple of the 9.0V boost converter is shown in Figure 7.
The input voltage is set to 2.7V, 5.0V and 7.0V.

Channel M1: **2.7V input voltage**, 125mV peak-peak
100mV/div, 5us/div

Channel M2: **5.0V input voltage**, 85mV peak-peak
100mV/div, 5us/div

Channel M3: **7.0V input voltage**, 77mV peak-peak
100mV/div, 5us/div

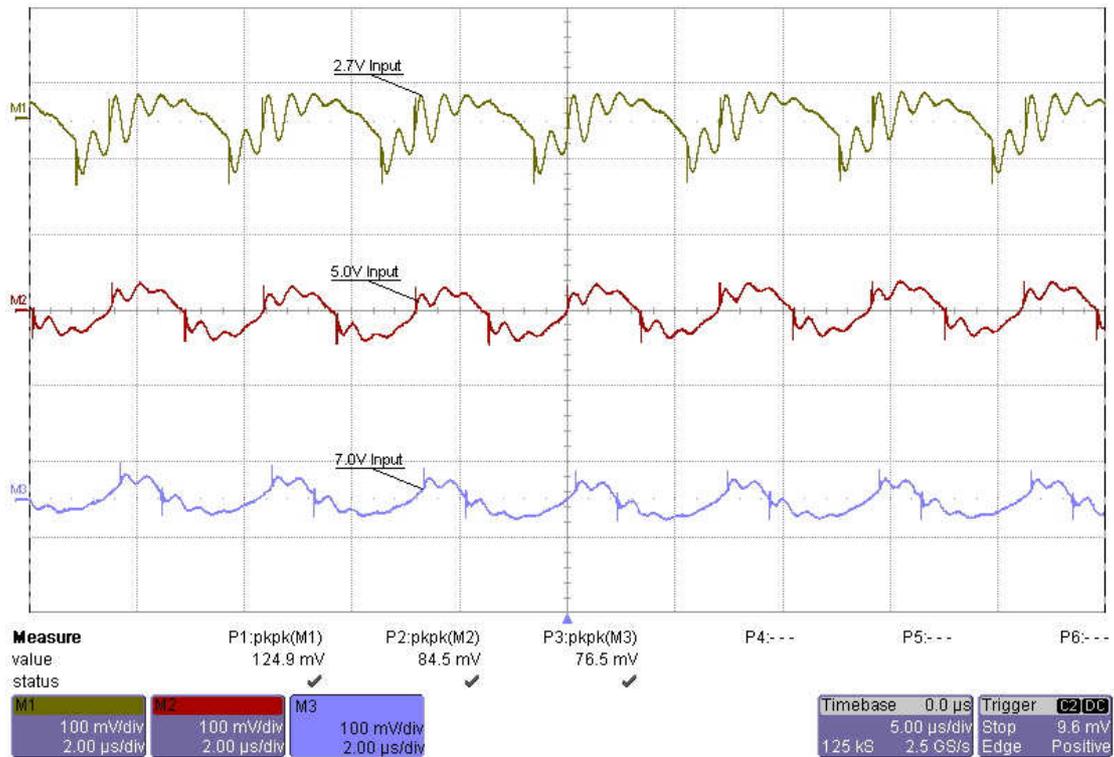


Figure 7

1.8 Input Voltage Ripple – Connector Side (+9.0V Boost Converter)

The output ripple of the 9.0V boost converter is shown in Figure 6.
The input voltage is set to 2.7V, 5.0V and 7.0V.

Channel M1: **2.7V input voltage**, 47mV peak-peak
20mV/div, 2us/div

Channel M2: **5.0V input voltage**, 20mV peak-peak
20mV/div, 2us/div

Channel M3: **7.0V input voltage**, 12mV peak-peak
20mV/div, 2us/div

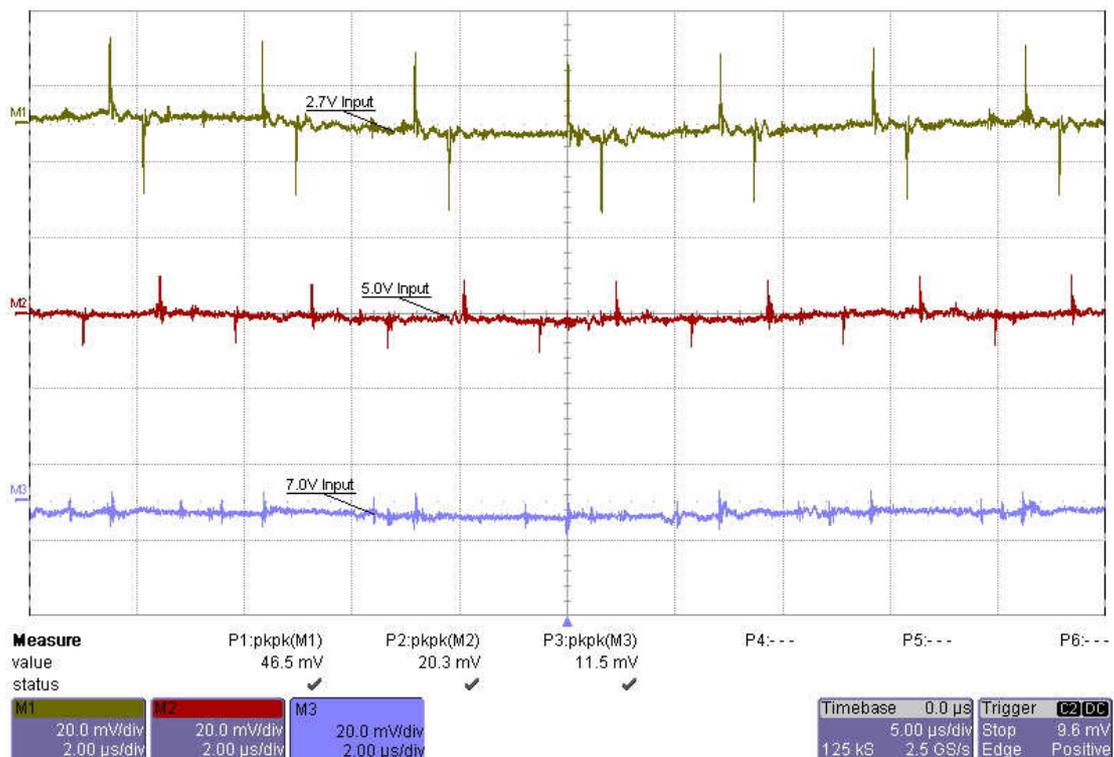


Figure 8

2 +6.0V Buck Converter

2.1 Switching Node (+6.0V Buck Converter)

The switching node is shown in Figure 9.

The input voltage is set to 12.0V with a 2.2A load on the 6.0V output.

Channel C2: **Switching node**, -1.0V min, 13.0V max
2V/div, 200ns/div

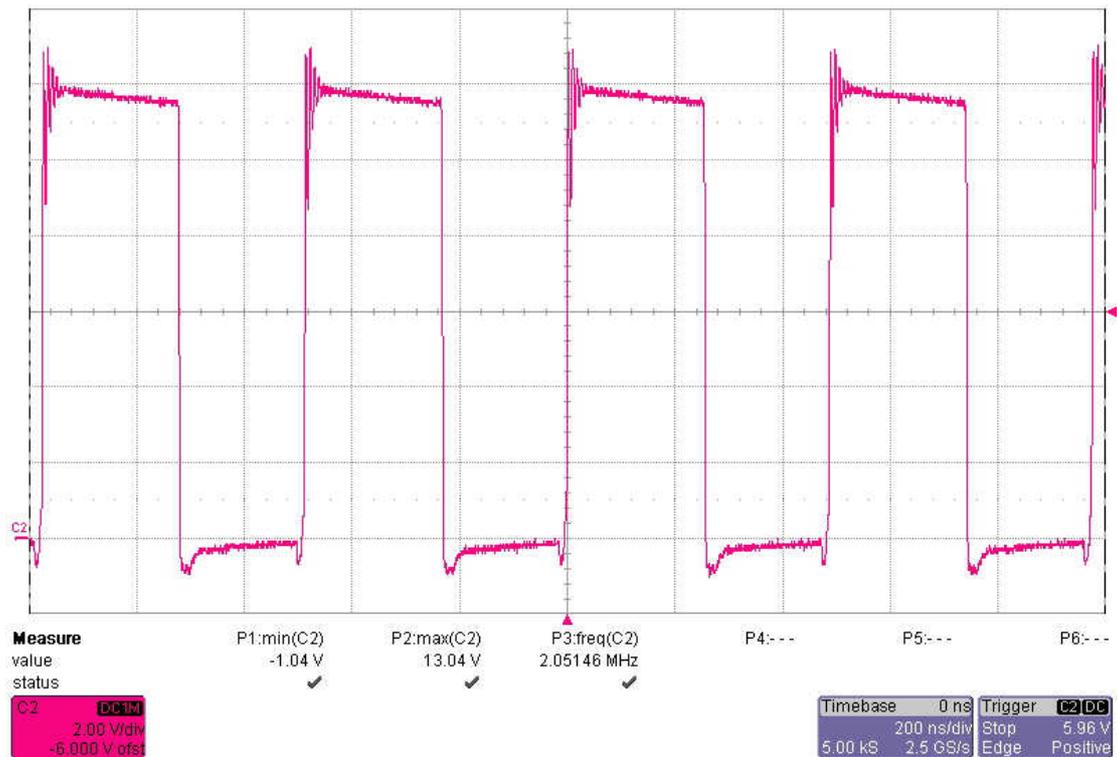


Figure 9

2.2 Transient Response (+6.0V Buck Converter)

The response to a load step is shown in Figure 10.

Channel C2: **Output voltage**, -48mV undershoot (0.8%), 45mV overshoot (0.8%)
 50mV/div, 1ms/div, AC coupled

Channel C1: **Load current**, load step 1.0A to 2.0A and vice versa
 1A/div, 1ms/div

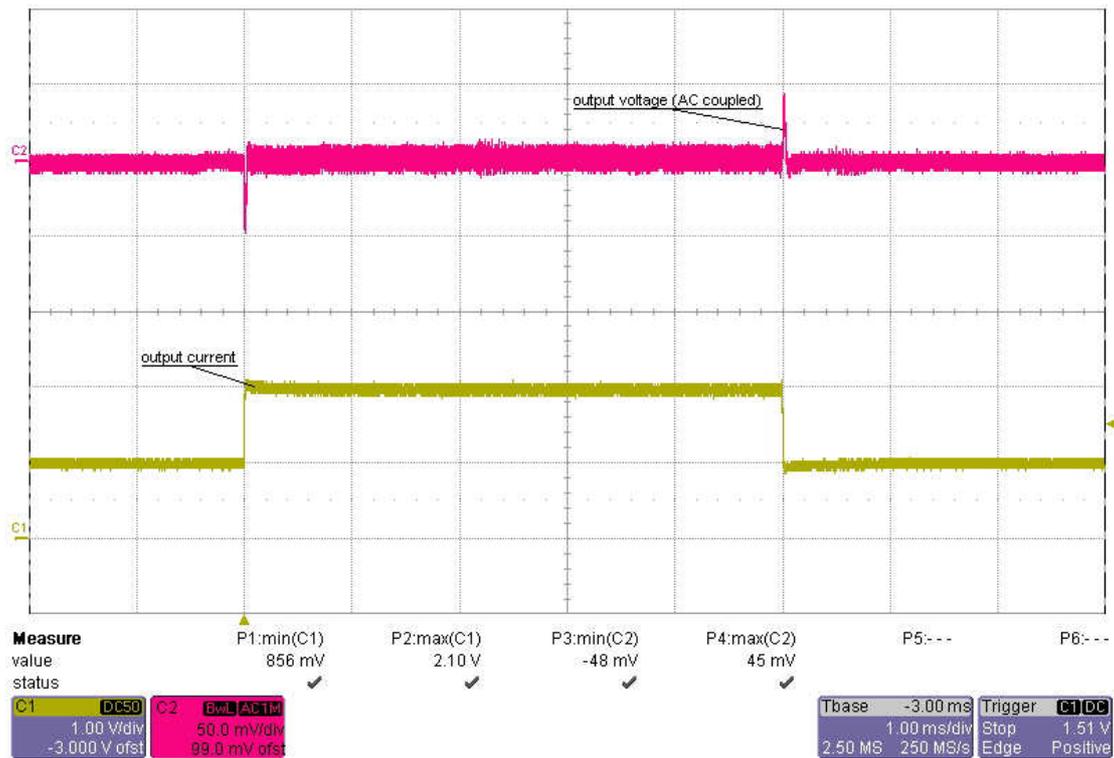


Figure 10

2.3 Frequency Response (+6.0V Buck Converter)

Figure 11 shows the loop response of the 6.3V buck converter at a load of 1.7A.

9.0V input

- 89 deg phase margin @ crossover frequency of 96.7 kHz
- -19 db gain margin

12.0V input

- 89 deg phase margin @ crossover frequency of 98.5 kHz
- -15 db gain margin

18.0V input

- 89 deg phase margin @ crossover frequency of 95.3 kHz
- -17 dB gain margin

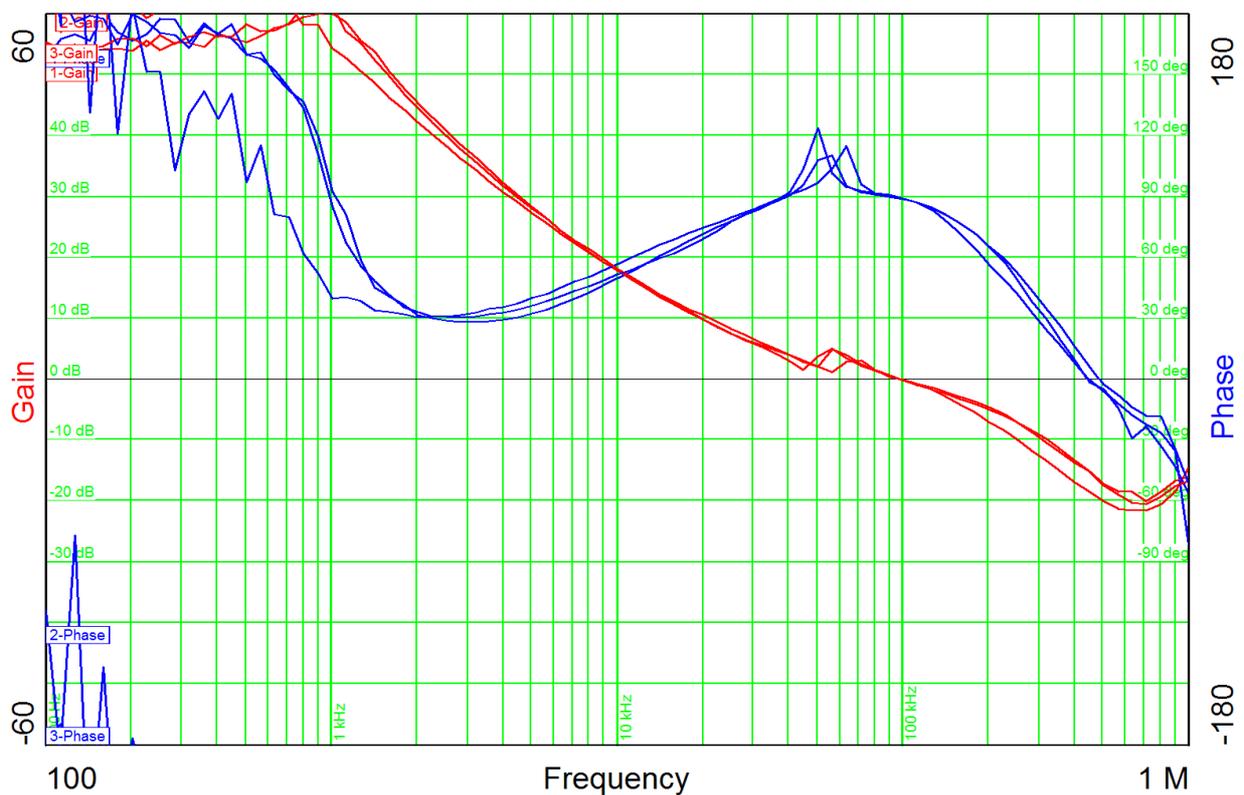


Figure 11

2.4 Efficiency (+6.0V Buck Converter)

The efficiency at 9.0V, 12V and 18.0V input voltage is shown in Figure 12.

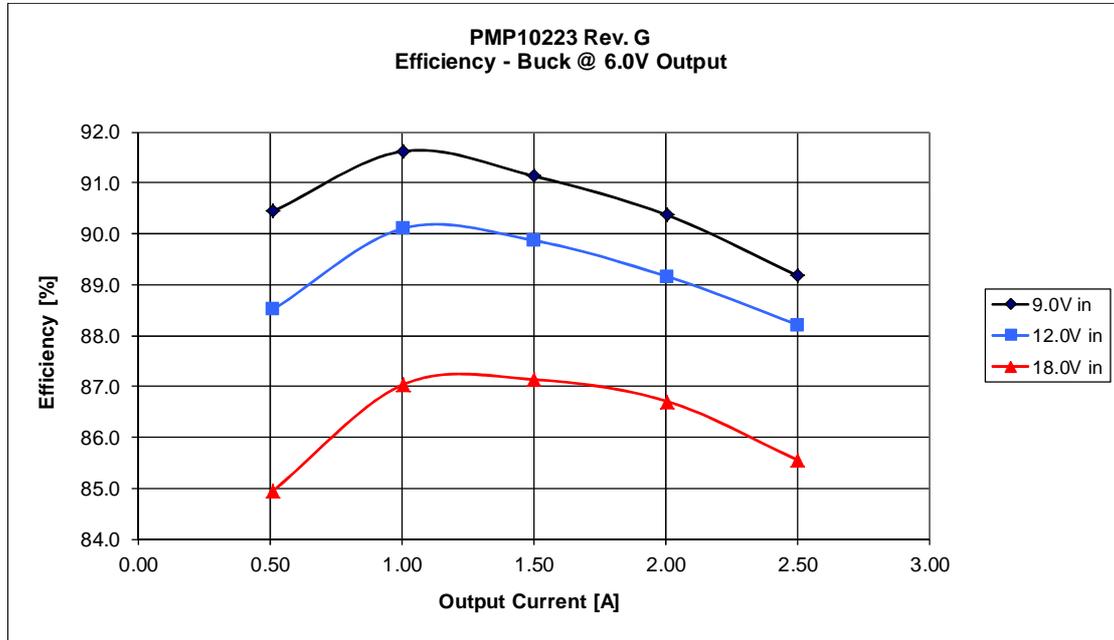


Figure 12

2.5 Load regulation (+6.0V Buck Converter)

The load regulation of the 6.0V buck converter is shown in Figure 13.

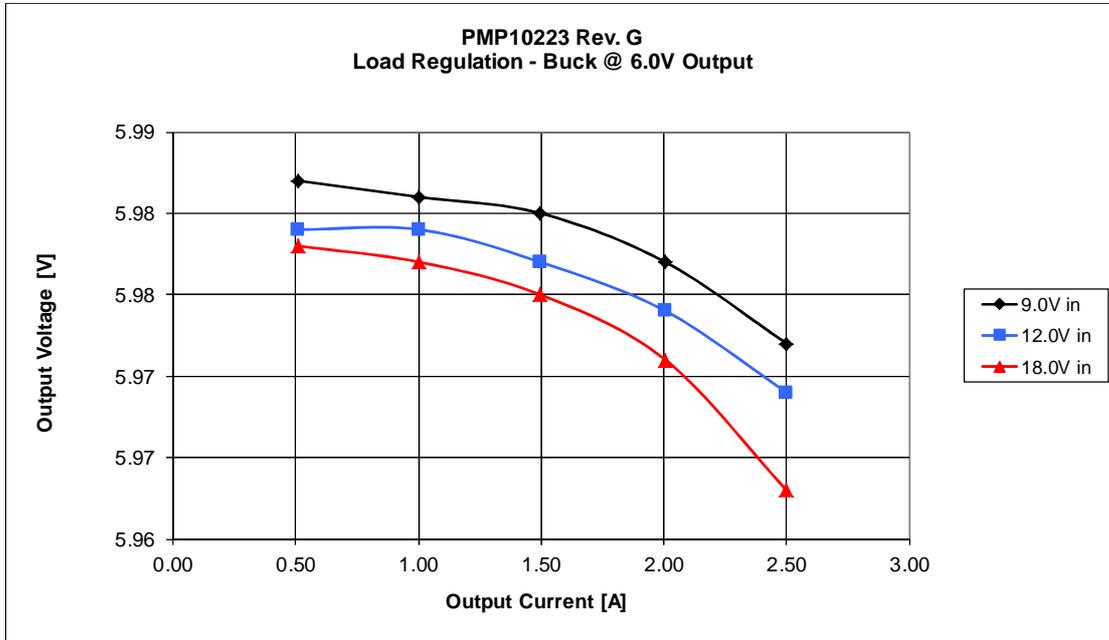


Figure 13

2.6 Output voltage ripple (+6.0V Buck Converter)

The output ripple of the 6.0V buck converter with 2.2A load is shown in Figure 14. The input voltage is set to 12.0V.

Channel C2: **12.0V input voltage**, 8mV peak-peak
20mV/div, 200ns/div

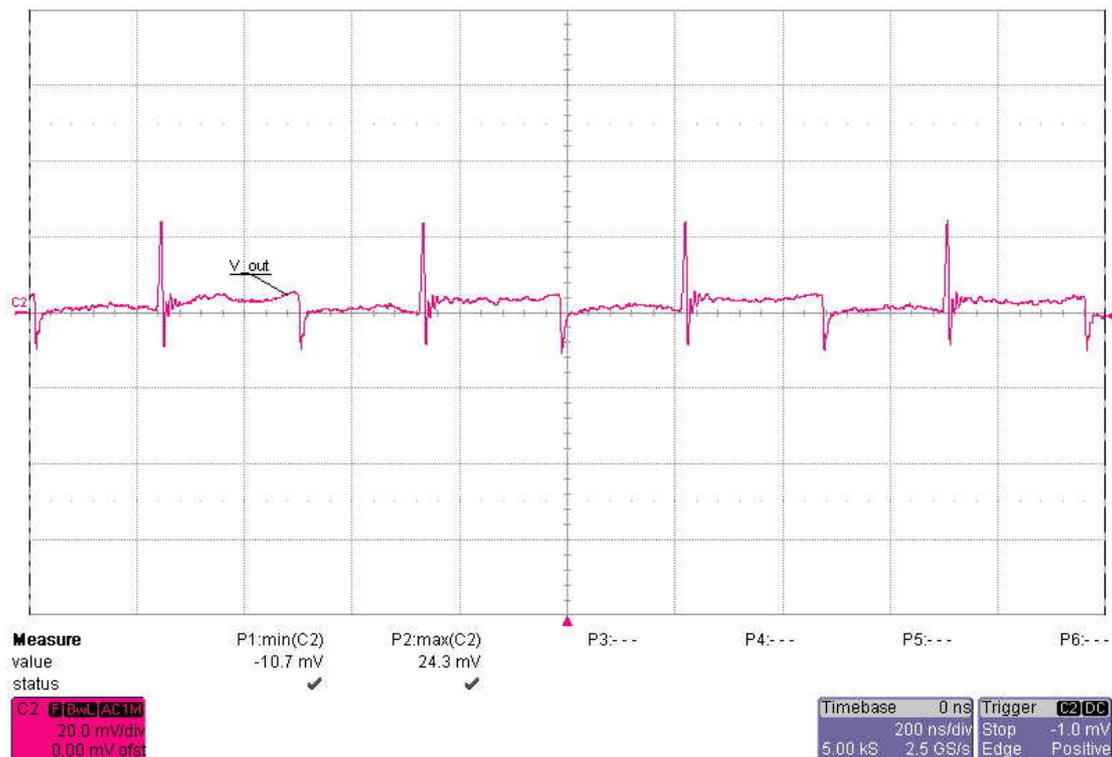


Figure 14

2.7 Startup (+6.0V Buck Converter)

The startup of the 6.0V buck with no load on the output is shown in Figure 15.

Channel C1: **12.0V Input voltage**
2V/div, 2ms/div

Channel C2: **6.0V Output voltage**
2V/div, 2ms/div

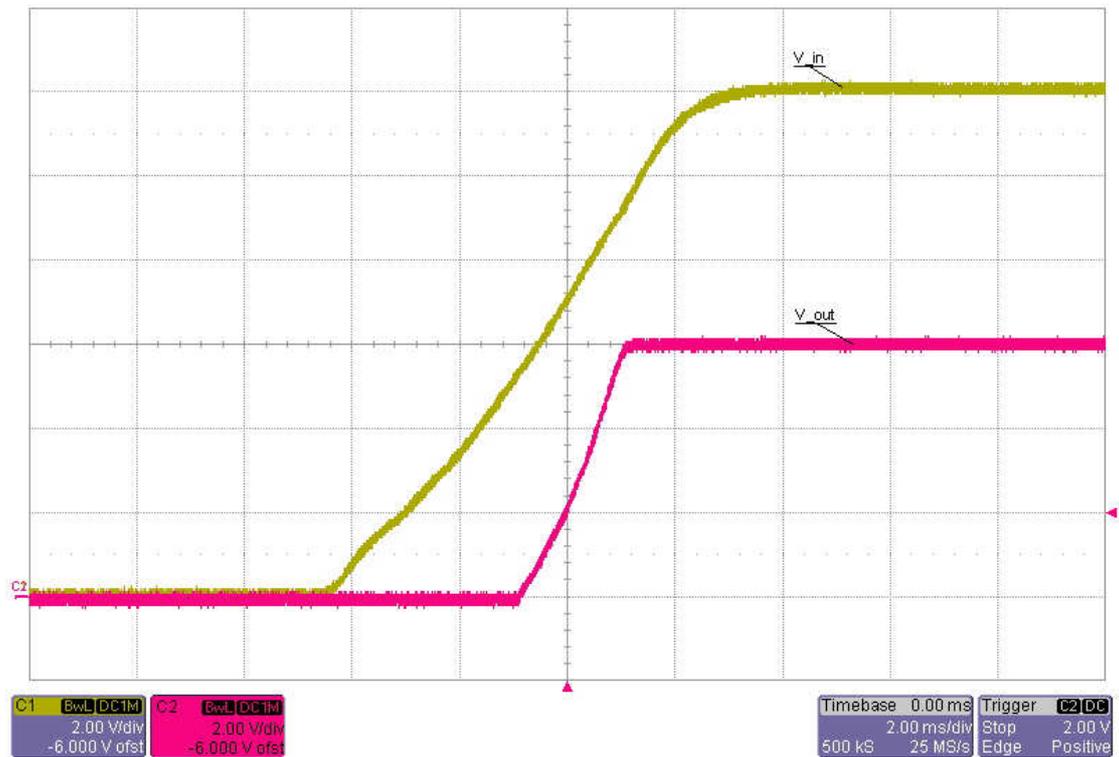


Figure 15

2.8 Shutdown (+6.0V Buck Converter)

The shutdown of the 6.0V buck with 2.2A load on the output is shown in Figure 16.

Channel C1: **12.0V Input voltage**
2V/div, 2ms/div

Channel C2: **6.0V Output voltage**
2V/div, 2ms/div

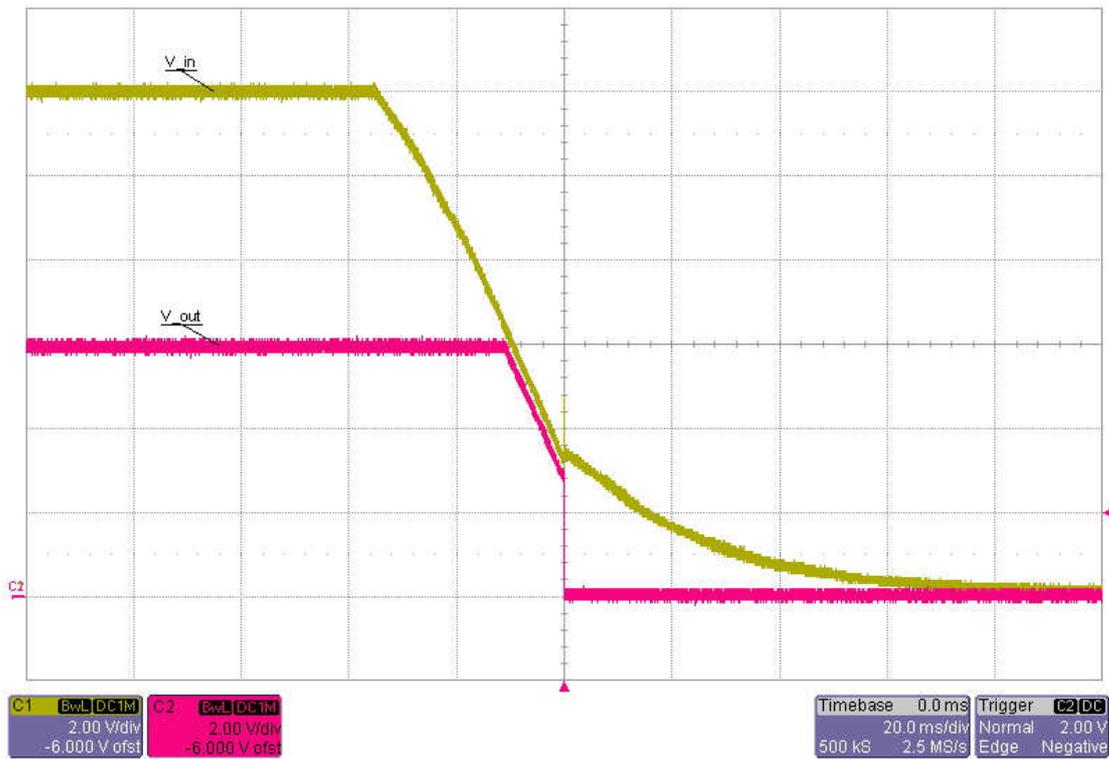


Figure 16

3 +5.0V Buck Converter

3.1 Switching Node (+5.0V Buck Converter)

The switching node is shown in Figure 17.

The input voltage is set to 6.0V with a 1.1A load on the 5.0V output.

Channel C2: **Switching node**, -0.8V min, 6.9V max
1V/div, 500ns/div

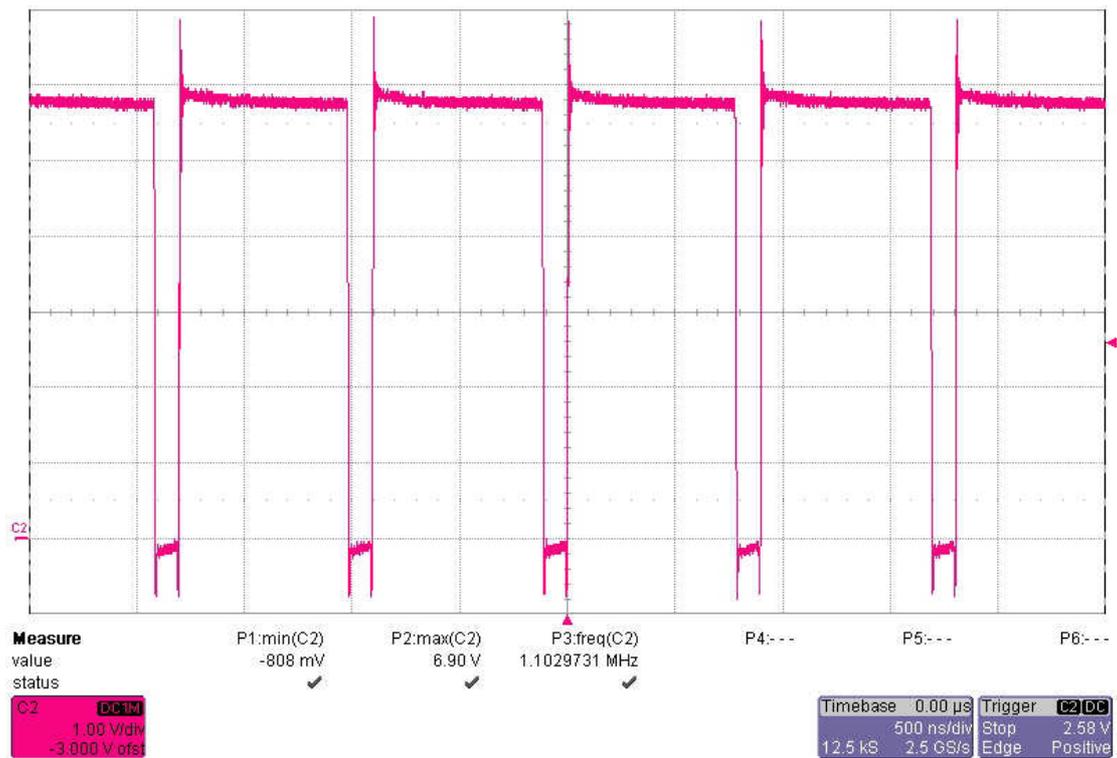


Figure 17

4 +3.3V Buck Converter

4.1 Switching Node (+3.3V Buck Converter)

The switching node is shown in Figure 18.

The input voltage is set to 6.0V with a 0.6A load on the 3.3V output.

Channel C2: **Switching node**, -0.8V min, 7.0V max
1V/div, 500ns/div

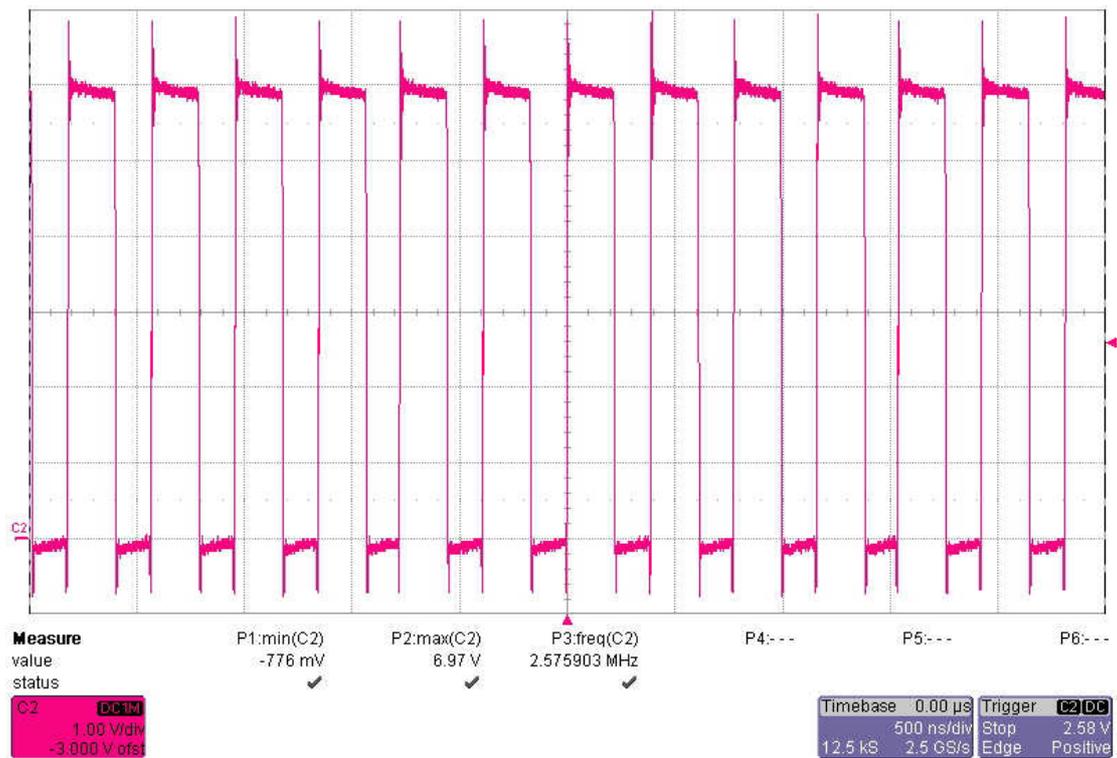


Figure 18

4.2 Frequency Response (3.3V Buck Converter)

Figure 19 shows the loop response of the 3.3V buck converter at a load of 0.6A.

6.0V input

- 79 deg phase margin @ crossover frequency of 22.0 kHz
- -22 dB gain margin

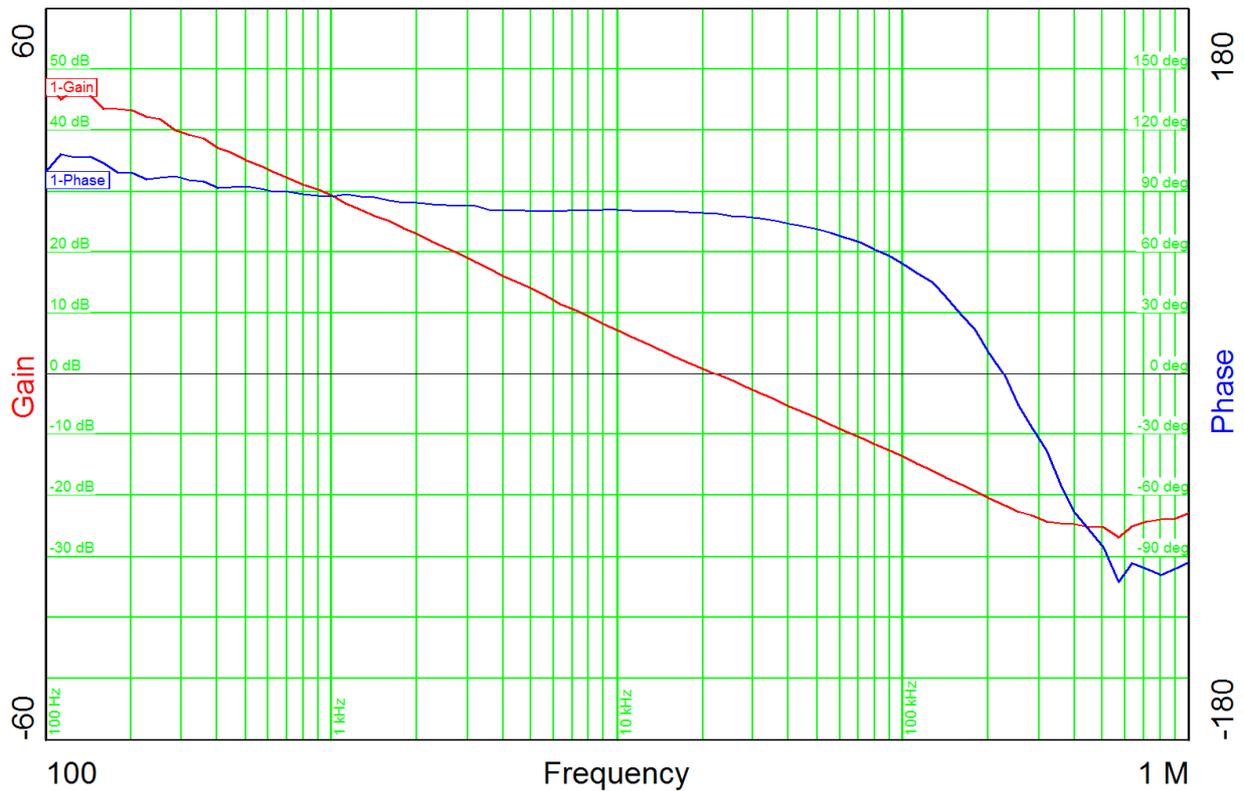


Figure 19

5 +1.32V Buck Converter

5.1 Switching Node (+1.32V Buck Converter)

The switching node is shown in Figure 20.

The input voltage is set to 6.0V with a 1.0A load on the 1.32V output.

Channel C2: **Switching node**, -0.8V min, 6.1V max
1V/div, 500ns/div

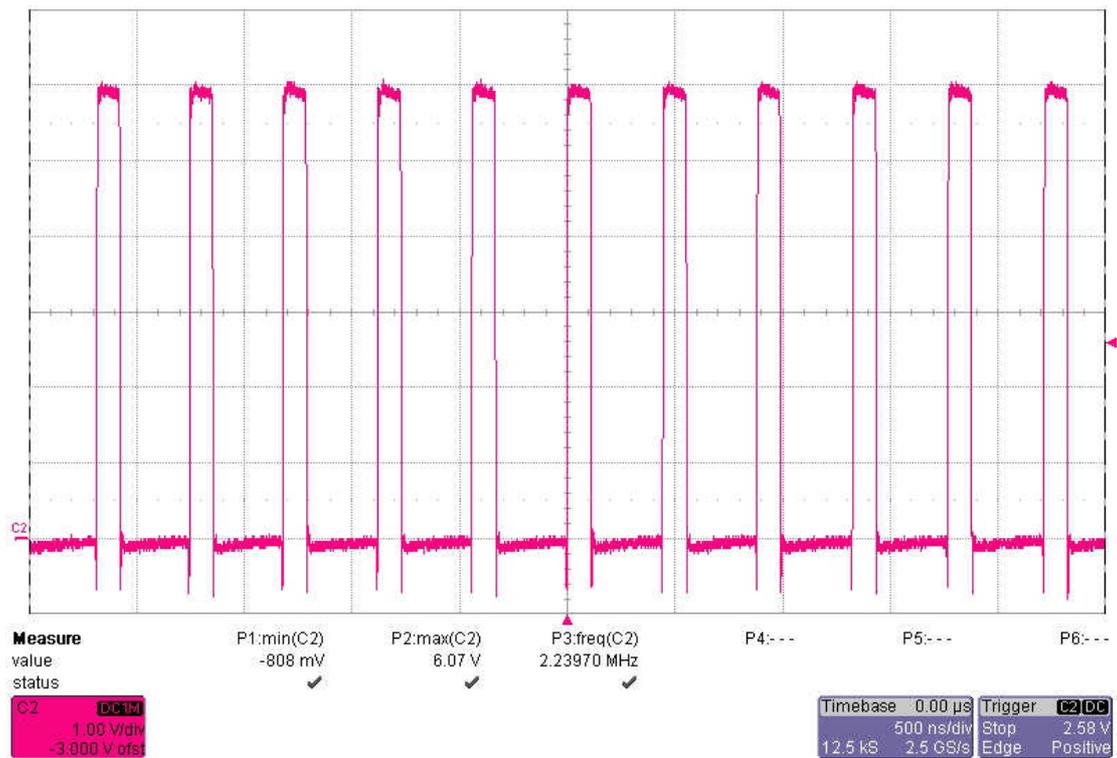


Figure 20

5.2 Frequency response (3.3V Buck Converter)

Figure 21 shows the loop response of the 1.32V buck converter at a load of 1.0A.

6.0V input

- 69 deg phase margin @ crossover frequency of 46.8 kHz
- -15 dB gain margin

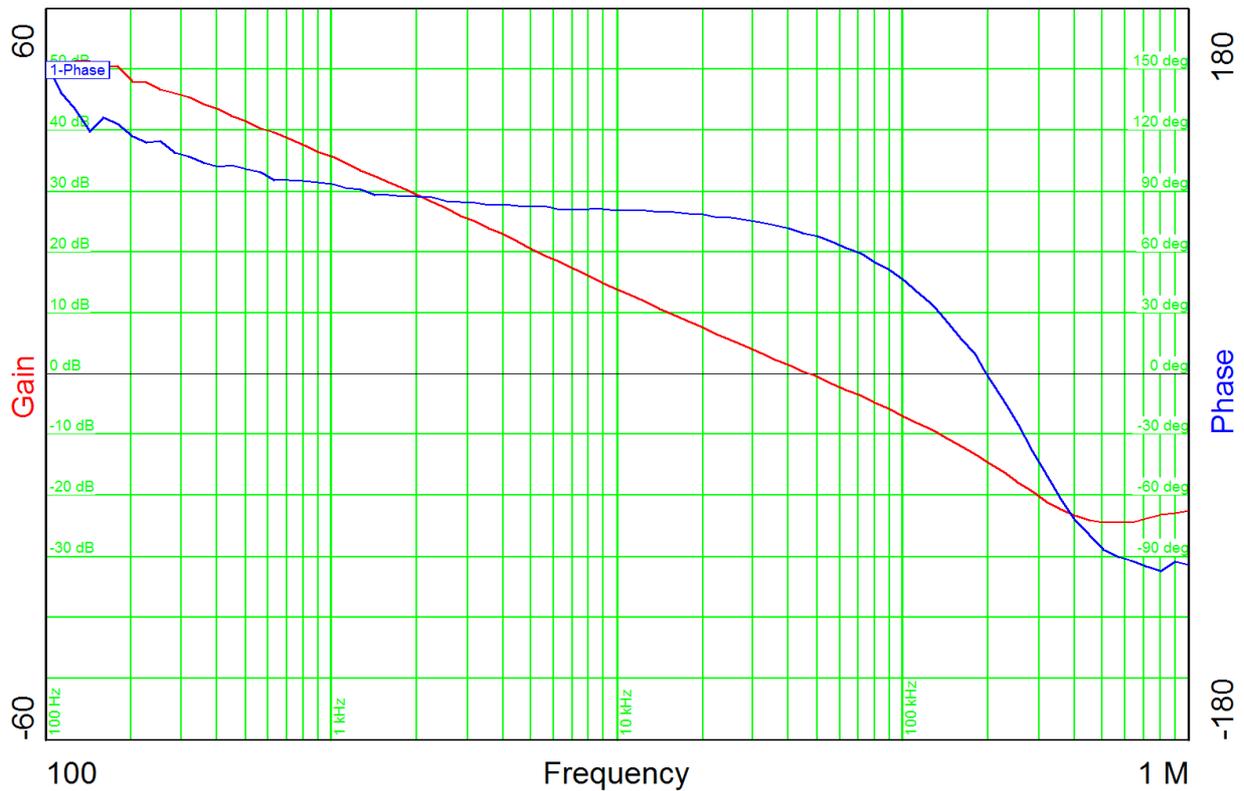


Figure 21

6 Thermal measurement

The thermal image (Figure 22) shows the circuit at an ambient temperature of 21 °C with an input voltage of 7.0V and a load of 1.1A on the 5.0V buck, 0.6A load on the 3.3V buck and 1.0A on the 1.32V buck.

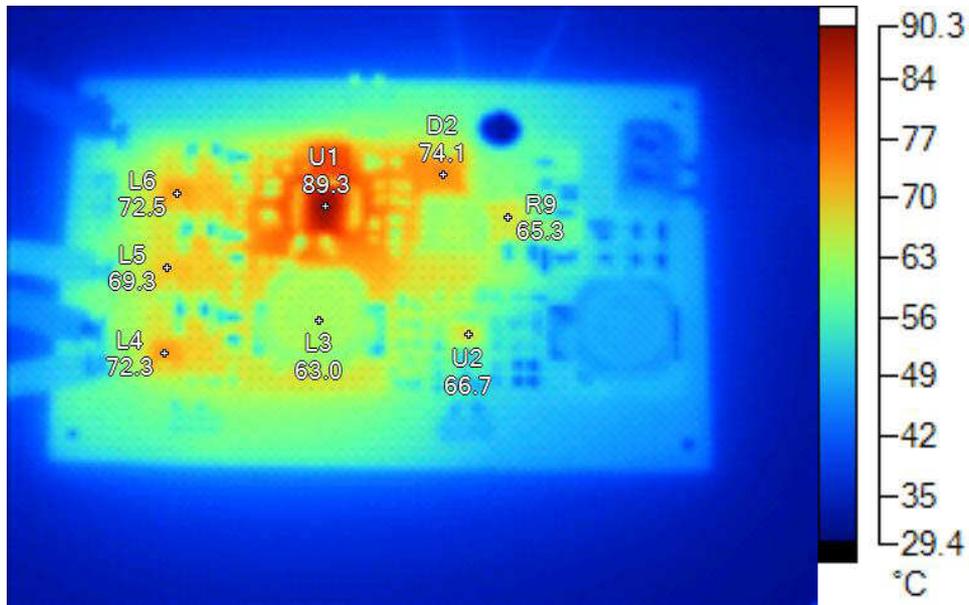


Figure 22

Name	Temperature	Emissivity	Background
U1	89.3°C	0.95	21.0°C
U2	66.7°C	0.95	21.0°C
L3	63.0°C	0.95	21.0°C
L6	72.5°C	0.95	21.0°C
L5	69.3°C	0.95	21.0°C
L4	72.3°C	0.95	21.0°C
D2	74.1°C	0.95	21.0°C
R9	65.3°C	0.95	21.0°C

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated