

Save Power with Negative-Edge-Triggered Flip-flops in Automotive CAN Applications

Dylan Hubbard



Introduction

In the ideal case, an idle electronic control unit (ECU) would consume no current when the vehicle is powered off. Unfortunately, Controller Area Network (CAN) controllers must continue to monitor the CAN bus for communications, therefore they are often left powered on and consume a significant amount of power, which eats into the standby power budget. By using the Schmitt-Trigger Integrated High Speed CMOS (HCS) logic family's new negative-edge triggered D-type flip-flop function, **SN74HCS72-Q1**, the majority of the power-hungry components can be turned off until they are required for operation.

	Low Power	Noise Rejection	Supports Slow Inputs
Input Voltage Waveforms			
Standard CMOS Input			
Schmitt-trigger CMOS Input			

Figure 1. Benefits of HCS Schmitt-trigger Inputs

Benefits of Using SN74HCS72-Q1

- Triggers off falling edge for immediate response from CAN wake-up pattern
- Low standby power consumption (2- μ A max)
- High input noise margins help mitigate false triggers
- Flexibility to accommodate active-high or active-low enables with complementary outputs
- Allows for less complex CAN transceivers saving power, size, and cost

Solution Implementation

The CAN protocol has a predefined wake-up pattern that tells the CAN transceiver to come out of standby mode. This wake-pattern will be key to the implementation of this low power CAN wake solution. An example of this circuit is illustrated in [Figure 2](#).

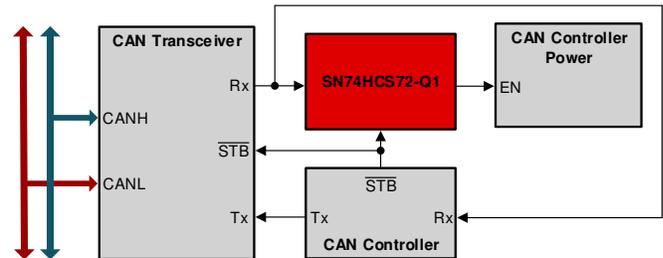


Figure 2. Low Power CAN Wake Solution

When the CAN transceiver interprets the wake-up pattern, it creates a LOW pulse at the RX pin which is typically HIGH in standby mode. With the RX pin connected to the flip-flop's CLK pin, the **SN74HCS72-Q1** will utilize the falling edge of that LOW pulse to assert the enable of whatever controls the power of the CAN controller. This can be a SBC, LDO, DC/DC or PMIC, which can then begin power sequencing or just powering the CAN controller. Once the CAN controller is done performing the actions needed, it will send a LOW signal to both clear the **SN74HCS72-Q1** and put the CAN transceiver back into standby mode to await the next wake-up pattern. An example timing diagram is provided in [Figure 3](#) to illustrate this process.

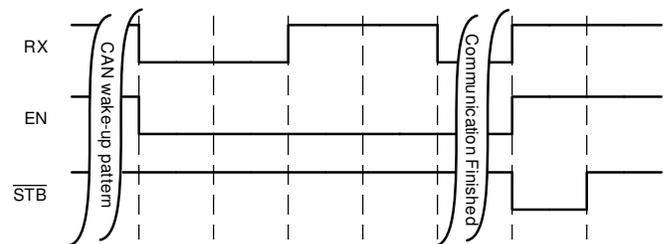


Figure 3. CAN Wake Timing Diagram

The **SN74HCS72-Q1** is the recommended solution for this application because it provides flexibility using complimentary outputs and conserves standby mode power budget with a maximum I_{CC} of only 2 μ A. Other devices in the HCS family can also be implemented for additional functionality in the circuit, for example if there are multiple CAN channels to monitor, an OR gate can be added to combine the enable signals.

1 References

1.1 Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated