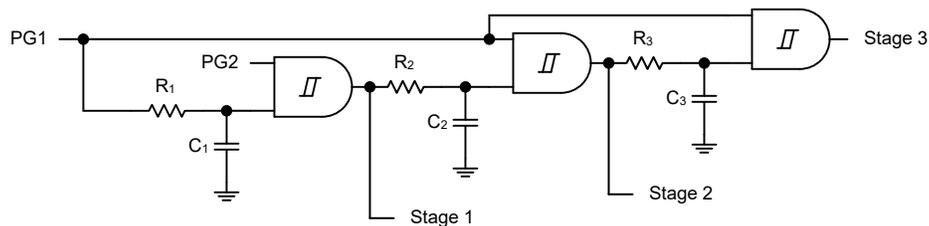


Sequence Supplies With Simple Timers and Logic



In many modern systems, multiple power supplies must be turned on in a pre-defined sequence before the system controller can be started. Often the exact timing of this is not as important as the order of operations. For these applications, logic gates with Schmitt-trigger inputs provide a fast and easy way to provide a reliable power-up sequence with minimum added power consumption.



Example: Using Logic to Provide a Power-Up Sequence

Design Considerations

- Schmitt-trigger inputs are a requirement for applying slow signals to a CMOS device; these can come from an individual Schmitt-trigger buffers such as the SN74LVC1G17, or be integrated as with the SN74LVC1G57 and the SN74HCS08
- Power the start-up logic directly from the system supply when possible; when not possible, a dedicated regulator can be used without much power loss due to the extremely low power consumption of CMOS logic gates
- Tying one PG signal directly to each AND gate can prevent later stages from ramping if the first PG signal goes LOW
- Expect a delay of approximately $2 \times R \times C$ for each RC circuit. For an example, a 10-k Ω resistor and 0.1- μ F capacitor is expected to provide approximately 2 ms of delay
- If any input is larger than V_{CC} , verify in the data sheet for your selected logic gate, if this is supported
- [\[FAQ\] How do I determine the output voltage or output current of a CMOS logic device?](#)
- Need additional assistance? Ask our engineers a question on the [TI E2E™ logic support forum](#)

Recommended Parts

Part Number	Automotive Qualified	V _{CC} Range	Type	Features
SN74HCS08-Q1	✓	2 V – 6 V	Quad AND gate	Schmitt-trigger inputs Positive input clamp diodes on all pins; add series resistors if input voltage exceeds V _{CC}
SN74HCS08				
SN74LVC1G17-Q1	✓	1.65 V – 5.5 V	Schmitt-trigger buffer	Schmitt-trigger inputs Inputs are overvoltage tolerant; signals can exceed V _{CC}
SN74LVC1G17				
SN74LVC1G57				
SN74LVC1G58		1.65 V – 5.5 V	Configurable Logic Gate	Schmitt-trigger inputs Between the '1G57 and '1G58, all 2-input logic gate functions can be produced. See data sheets for details.

For more devices, browse the [online parametric tool](#) where products can be sorted by desired voltage, channel numbers, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated