

High Current LDO Linear Regulators (UCCx81-ADJ, UCx82-ADJ, UCCx83-ADJ, UCx85-ADJ)

Jeff Falin

PMP Portable Power

ABSTRACT

This application provides an overview of the UCCx81-ADJ, UCx82-ADJ, UCCx83-ADJ, and UCx85-ADJ devices.

High-Current Low Dropout (LDO) Linear Regulators Extended Output Voltage Adjustment Range (1.2 Down to 0.5 V)

The UCCx81-ADJ 1-A, UCx82-ADJ 3-A, UCCx83-ADJ 3-A, and the UCx85-ADJ 5-A LDO regulators were designed to provide output voltages only as low as their internal reference voltages (see data sheets SLUS215A, SLUS214B, SLUS317A, and SLUS212D, respectively, for the exact reference voltage value). Using the auxiliary circuitry highlighted below, each regulator's output voltage range can be extended down to 0.5 V.

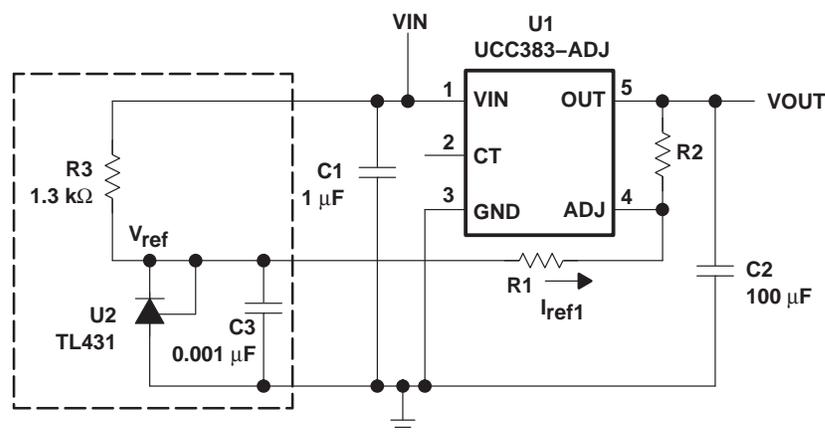


Figure 1. Extended Output Voltage Regulator Schematic

Three components are necessary to extend the output voltage range, an external voltage reference (U2), resistor (R3), and capacitor (C3), in addition to the input and output capacitors (C1 and C2) and feedback resistors (R1 and R2) normally required for the adjustable versions of these regulators. The size of feedback resistors R1 and R2 can be determined from the following equation:

$$I_{ref1} \geq \frac{V_{FB} - V_O}{R2} = \frac{V_{ref} - V_{FB}}{R1}$$

Trademarks are the property of their respective owners.

where:

- I_{ref1} is the value of feedback current normally required for output voltages greater than the regulator's internal reference voltage
- V_{FB} is the regulator's internal reference voltage per the data sheet
- V_O is the output voltage
- V_{ref} is the value of the reference voltage (the TL431 used in this application nominally provides 2.495 V).

The table below shows the values of R1 and R2 for $V_O = 0.7$ V as computed from the internal reference voltage, reference current per the respective data sheets and V_I set to its minimum voltage of 2.8 V.

DEVICE	V_{FB} (V)	I_{ref1} (μ A)	R1 (Ω)	R2 (Ω)
UCCx83-ADJ	1.25	25	49.9k	22k
UCCx81-ADJ	1.25	25	49.9k	22k
UCx82-ADJ	1.2	600	2.15k	835
UCx85-ADJ	1.2	600	2.15k	835

This auxiliary circuit requires that the regulator provide a minimum dc output current of the higher of I_{ref} or the specified minimum output current in the data sheet.

The use of the auxiliary circuitry above degrades the accuracy of the output of the regulator. In fact, assuming a resistor tolerance of $\pm 0.1\%$, reference tolerance of $\pm 2\%$, and UCCx83 regulator reference voltage accuracy of $\pm 1.6\%$ at $T_A = 25^\circ\text{C}$, the error of the adjustable regulator at $T_A = 25^\circ\text{C}$ with $V_O = 0.7$ V can be as high as $\pm 7.75\%$.

To improve accuracy, it is recommended to use the circuit below.

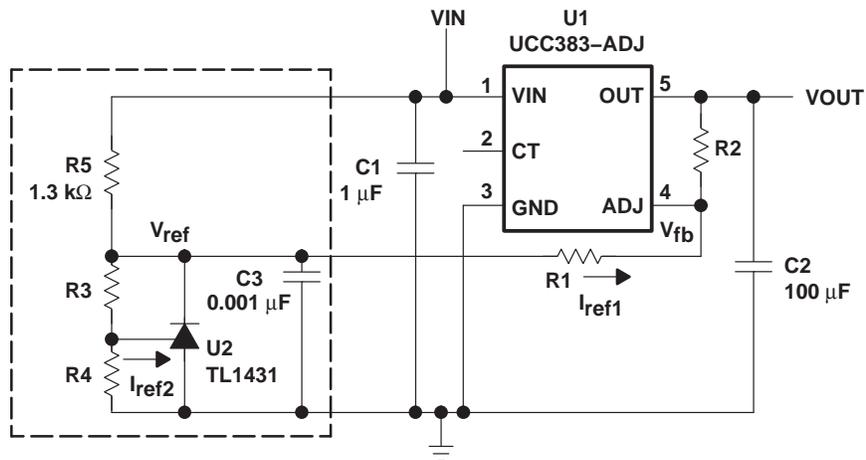


Figure 2. More Accurate Extended Output Voltage Regulator Schematic

The TL431 reference has 0.4% accuracy. The equation for the output voltage from the circuit in Figure 2 is:

$$V_{OUT} = V_{FB} \times \left(\frac{R2}{R1} + 1 \right) - \frac{R2}{R1} \times \left[V_{ref} \times \left(1 + \frac{R3}{R4} \right) + I_{ref2} \times R3 \right]$$

Taking partial derivatives of the equation above with respect to each variable, it is readily apparent that making resistor R1 as large as possible results in the highest accuracy part. Resistor R1 is determined by I_{ref1} , so increasing V_{ref} is the only way to increase R1. Choosing $V_I = 3.3$ V allows $V_{ref} = 3.2$ V and $R1 = 77,700 \Omega$, $R2 = 22,100$, $R3 = 352,000 \Omega$ (for an average $I_{ref2} = 2.0 \mu\text{A}$ between V_I and ground) and $R4 = 2,770 \Omega$. The accuracy is improved from 7.75% to 5.1%. Further increases in R1 improve the accuracy but the efficiency of the part suffers.

The UCCx81-ADJ 1-A regulator can be configured exactly as shown in Figures 1 and 2. The UCx82-ADJ 3-A and the UCx85-ADJ 5-A LDO regulators can be similarly configured; however, they require higher feedback currents and thus lower feedback resistors, so their output voltage tolerance is higher.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2003, Texas Instruments Incorporated