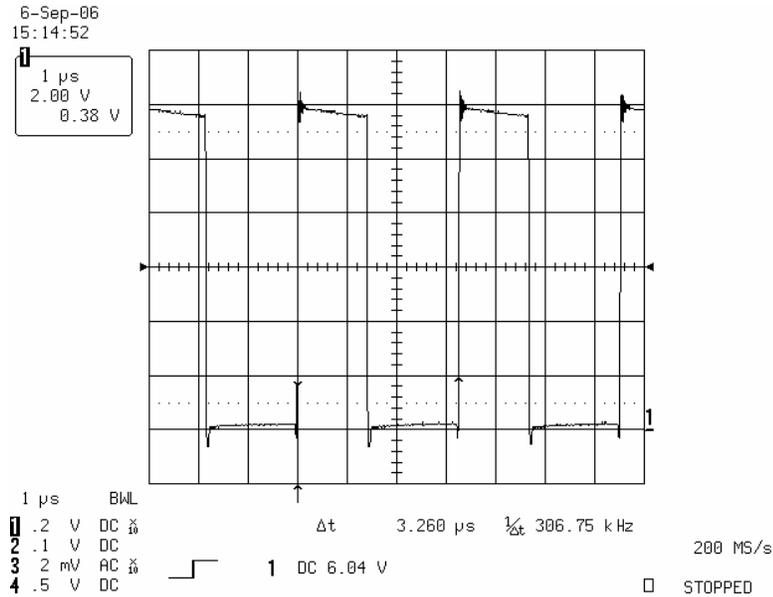



## 1 Switch Node Waveform (5V)

The photo below is of the switching node waveform. The input voltage is 12V and the output is loaded to 6A. The converter is running at 306KHZ.



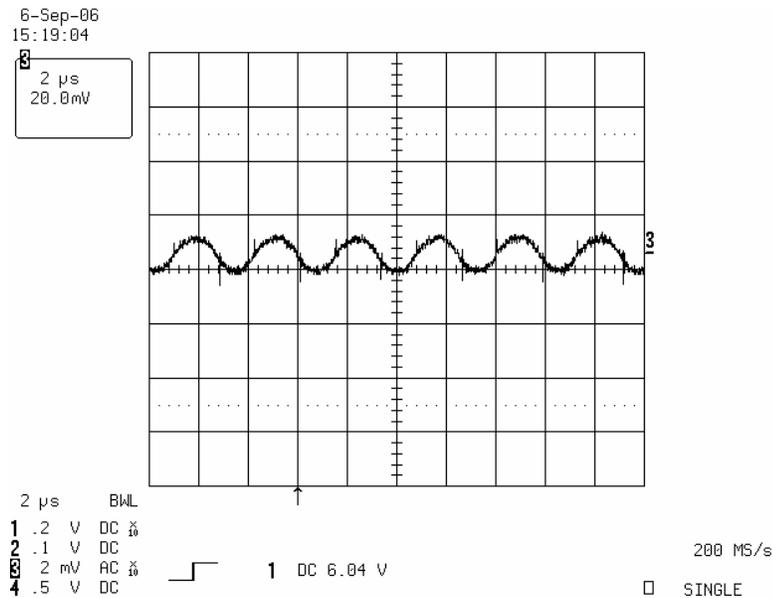
## 2 Output Ripple Voltage (5V)

The 5V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 6A and the input voltage set to 12Vdc.



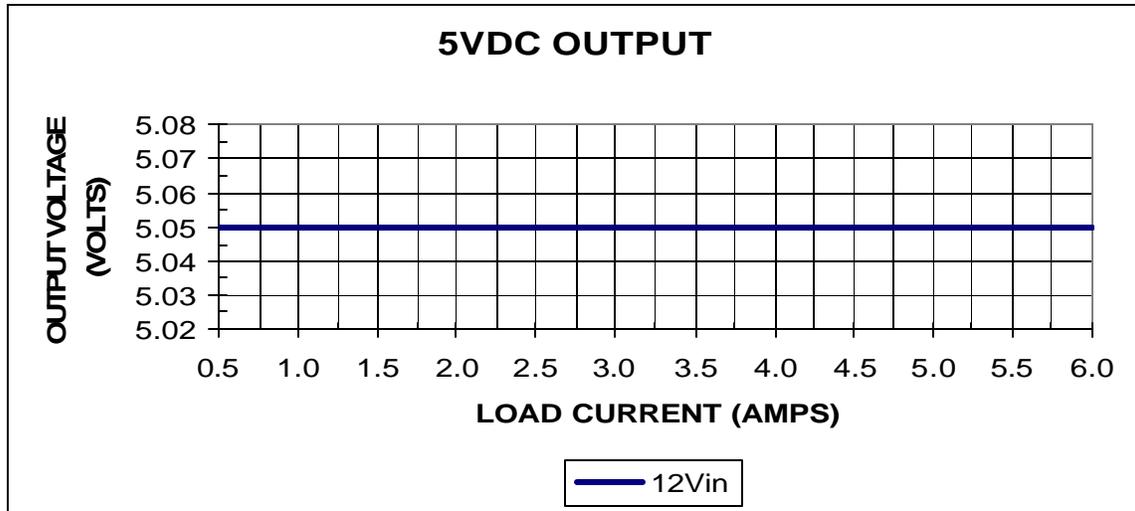
### 3 Load/Line Regulation (5V output)

The converter regulation over load and line are shown in the figures below.


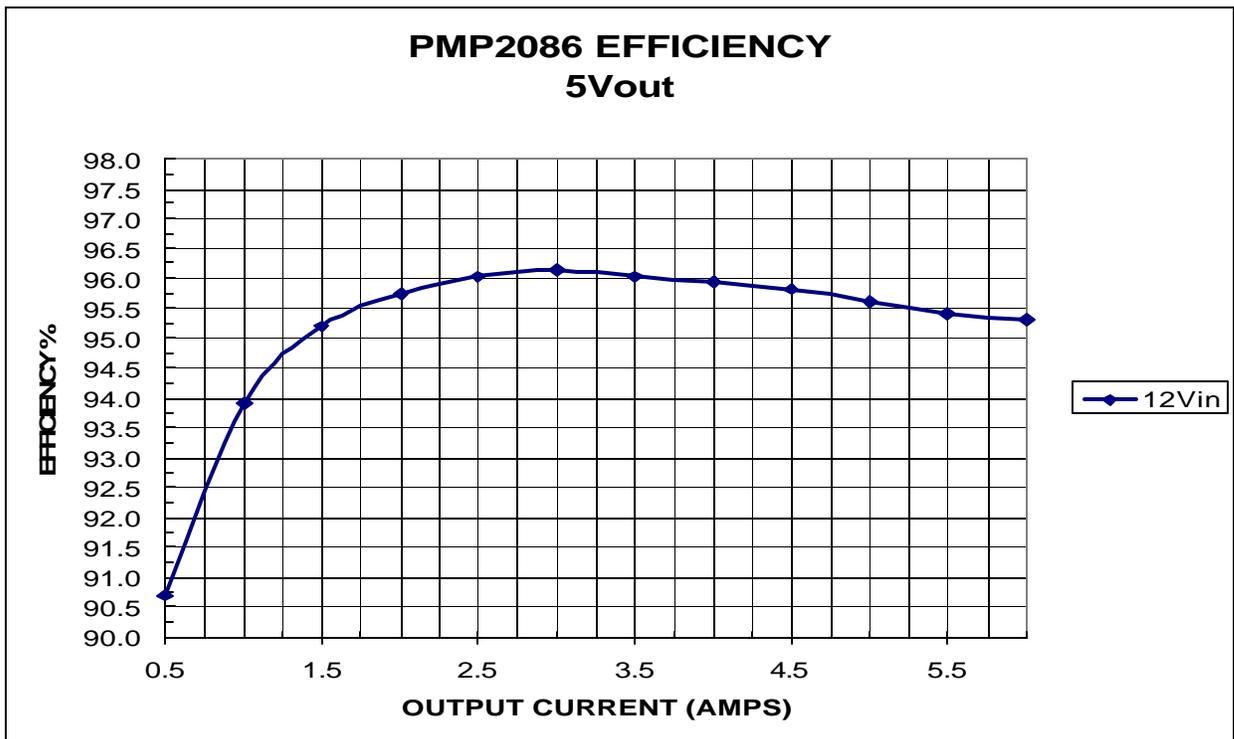
### 4 Efficiency (5V output)



The converter regulation over load and line are shown in the figures below.



## 5 Load Transient (5V)


The photo below shows the 5V output voltage when the load current is pulsed between 1.5A (25%) and 4.5A (75%).

Vin = 12Vdc.

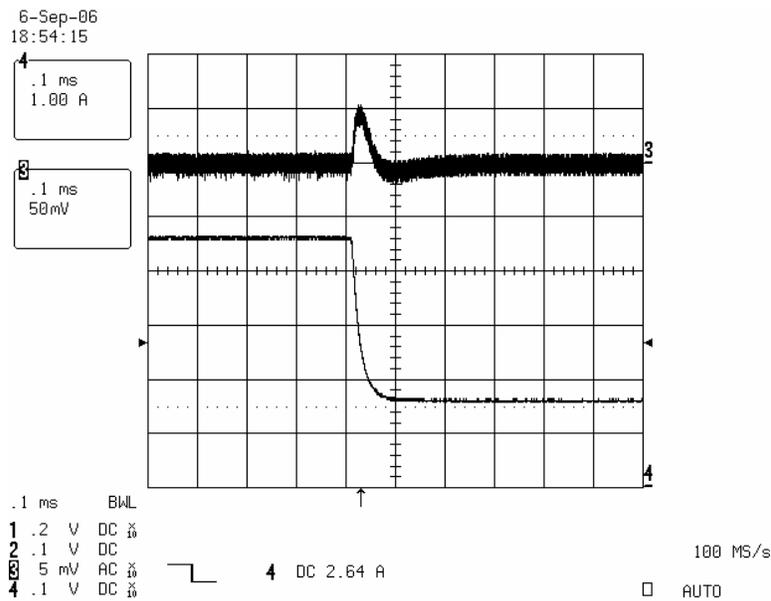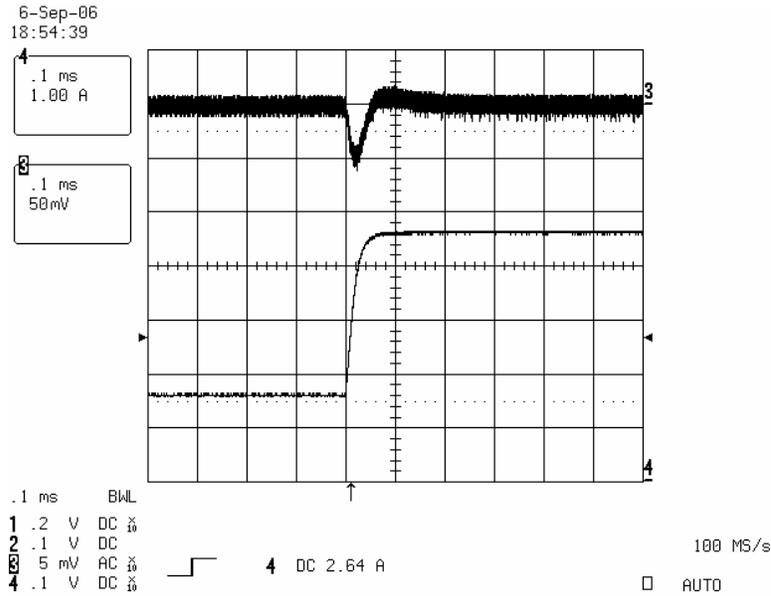

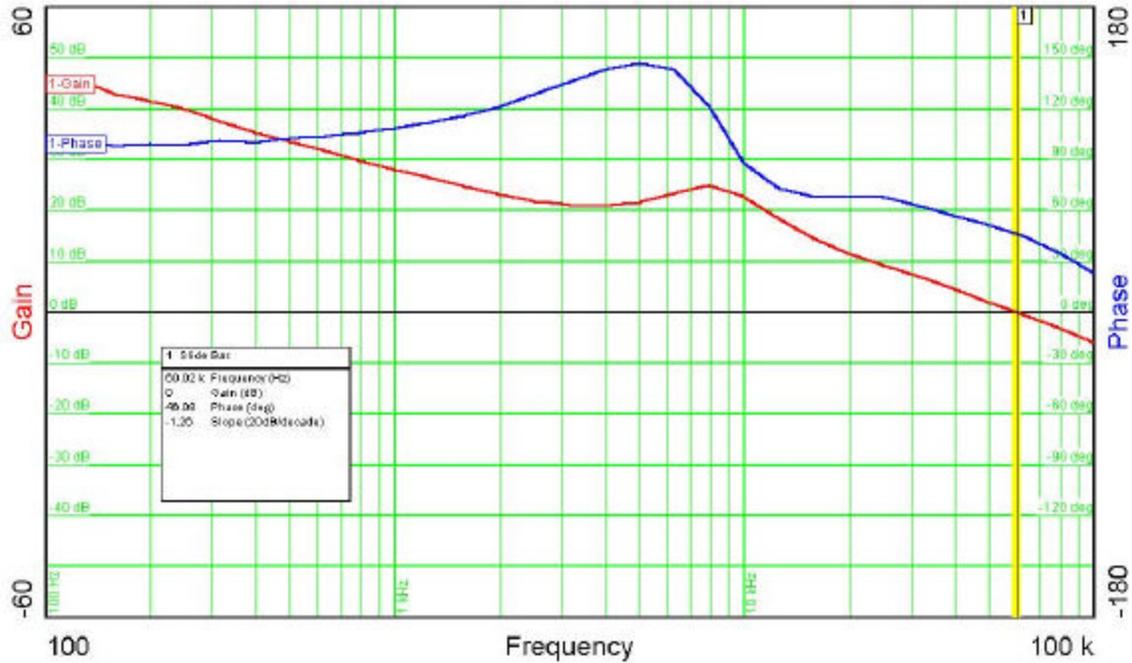
### 6 Control Loop Gain / Stability (1.2V)


The plot below shows the loop gain and phase margin with output voltage set to 5V. The output was loaded to 0A.  $V_{in} = 12V$



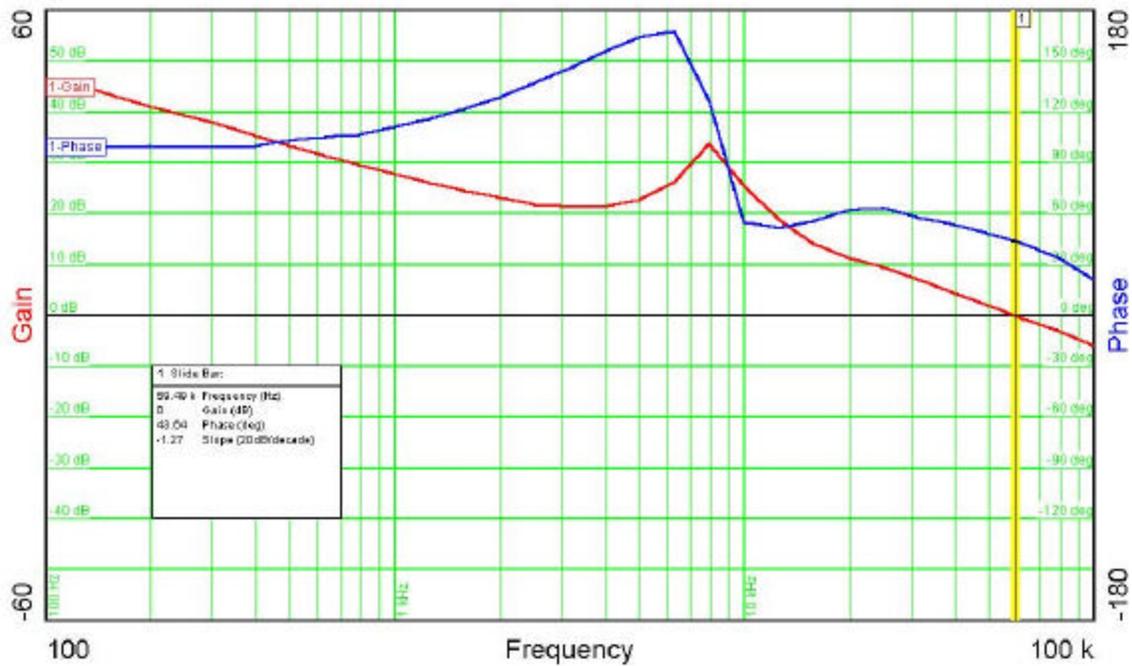
The plot below shows the loop gain and phase margin with output voltage set to 5V. The output was loaded to 3A.  $V_{in} = 12V$



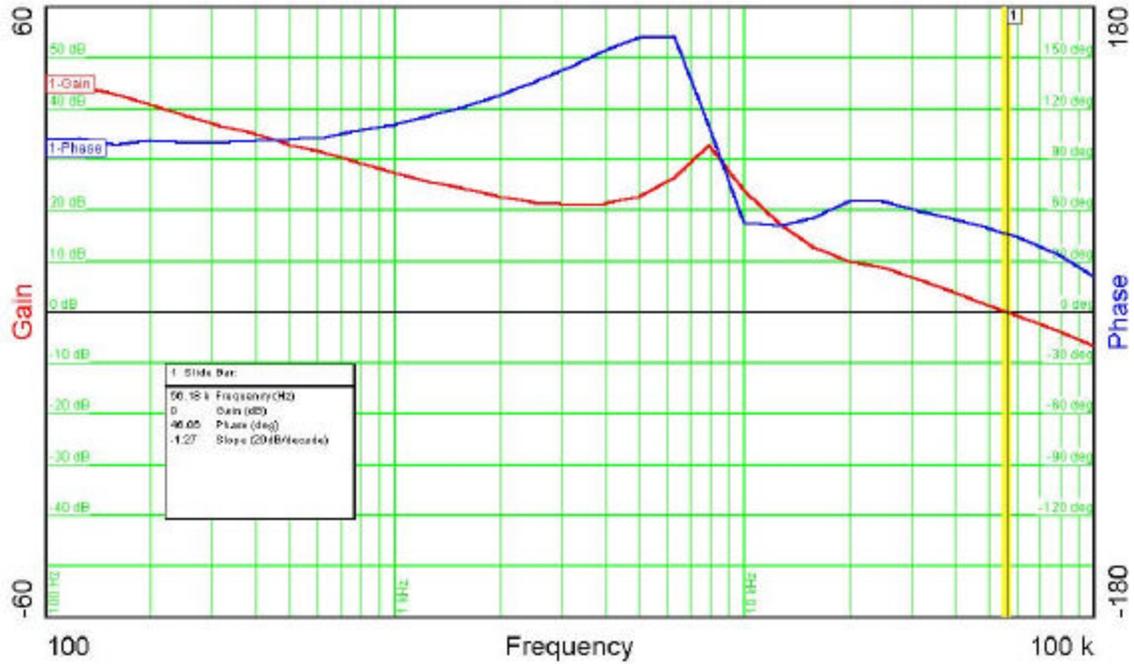The plot below shows the loop gain and phase margin with output voltage set to 5V. The output was loaded to 6A.  $V_{in} = 12V$



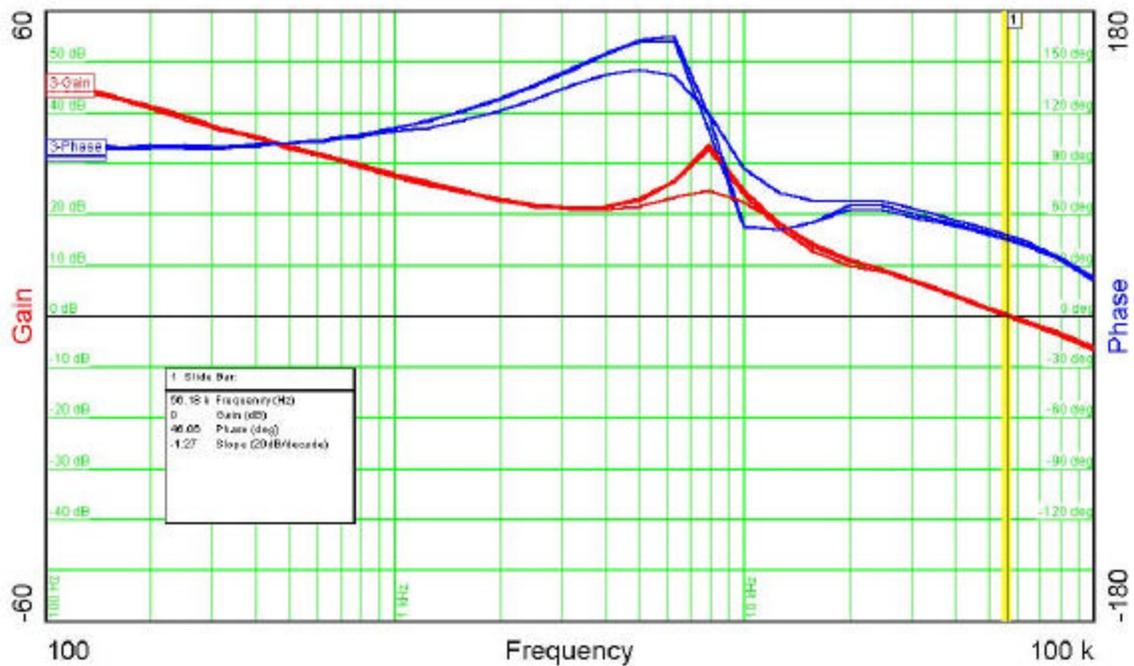The plot below shows the loop gain and phase margin with output voltage set to 5V. The output shows all 3 variations on one graph.




## 7 Output Current Limit (5V)

The output current limit when Vout begins to stop regulating is 20A.
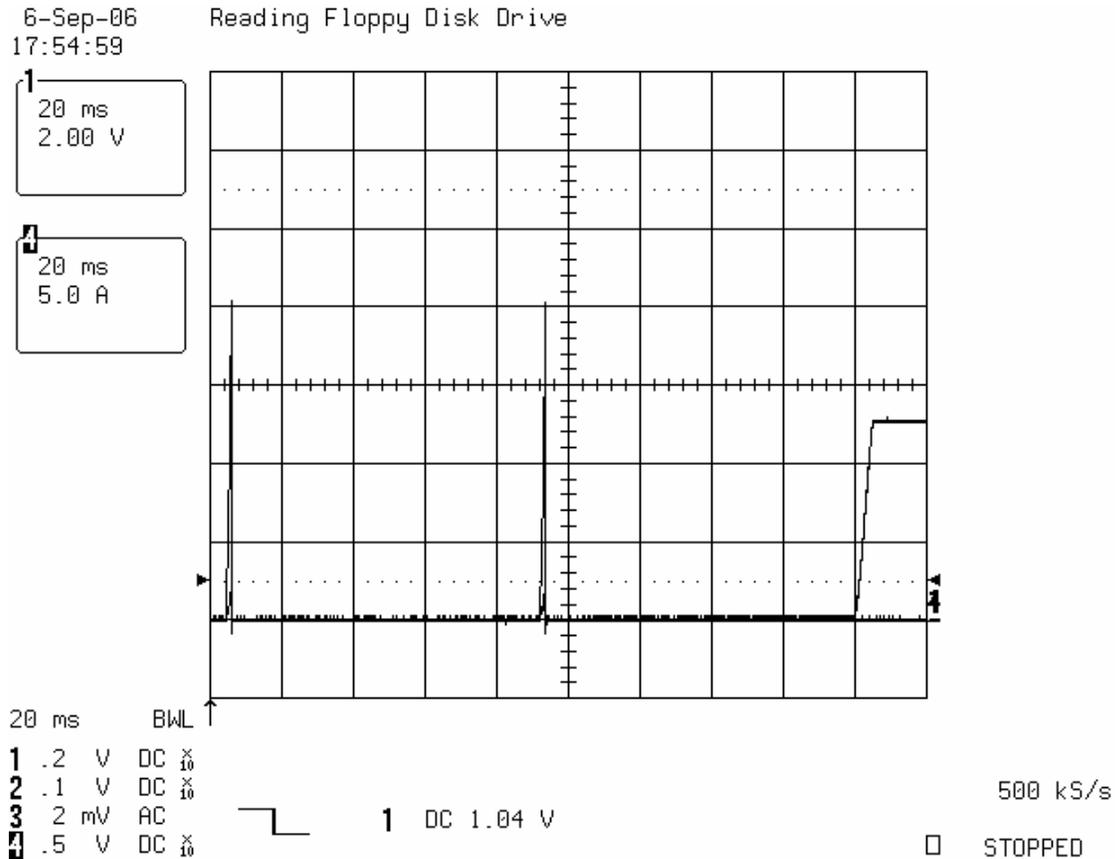
## 8 Short Circuit Current and Recovery (5V)

The short circuit current and recovery time are shown on the graph below. The short circuit current show on the graph below is approx. 20A.




## 9 Short Circuit Power Dissipation (5V)


The short circuit power dissipation drew 13mA for a power dissipation of 156mW.
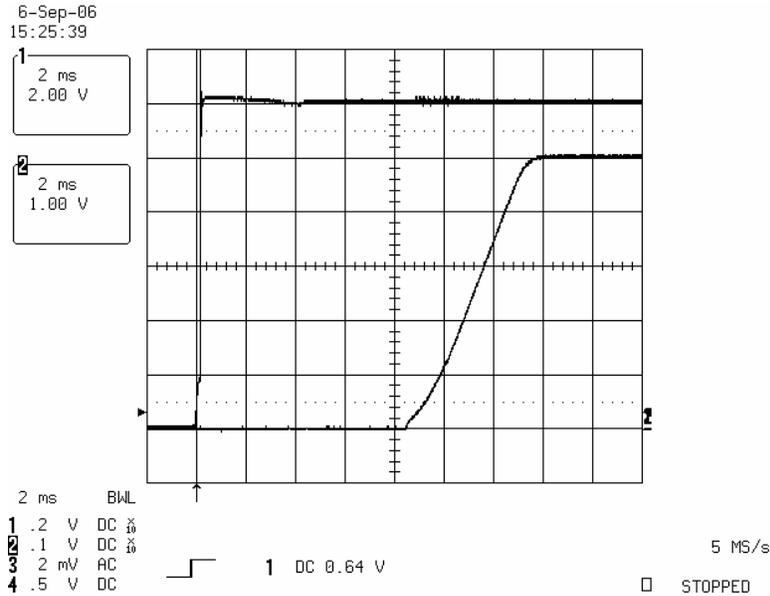
## 10 Startup/Shutdown (5V)


The photo below shows the 5V output voltage (Ch2) startup waveform after the application of 12Vdc in (Ch1). The output was loaded to 0A.



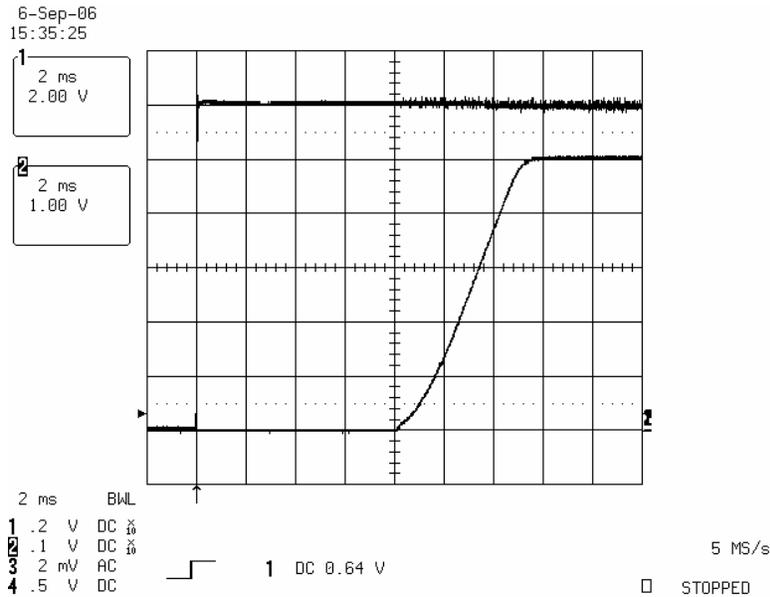
The photo below shows the 5V output voltage (Ch2) startup waveform after the application of 12Vdc in (Ch1). The output was loaded to 3A.



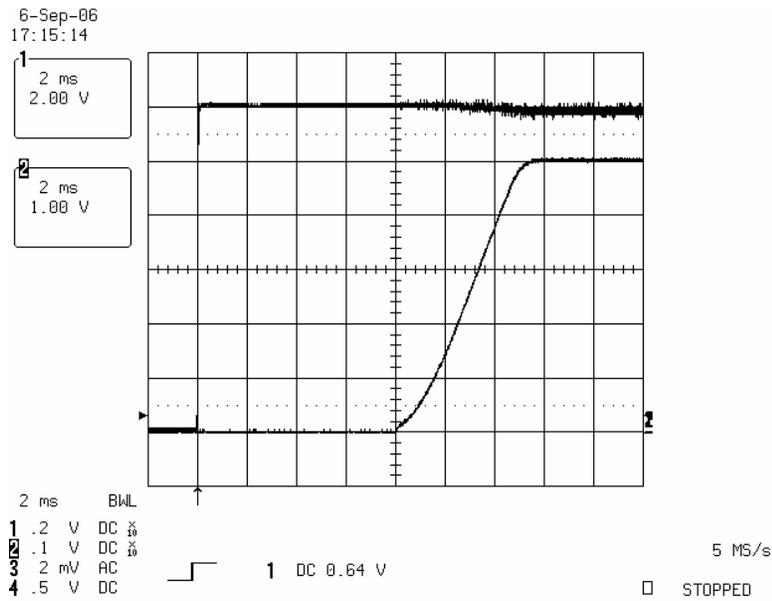The photo below shows the 5V output voltage (Ch2) startup waveform after the application of 12Vdc in (Ch1). The output was loaded to 6A.



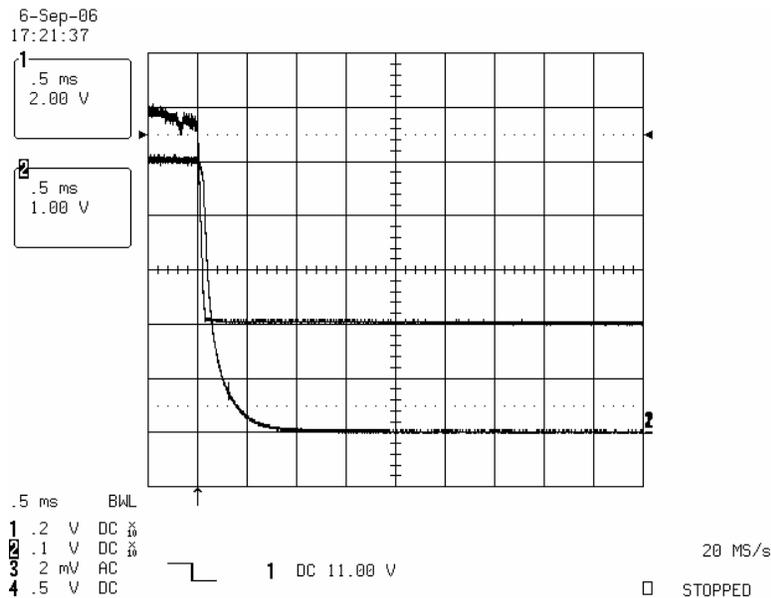The photo below shows the 5V output voltage (Ch2) shutdown waveform after the removal of 12Vdc in (Ch1). The output was loaded to 6A.



## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2008, Texas Instruments Incorporated