

## TI Designs

# Xilinx Kintex UltraScale® MGT Power Supplies (PMP9463)



### System Description

This TI Design demonstrates a proven design for the Multi-Gigabit Transceiver (MGT) power supply rails on the Xilinx Kintex UltraScale® platform. It features +1.0V/8A output for the MGTAVCC, +1.2V/8A output for the MGTAVTT, and +1.8V/1A output for the MGTVCCAUX rails. This design is powered from a +5V input voltage and also provides power-up and power-down sequencing. This design aims for a controller + external FET solution to lower costs vs. an integrated solution.

### Featured Applications

- FPGA

### Design Resources

- Block Diagram and Schematic
- Test Data
- Gerber Files
- Design Files
- Bill of Materials


### Design Features

- 5V Input Voltage
- Full power solution for MGT rails
  - +1.0V/8A MGTAVCC
  - +1.2V/8A MGTAVTT
  - +1.8V/1A MGTVCCAUX
- Power-up and power-down sequencing
- PMBUS compatible interface
- Selectable PMBUS address

### Design Photo



### Block Diagram

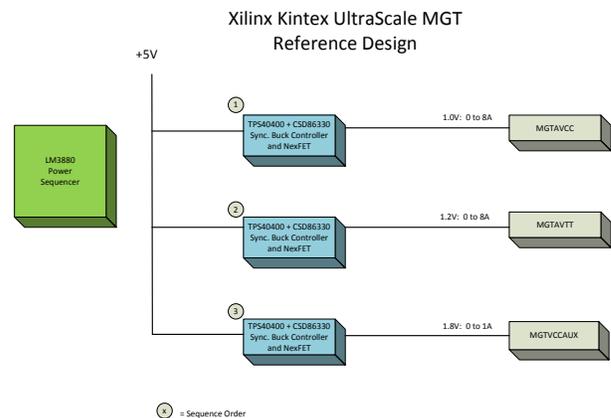

### Jump start system design and speed time to market

Comprehensive designs include schematics or block diagrams, BOMs, design files and test reports by experts with deep system and product knowledge. Designs span TI's portfolio of analog, embedded processor and connectivity products and supports a board range of applications including industrial, automotive, medical, consumer, and more. To explore the designs, go to <http://www.ti.com/tidesigns>

## TI Designs

# Xilinx Kintex UltraScale® MGT Power Supplies (PMP9463)



### Associated Part Numbers

<u>Part Number</u>	<u>Part Description</u>
TPS40400	Synchronous buck controller that operates from a nominal 3V to 20V supply. It is an analog PWM controller that allows programming and monitoring via the PMBus interface.
CSD86330Q3D	Synchronous buck NexFET power block MOSFET pair designed for applications offering high current, efficiency, and frequency capability with a 5V gate drive.
LM3880	Power sequencer that can control power up and power down of multiple power supplies using a precision enable pin and three output flags.
TS3A5017RGY	Dual single-pole quadruple-throw (4:1) analog switch designed to operate from 2.3 to 3.6V. This device can handle both digital and analog signals.

### Design Considerations:

This design goal is to provide a power supply module to power MGT rails (MGTAVCC, MGTAVTT, MGTVCCAUX) on a Xilinx Kintex UltraScale platform and meet the current and voltage requirements. The solution is meant to fit into a 1.95" x 3.00" form factor and include all MGT rails and plug into a customer host characterization platform through mating connectors on the bottom layer. PMBUS, telemetry, sequencing, and low noise were all a requirement for this application.

**MGTAVCC** – The MGTAVCC rail required +1.0V/8A with +/-10mV output ripple and 3% tolerance on load transients.

- 1) TPS40400 was chosen since it's a voltage mode controller for lower output noise and also because of it's PMBUS and telemetry features. CSD86330 was chosen because of it's smaller 3mm x 3mm size, low R<sub>dson</sub>, and current ratings.

**MGTAVTT** – The MGTAVTT rail required +1.2V/8A with +/-10mV output ripple and 3% tolerance on load transients.

- 1) TPS40400 was chosen since it's a voltage mode controller for lower output noise and also because of it's PMBUS and telemetry features. CSD86330 was chosen because of it's smaller 3mm x 3mm size, low R<sub>dson</sub>, and current ratings.

**MGTVCCAUX** – The MGTVCCAUX rail required +1.8V/1A with +/-10mV output ripple and 3% tolerance on load transients.

- 2) TPS40400 was chosen since it's a voltage mode controller for lower output noise and also because of it's PMBUS and telemetry features. CSD86330 was chosen because of it's smaller 3mm x 3mm size, low R<sub>dson</sub>, and current ratings.

**Sequencing** – Power-up and power-down sequencing was a requirement for this design.

- 1) A LM3880 was selected to provide 1-2-3 power-up and 3-2-1 power down sequencing.

**PMBUS Address Selection** – The TSA3A5017RGY is a SP4T switch that gives four different options for PMBUS address for each of the rails. By configuring ALT\_PMBUS\_ADDR0 and ALT\_PMBUS\_ADDR1, the user can select between each of the four addresses.



### **Jump start system design and speed time to market**

Comprehensive designs include schematics or block diagrams, BOMs, design files and test reports by experts with deep system and product knowledge. Designs span TI's portfolio of analog, embedded processor and connectivity products and supports a board range of applications including industrial, automotive, medical, consumer, and more. To explore the designs, go to <http://www.ti.com/tidesigns>

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated