

**Test Report  
For PMP15014  
04/27/2016**




## 1. Design Specifications

<b>Vin Min</b>	<b>4.5VDC</b>
<b>Vin Max</b>	<b>38VDC</b>
<b>Vout</b>	<b>3.3VDC-First stage</b>
<b>Iout</b>	<b>3.5A</b>
<b>Wide Vin DCDC Switching Frequency</b>	<b>2.2MHz</b>
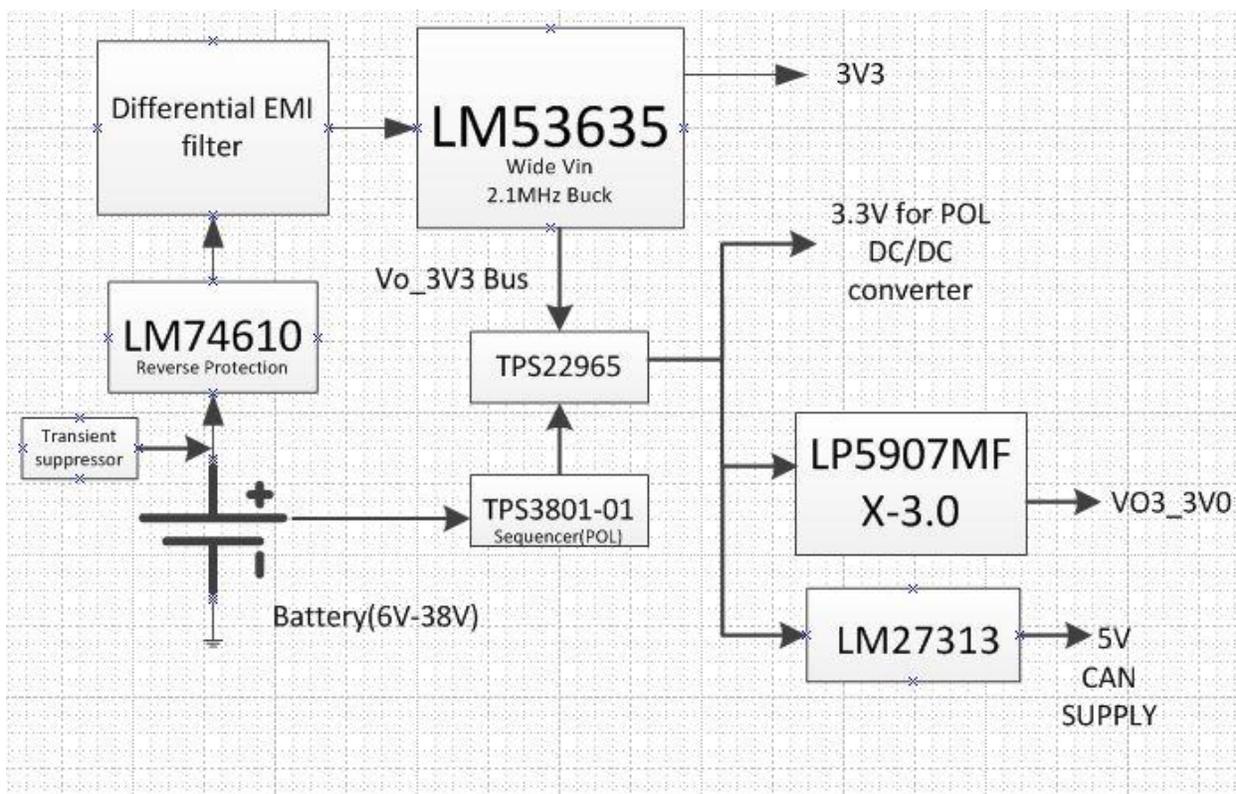
## 2. Circuit Description

This solution is designed to be an automotive off-battery front end power supply for infotainment systems. It was created using a two stage power system meeting high voltage input needs and providing multi output rails for different load needs. The system also provides transient and reverse polarity protection. Both stages of power are working at 2.1Mhz to provide good EMI performance with an EMI filter to support CISPER 25. The block diagram is as below.




### 3. Board Photos




Top (75x25mm<sup>2</sup>)

### 4. Thermal Data

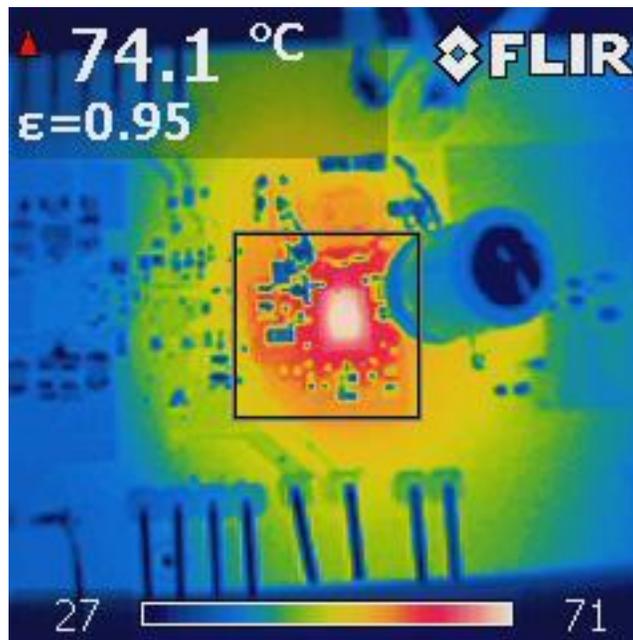

IR thermal image taken at steady state at Full load and  $V_{IN} = 12V$  with no airflow

## 5. Efficiency

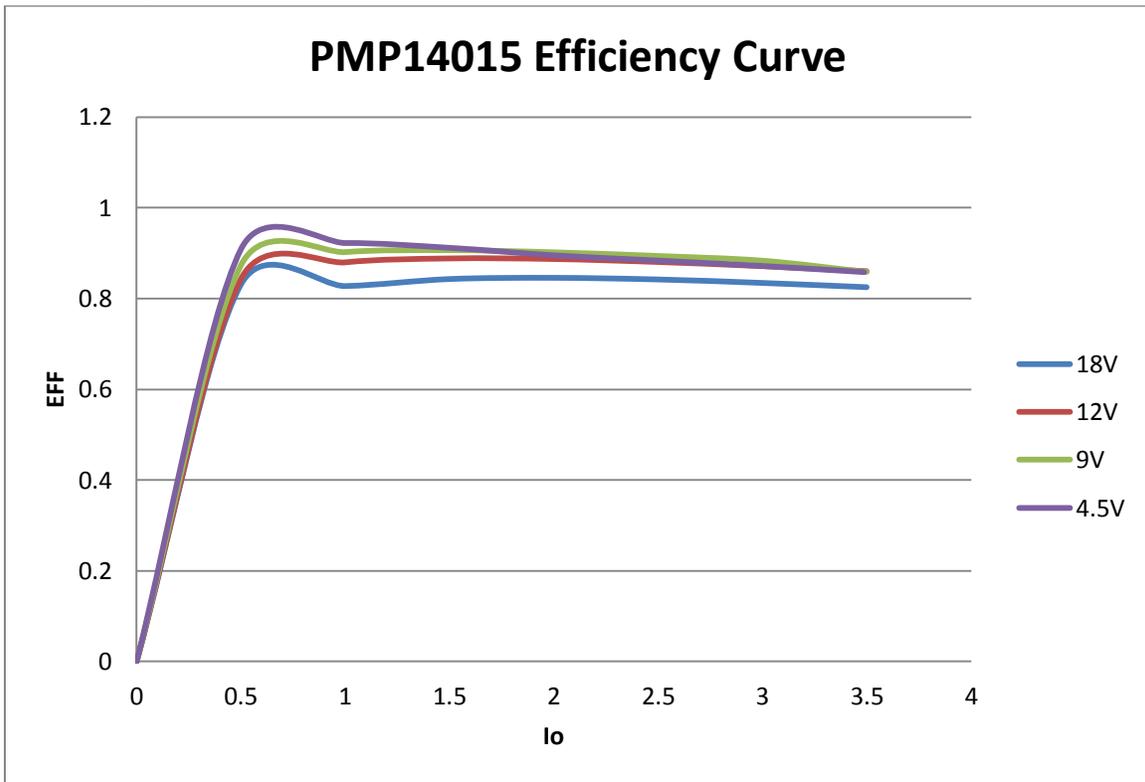

## 6. Waveform

### 6.1 Load Transient (Slew Rate: 100mA/uS)




$V_{IN}=12V$ , 3V3 Channel: 1.75A-3A-1.75A



Agilent Technologies

THU MAY 12 14:04:21 2016

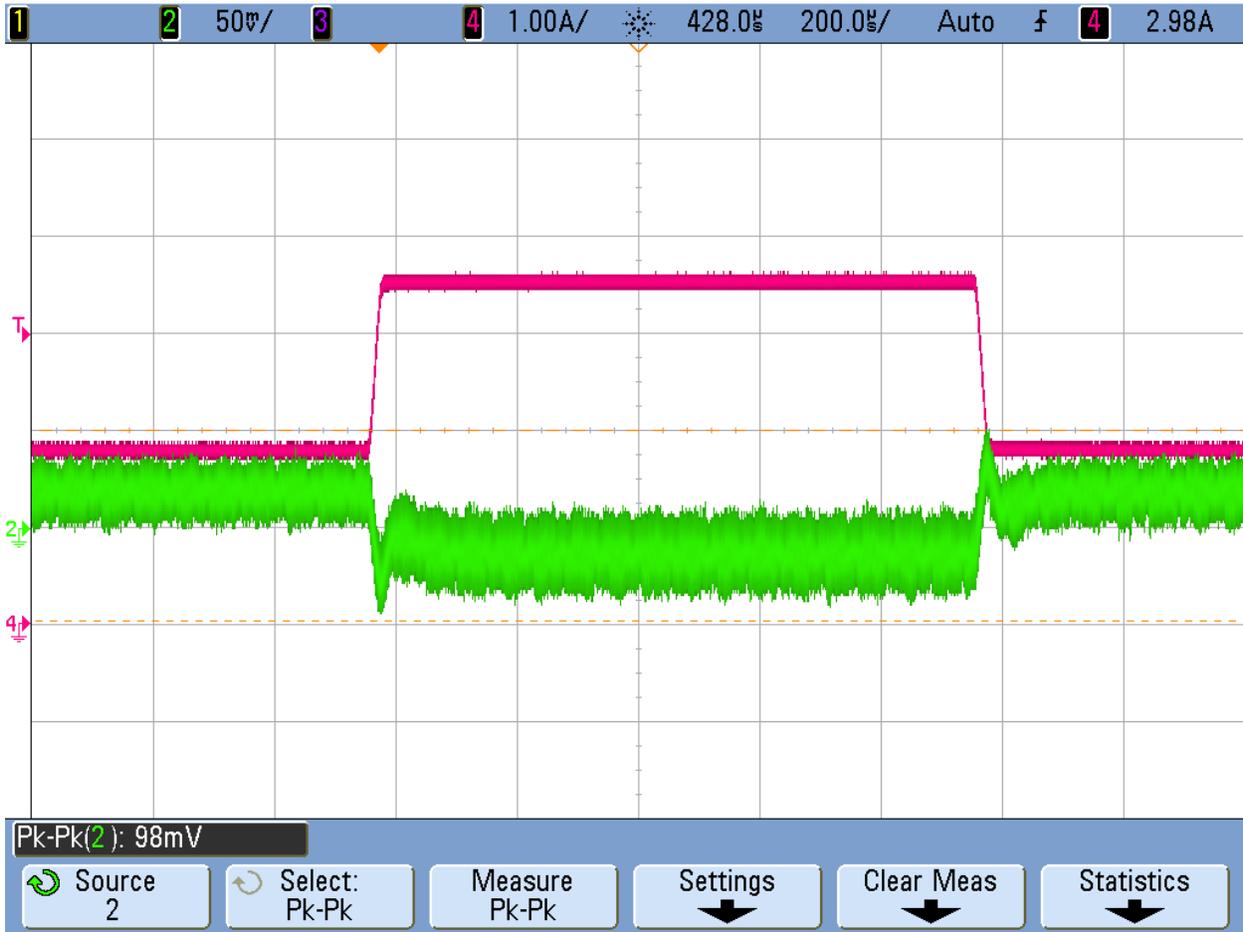


$V_{IN}=18V, 3V3$  Channel: 1.75A-3A-1.75A



Agilent Technologies

THU MAY 12 14:04:35 2016

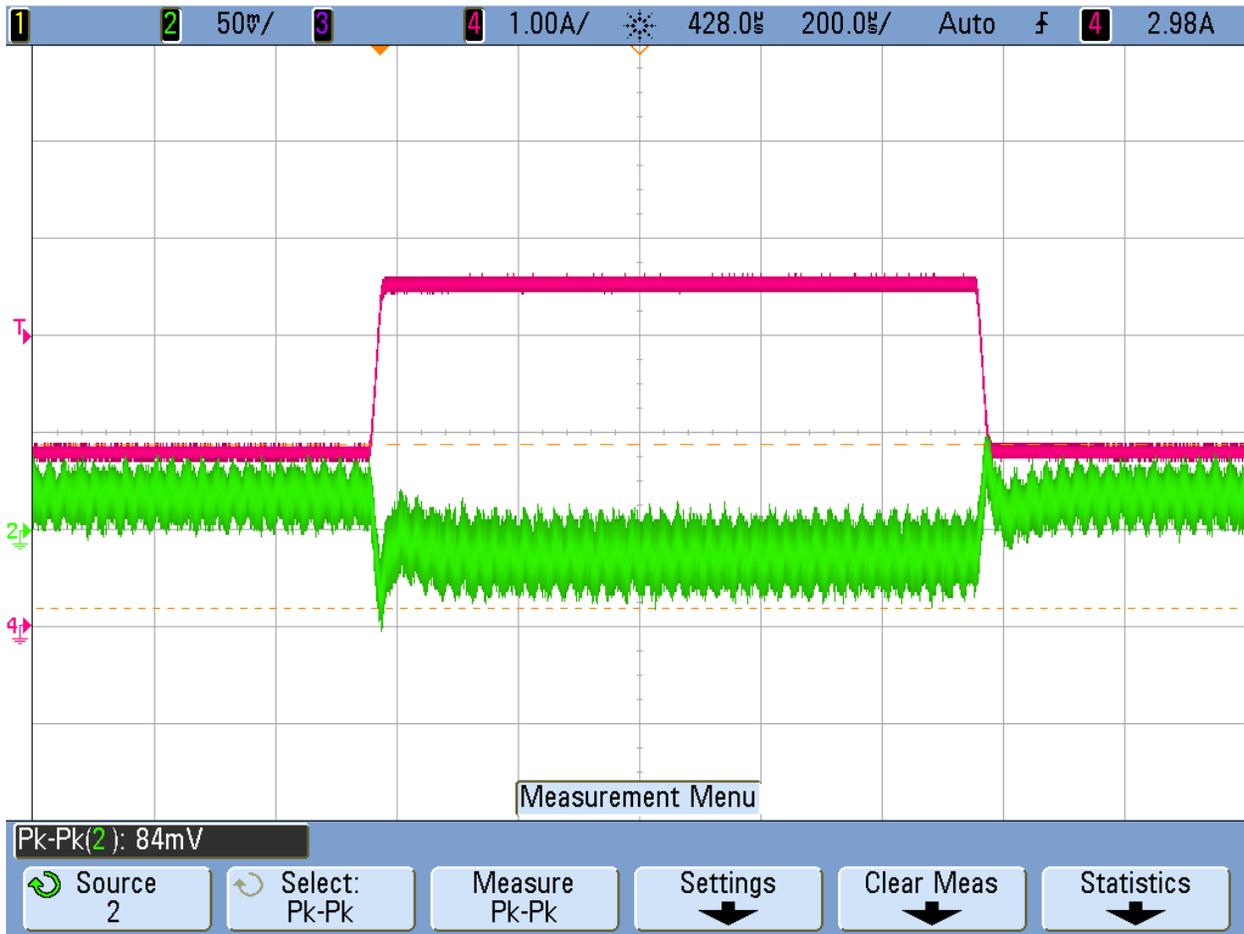


$V_{IN}=9V$ , 3V3 Channel: 1.75A-3A-1.75A



Agilent Technologies

THU MAY 12 15:39:30 2016

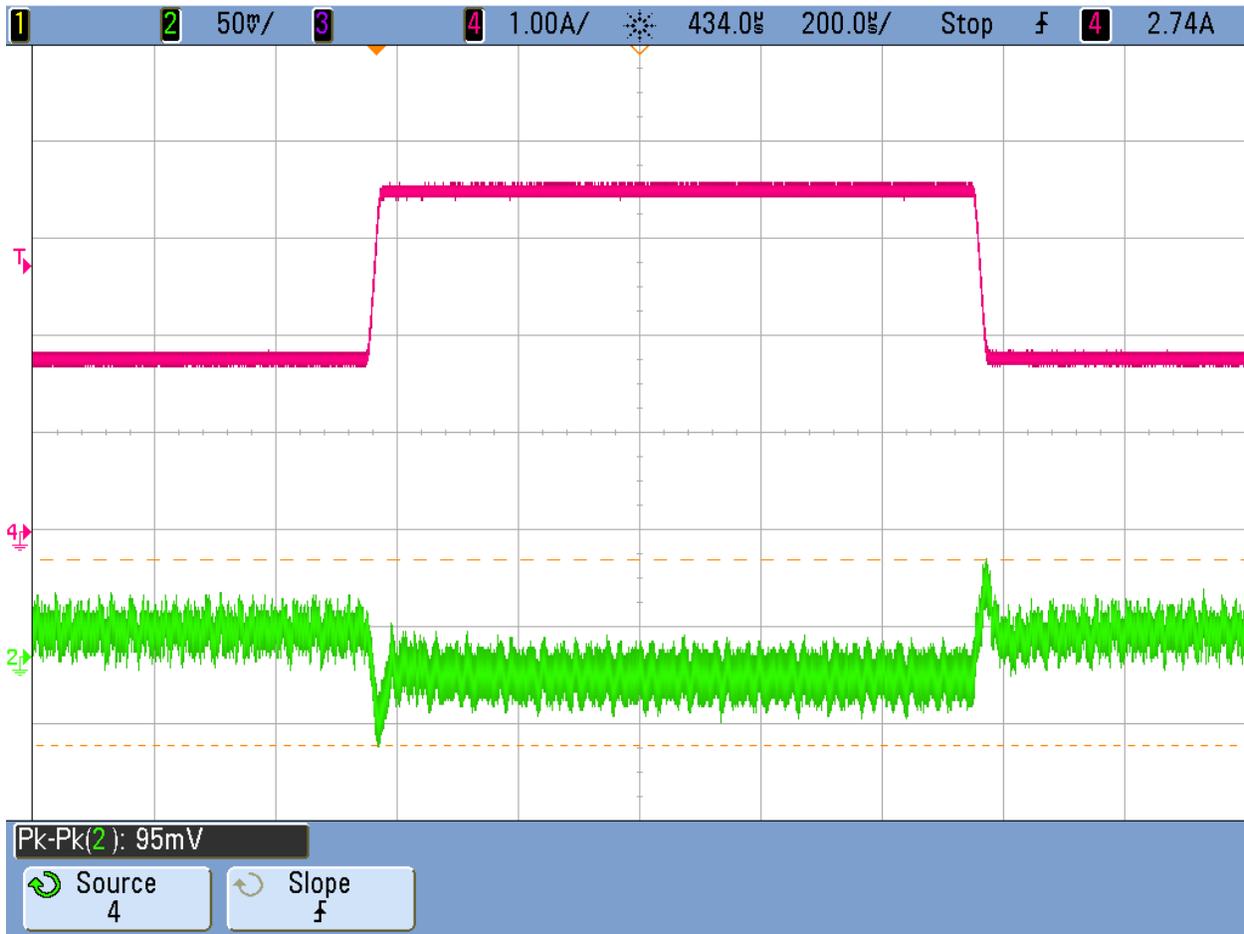

$V_{IN}=4.5V$ , 3V3 Channel: 1.75A-3A-1.75A

## 6.2 Start up




12Vin 3.3Vo Io=3.5A




12Vin 3.3Vo Io=0A

### 6.3 Ripple

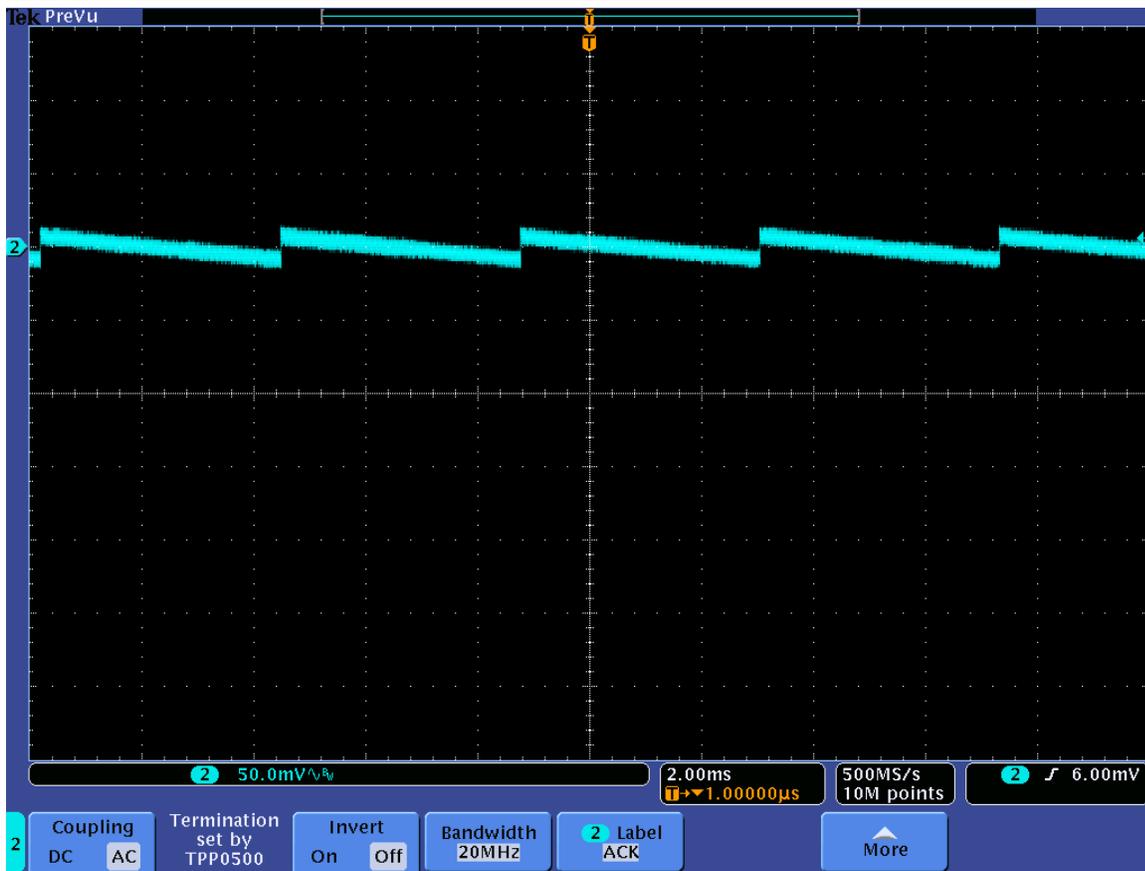


12Vin 3.3Vo Io=0A

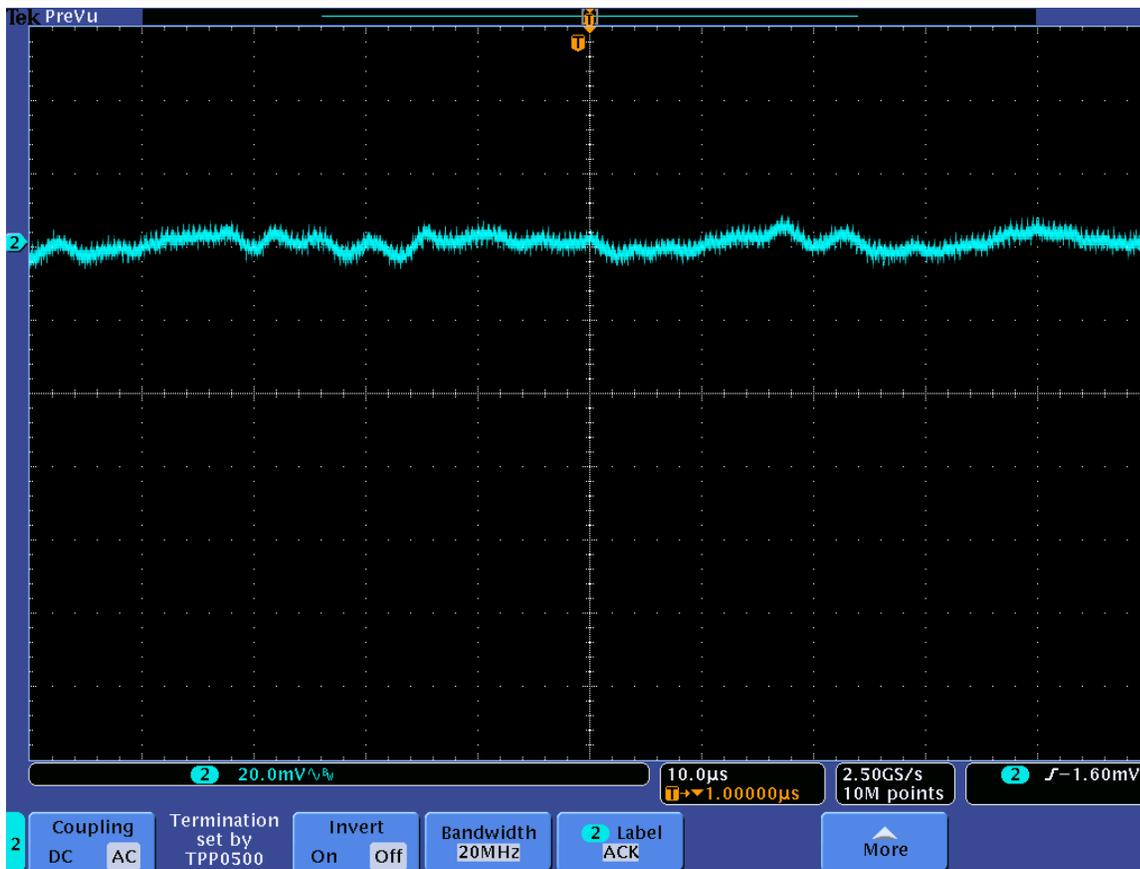


12Vin 3.3Vo Io=3.5A


### 6.3 SW Waveform

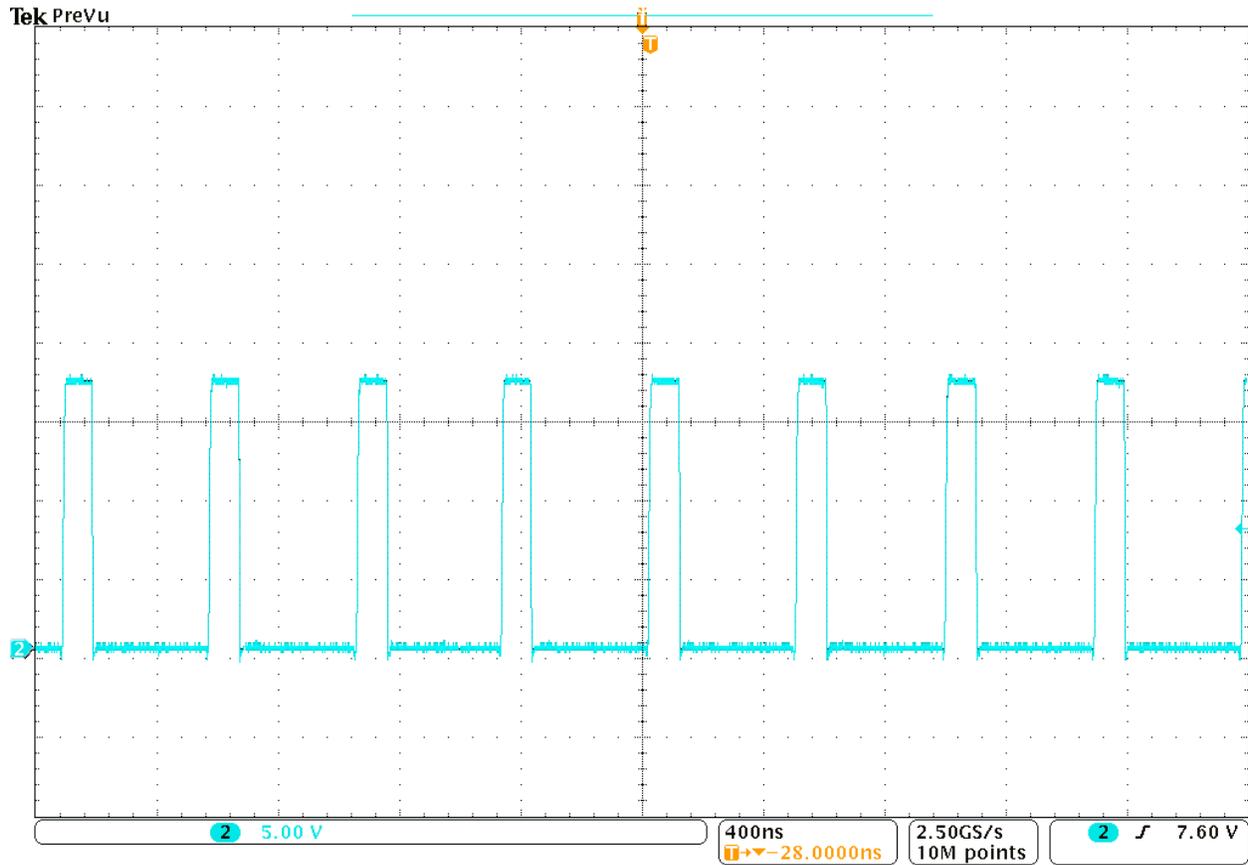


18Vin 3.3Vo Io=3.5A

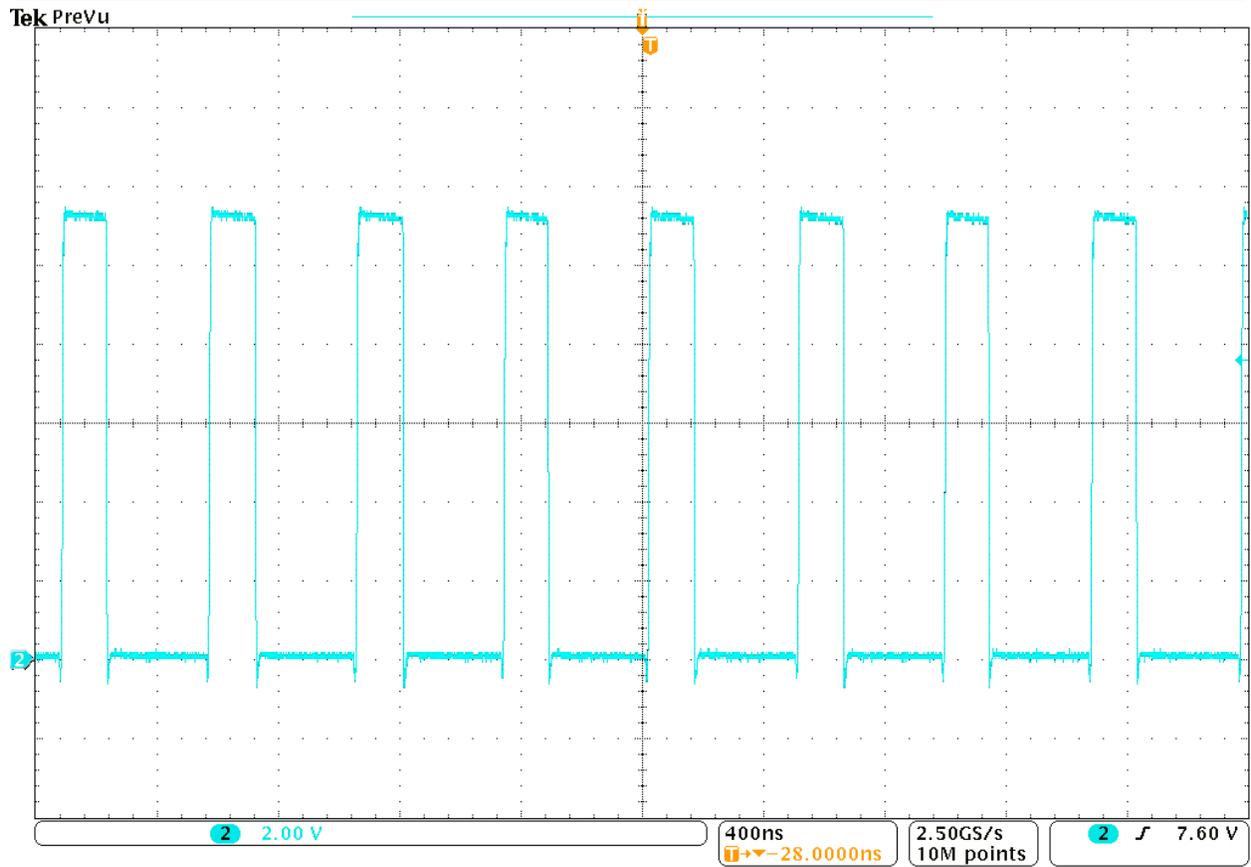

12Vin 3.3Vo Io=3.5A

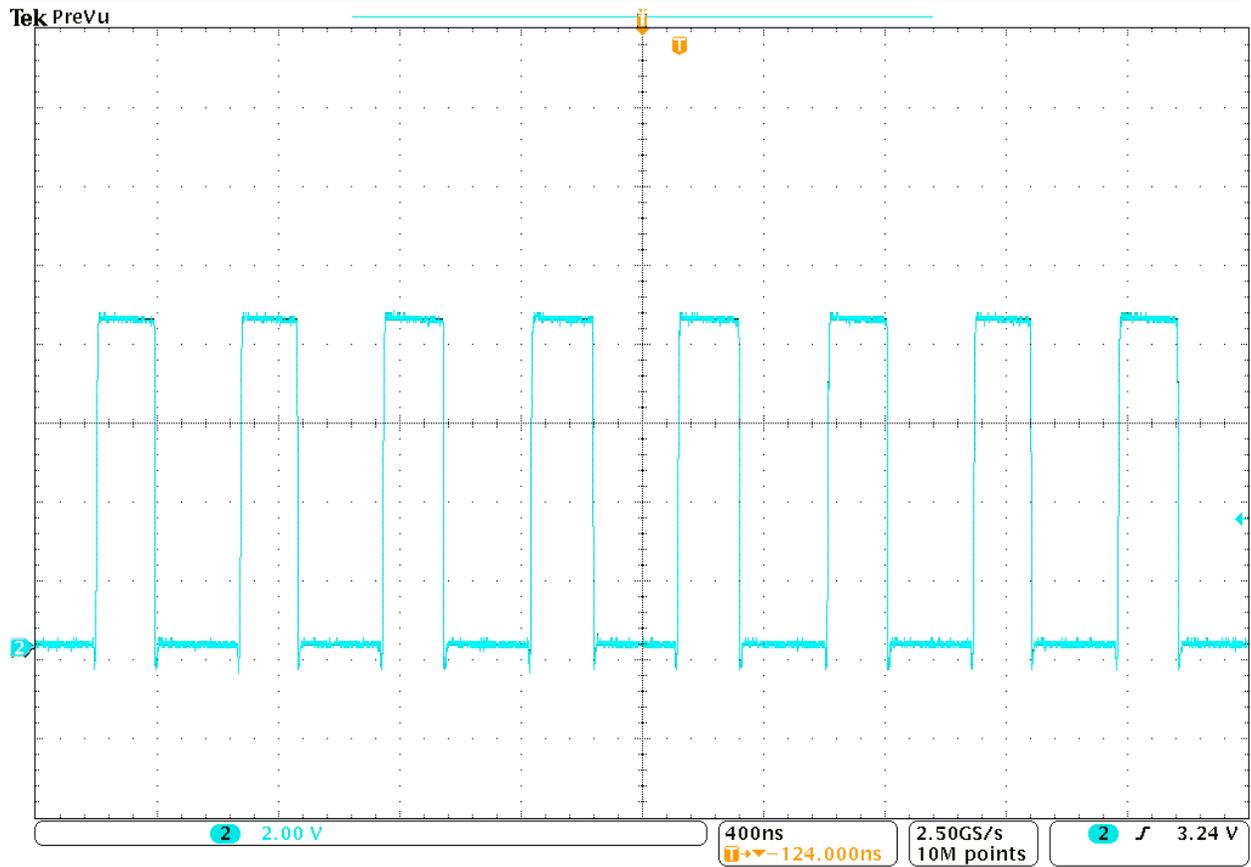


9Vin 3.3Vo Io=3.5A

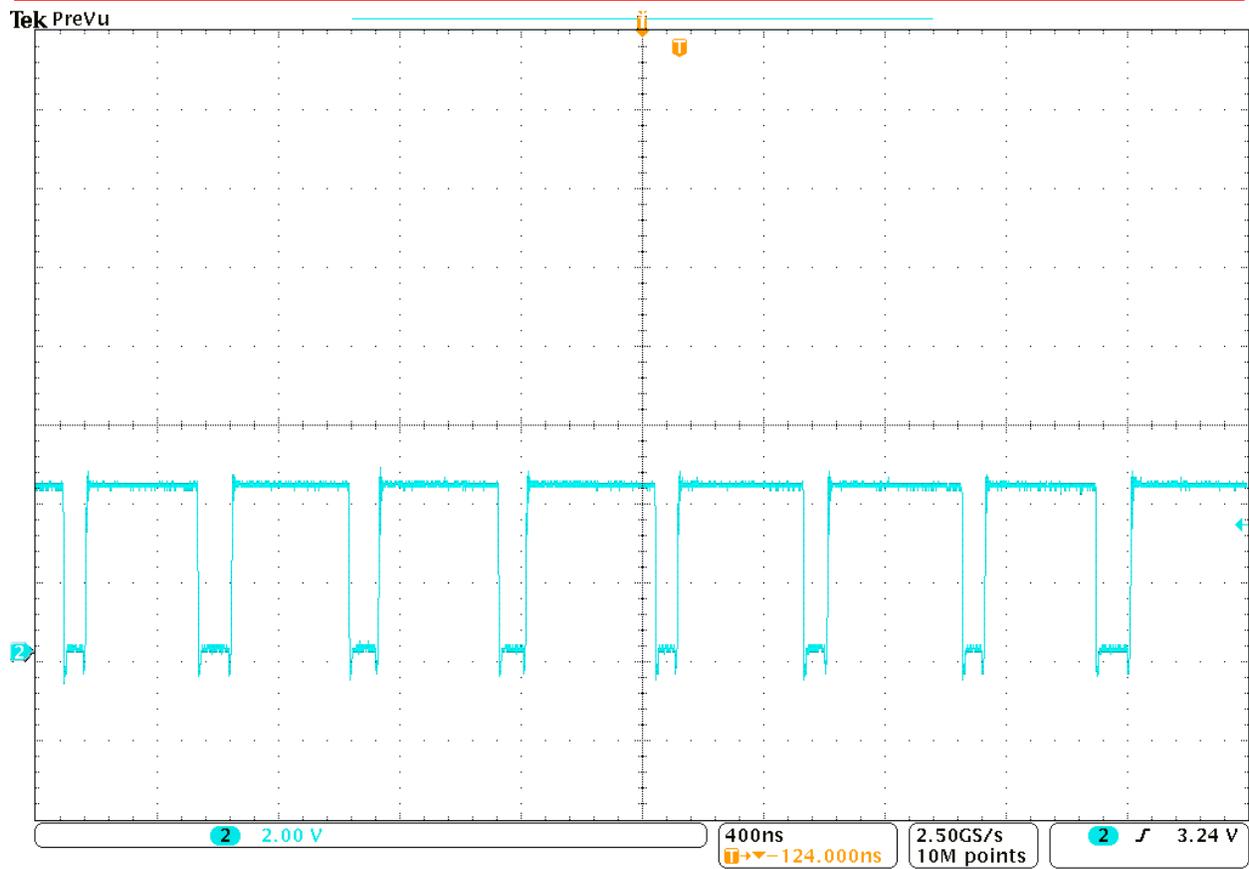

4.5Vin 3.3Vo Io=3.5A

## 6.4 Reverse Polarity Protection

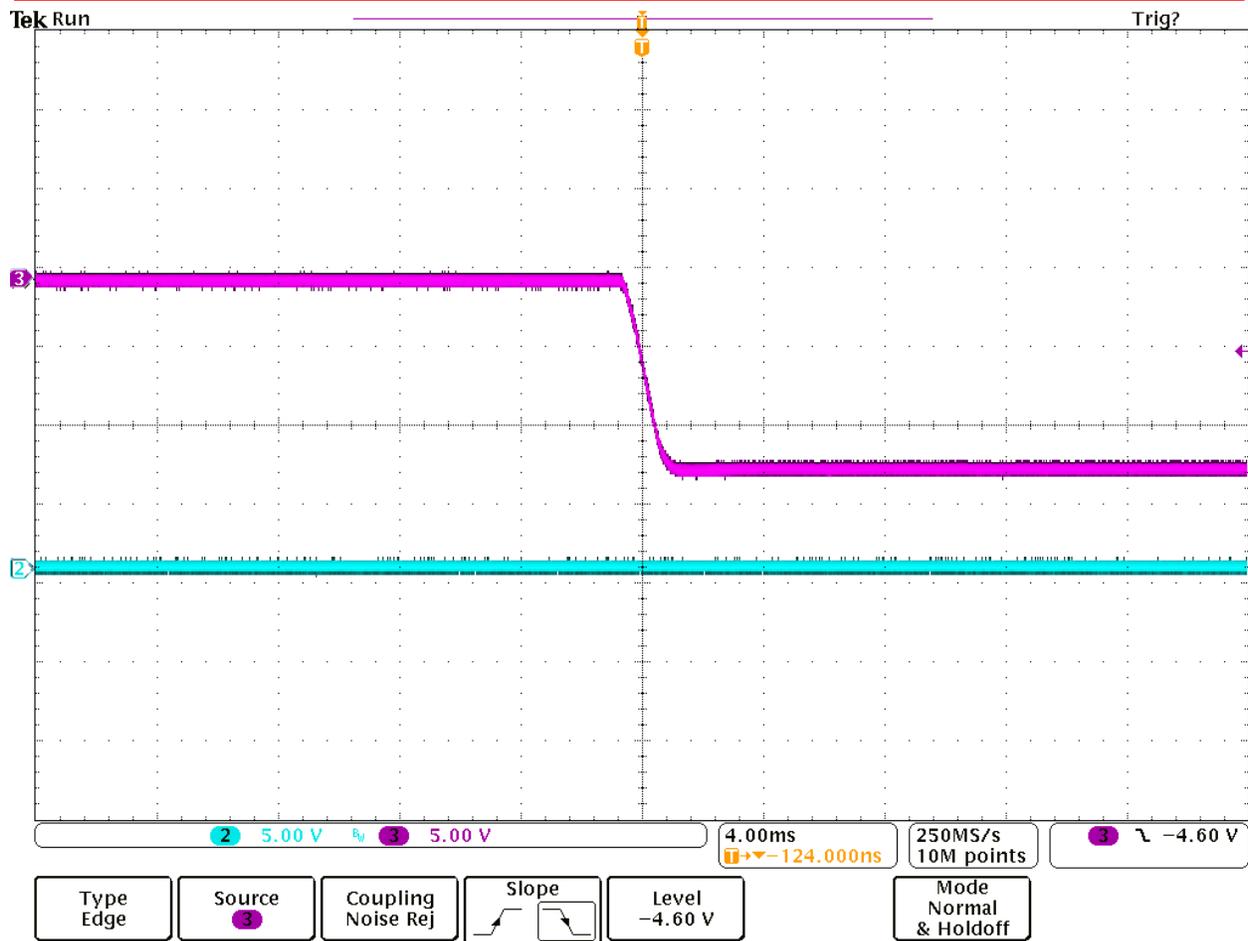

-12Vin added at the input port(CH3: Battery voltage, Ch2: Input voltage of LM53635)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated