

TI Designs: PMP9806

Accurate Output Current Limit Circuit Reference Design for TPS61088 Boost Converter



Description

The PMP9806 reference design delivers an accurate output current-limit solution for the TPS61088 boost converter. This feature is made possible by utilizing an output current sense resistor and an operational amplifier for low cost applications. When the output current exceeds the current limit point, the output of the operational amplifier increases to a voltage higher than the TPS61088 1.204-V reference voltage, which causes the output voltage to drop. If the output current continues to increase, the output voltage decreases further in response. This configuration ensures that the maximum output power is always limited below a certain level.

Features

- 2.7-V to 4.2-V Input Voltage Range
- 5-V/3-A, 9-V/2-A, and 12-V/1.5-A Output Capabilities
- Accurate Output Current Limit
- Limited Maximum Output Power
- Small Solution Size; Easy to Implement

Applications



- [Power Banks](#)
- [Limited Maximum Output Power in Boost Converter Applications](#)

Resources

PMP9806	Design Folder
TPS61088	Product Folder
TLV2314	Product Folder



[ASK Our E2E Experts](#)

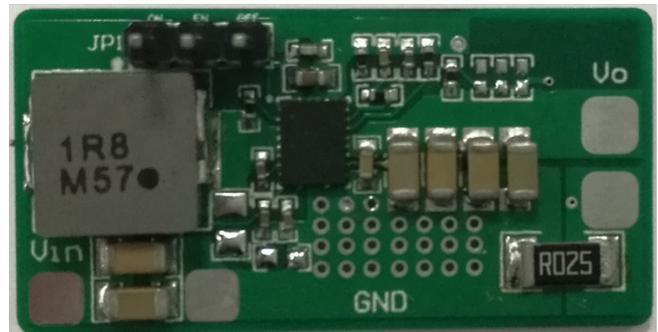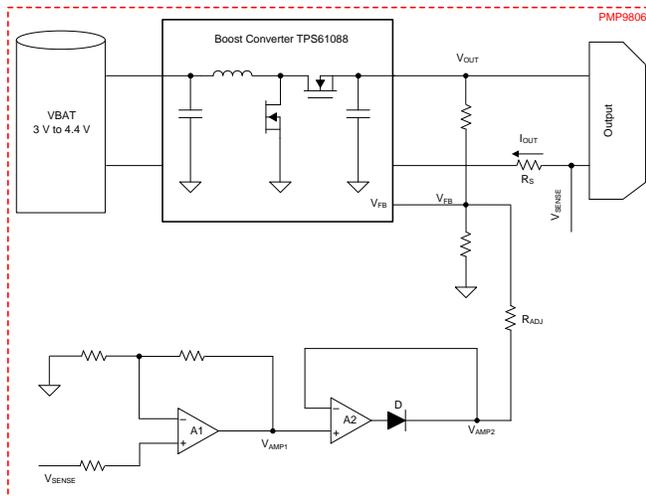

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Description

The latest generation power banks must utilize output power limit functions to avoid the overpower and overheating problems that occur during usage. Overheating is not allowable per Quick Charge 3.0 requirements.

The synchronous boost converter TPS61088 is widely used in quick charge power bank applications. This converter implements cycle-by-cycle current limit to protect the device from overload conditions during boost switching. This current limit function is realized by detecting the current flowing through the low-side MOSFET and has an approximate $\pm 10\%$ precision. The maximum output power varies significantly if designers utilize the current limit function of the TPS61088 itself. The part with a higher current limit threshold generates more heat in the overload conditions and some parts encounter overheating problems.

The PMP9806 reference design delivers an accurate output current-limit solution for the TPS61088 boost converter. This feature is made possible by utilizing an output current sense resistor and an operational amplifier for low cost applications. When the output current exceeds the current limit point, the output of the operational amplifier increases to a voltage higher than the TPS61088 1.204-V reference voltage and causes the output voltage to drop. If the output current continues to increase, the output voltage decreases further in response. This configuration ensures that the maximum output power is always limited below a certain level. The TLV2314 is a low-cost, small packaged operational amplifier. The PMP9806 reference design offers a cost effective and compact solution for power bank applications.

1.1 Key System Specifications

[Table 1](#) provides the performance specification of this reference design. When the output current is higher than the setting point, the output voltage drops.

Table 1. Performance Specifications

INPUT VOLTAGE	OUTPUT VOLTAGE AND OUTPUT CURRENT	OUTPUT CURRENT LIMIT POINT
3 V to 4.2 V	9 V, 2 A	$I_o \geq 2.1$ A
	5 V, 3 A	$I_o \geq 3.15$ A
	12 V, 1.5 A	$I_o \geq 1.575$ A


2 System Overview

2.1 Block Diagram

Figure 1 shows the block diagram of the PMP9806 reference design. A shunt resistor, R_S , is placed in the output return and this resistor converts the output current to a voltage signal V_{SENSE} . The operational amplifier, A1, senses the voltage V_{SENSE} across the shunt resistor R_S and provides a magnified voltage, V_{AMP1} , to the amplifier A2.

When the output current is lower than the current limit point, V_{AMP1} is lower than the 1.204-V reference voltage of the TPS61088 device, the diode D cannot conduct, and resistor R_{ADJ} is floating. The boost converter functions per usual.

When the output current is higher than the current limit point, V_{AMP1} exceeds the 1.204-V reference voltage of the TPS61088 device and diode D conducts. Voltage V_{AMP2} is equal to the voltage V_{AMP1} ; so, V_{FB} increases and the output voltage V_{OUT} drops. If the output current continues to increase, the output voltage decreases further. Thus the maximum output power always remains limited below a certain level.

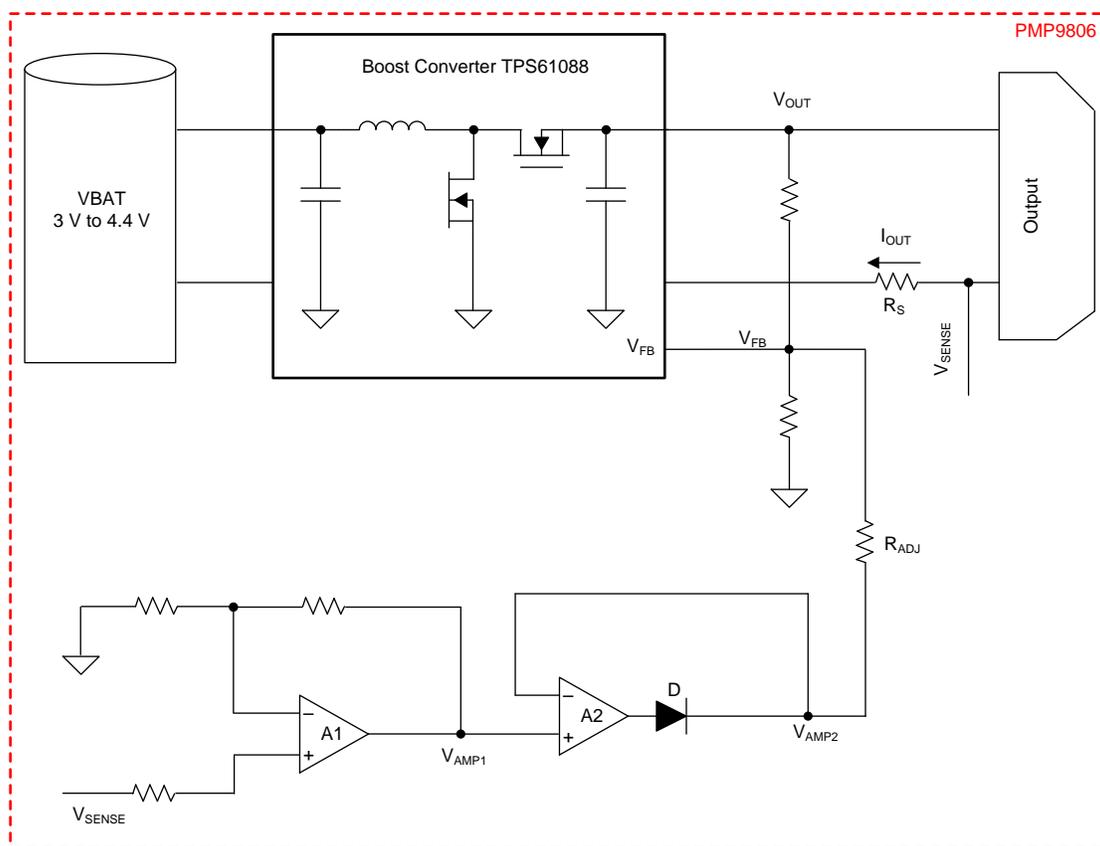

Copyright © 2017, Texas Instruments Incorporated

Figure 1. PMP9806 Block Diagram

2.2 System Design Theory

This section provides the PMP9806 output current limit circuit design. For the power components and compensation network calculation, see the [TPS61088 10-A Fully-Integrated Synchronous Boost Converter](#) datasheet[1].

2.2.1 Setting Current Limit Point

The output current limit point must be higher than the maximum output current. In this reference design, the maximum output current is 3 A when $V_O = 5\text{-V}$ condition, 2 A when $V_O = 9\text{-V}$ condition, and 1.5 A when $V_O = 12\text{-V}$ condition. Set the output current limit point to 3.15 A, 2.1 A, and 1.575 A, respectively, to avoid the current limit circuit from false triggering during normal output current conditions.

2.2.2 Shunt Resistor Selection

The use of a shunt resistor is the most versatile and cost-effective means to measure the current. The voltage across this resistor must be kept to a low value to reduce the power loss. In this reference design, the shunt resistor value, R_S , has been selected as 25 m Ω . The maximum continuous current, I_{O_MAX} , which flows through the shunt resistor is 3.15 A when $V_O = 5\text{-V}$ condition. So the maximum shunt voltage, V_{SENSE_MAX} , can be calculated using the following Equation 1:

$$V_{SENSE_MAX} = R_S \times I_{O_MAX} \quad (1)$$


The minimum power rating, P_{RATING} , of the shunt resistor can be calculated using the following Equation 2:

$$P_{RATING} = V_{SENSE_MAX} \times I_{O_MAX} \quad (2)$$

Using the previous equation, the minimum power rating of the shunt resistor is calculated as 0.248 W in this reference design. A general rule of thumb is to multiply this minimum power rating by 2. Therefore, TI recommends that the designer choose a $\geq 0.5\text{-W}$ resistor in this reference design to make it more robust in the overload or output short-circuit condition.

2.2.3 Output Current Limit Circuit Design

Figure 2 shows the output current limit circuit in this reference design. The current sense signal V_{SENSE} is connected to the non-inverting input of A1 through R15.

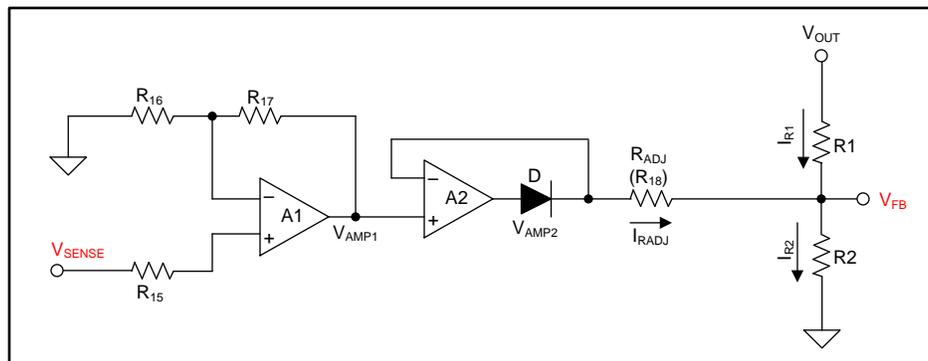

Copyright © 2017, Texas Instruments Incorporated

Figure 2. Output Current Limit Circuit

During the theoretical calculation (using the 9-V, 2-A output condition for example) of this reference design, the designer sets the operational amplifier A1 output voltage (V_{AMP1}) to 1.204 V when the output current is 2.1 A. This setting is 5% higher than the 2-A maximum normal output current.

When the output current increases to the targeted transition point of 2.1 A, the voltage V_{SENSE} at the non-inverting positive input of A1 is calculated as the following Equation 3 shows:

$$V_{SENSE} = R_S \times I_{O_MAX} = 52.5 \text{ mV} \quad (3)$$

To make V_{AMP1} equal to 1.204 V, the designer must rearrange the equation as follows in Equation 4:

$$V_{SENSE} \times \frac{R_{17} + R_{16}}{R_{16}} = V_{AMP1} \quad (4)$$

This rearrangement results in the following [Equation 5](#):

$$\frac{R_{17} + R_{16}}{R_{16}} = \frac{V_{AMP1}}{V_{SENSE}} = \frac{1.204}{0.0525} = 22.93 \quad (5)$$

So select $R_{17} = 232 \text{ k}\Omega$ and $R_{16} = 10.5 \text{ k}\Omega$ in this reference design.

When the output current is higher than 2.1 A, V_{AMP1} exceeds the 1.204-V reference voltage of the TPS61088 device, the diode D conducts. This action causes V_{FB} to increase and the output voltage V_{OUT} to drop. The output voltage dropout is controlled by the resistor R_{ADJ} . The relationship between the output voltage V_{OUT} to the resistor R_{ADJ} can be deduced by the following [Equation 6](#) through [Equation 9](#):

$$I_{RADJ} + I_{R1} = I_{R2} \quad (6)$$

$$I_{RADJ} = \frac{(V_{AMP2} - V_{FB})}{R_{ADJ}} \quad (7)$$

$$I_{R1} = \frac{V_O - V_{FB}}{R1} \quad (8)$$

$$I_{R2} = \frac{V_{FB}}{R2} \quad (9)$$

Insert [Equation 7](#), [Equation 8](#), and [Equation 9](#) into [Equation 6](#) to obtain the following [Equation 10](#):

$$V_O = V_{FB} + \left(\frac{V_{FB}}{R2} - \frac{(V_{AMP2} - V_{FB})}{R_{ADJ}} \right) \times R1 \quad (10)$$

Set the V_O to 6.5 V at a 3-A output current condition to limit the output power below a certain level, which results in the following [Equation 11](#):

$$R_{ADJ} = \frac{(V_{AMP2} - V_{FB})}{\frac{V_{FB}}{R2} - \frac{(V_O - V_{FB})}{R1}} \approx 169 \text{ k} \quad (11)$$

where,

- $V_{AMP2} = V_{AMP1} = V_{SENSE} \times (R_{17} + R_{16}) / R_{16} = 1.73 \text{ V}$ when $I_O = 3 \text{ A}$
- $R1 = 768 \text{ k}$
- $R2 = 120 \text{ k}$.

If set the V_O to 5.5 V when at a 3-A output current condition, $R_{ADJ} = 121 \text{ k}$.

3 Test Results

3.1 Start-Up Waveforms

Figure 3 shows the start-up waveforms of the inductor current and the output voltage at $V_{IN} = 3.3\text{ V}$ and $I_o = 2\text{-A}$ condition.

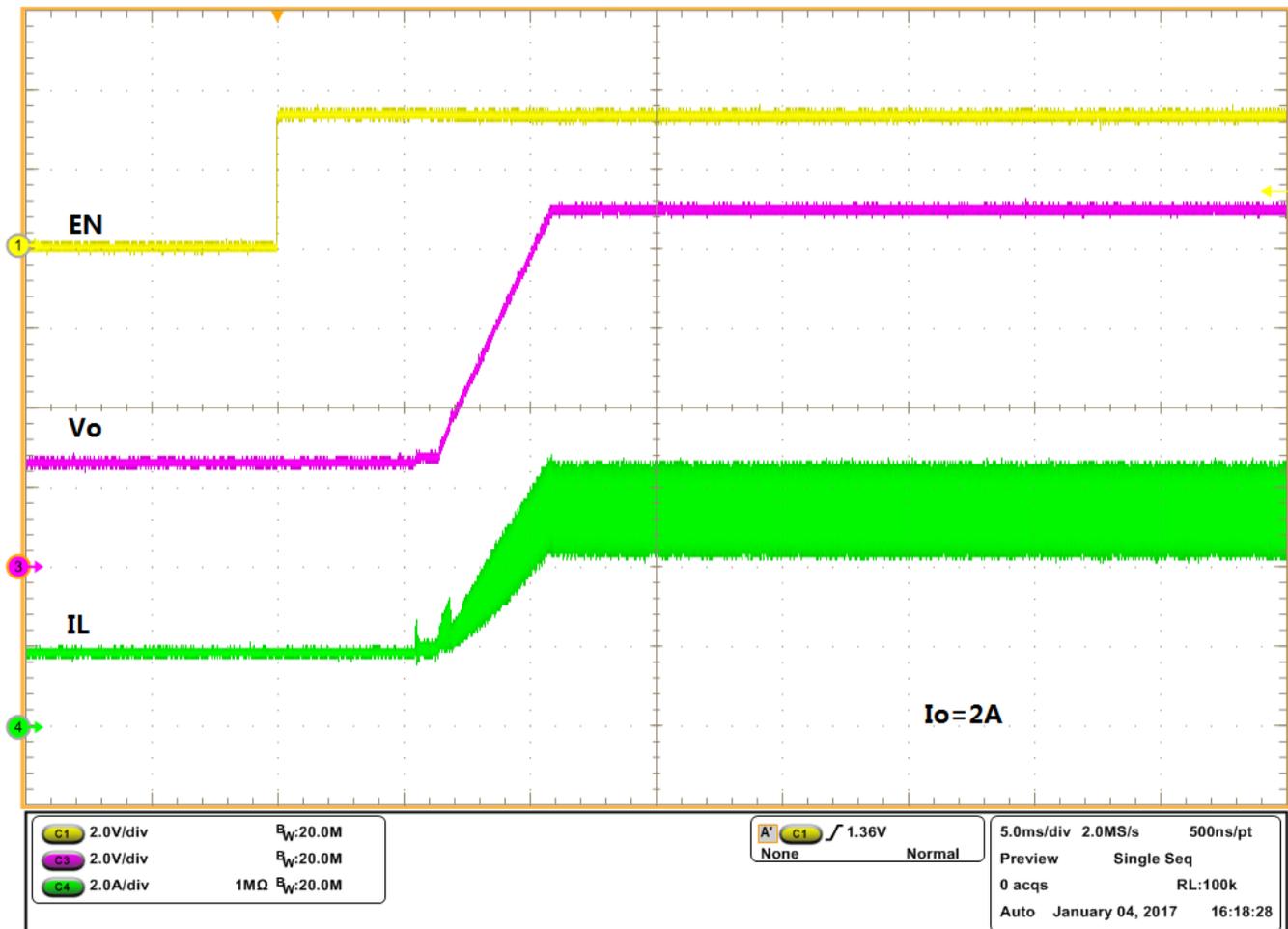


Figure 3. Start-up Waveforms at $I_o = 2\text{ A}$ ($V_o = 9\text{ V}$)

Figure 4 shows the start-up waveforms of the inductor current and the output voltage at $V_{IN} = 3.3\text{ V}$ and $I_o = 3\text{-A}$ condition. As the output current is higher than the current limit point, the boost converter enters into the current limit mode after start-up. The output voltage after start-up is 6.2 V .

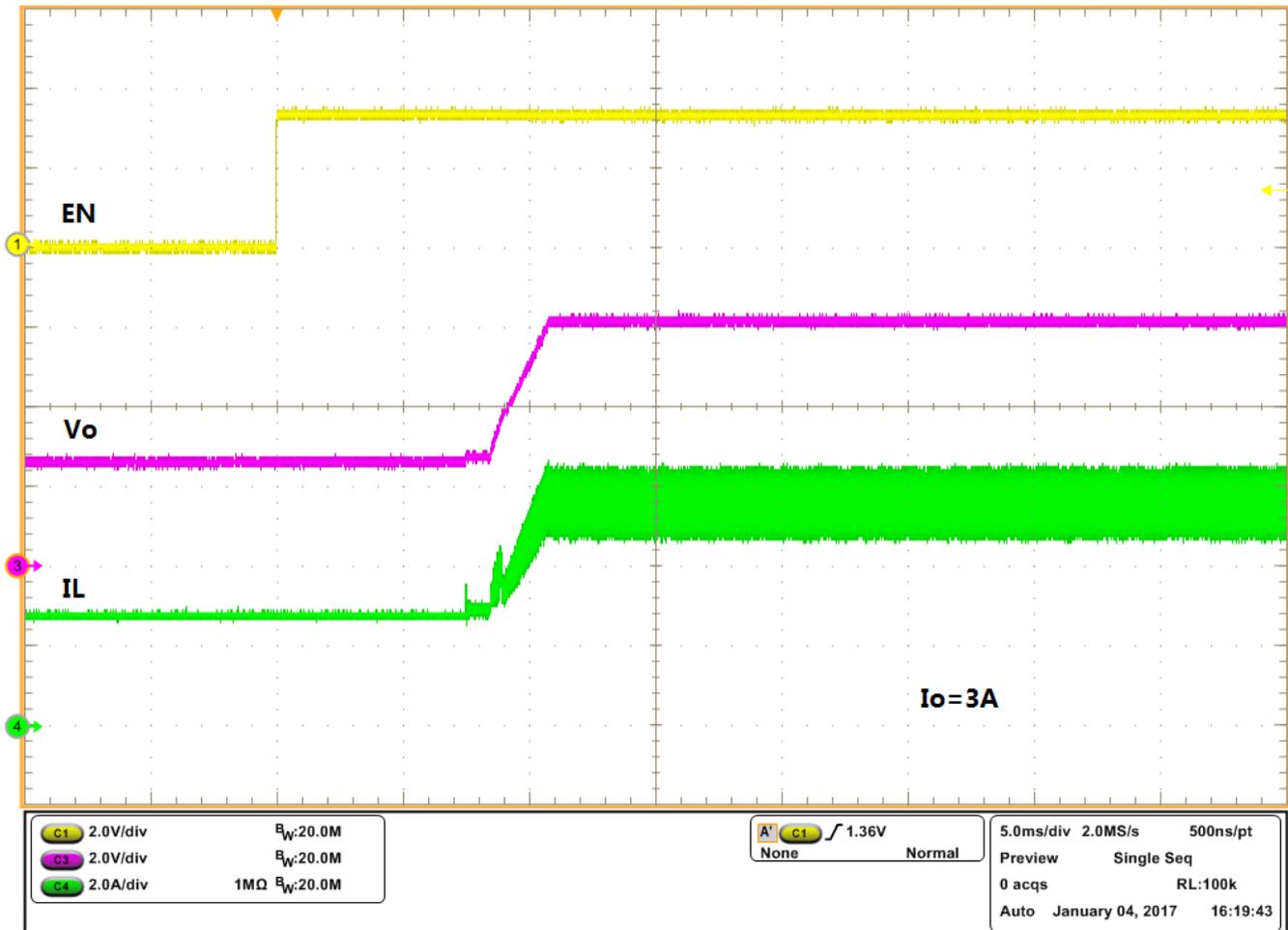


Figure 4. Start-up Waveforms at $I_o = 3\text{ A}$ ($V_o = 9\text{ V}$)

3.2 Output Current Limit Waveforms

Figure 5 shows the output current limit waveforms at $V_o = 9\text{-V}$ condition. From the waveforms of the output voltage, output current, and the inductor current, the designer can observe that the output voltage drops from 9 V to 6.2 V within 50 μs when the output current suddenly increases from 2 A to 3 A.

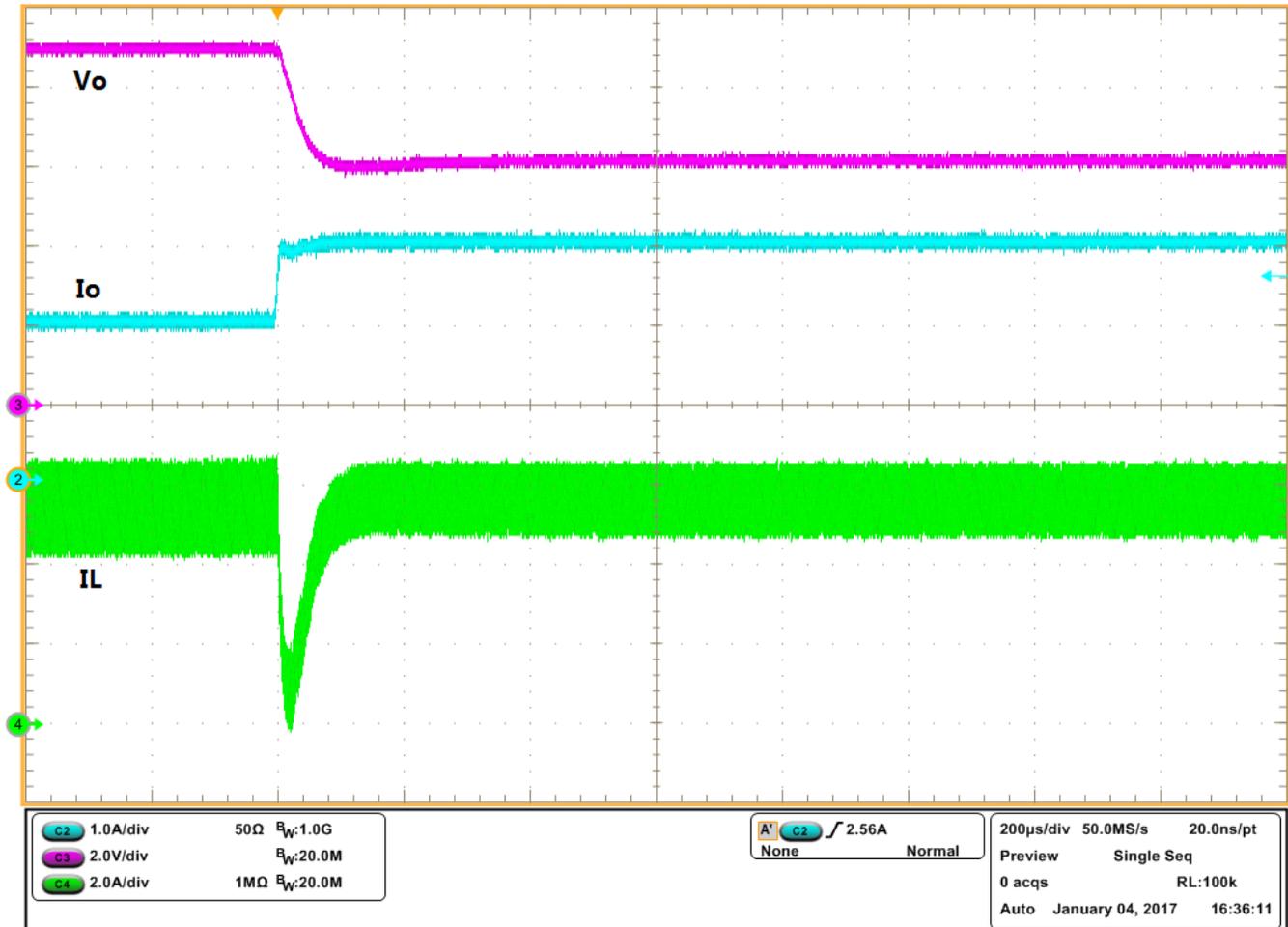


Figure 5. Output Current Limit Waveforms at $V_o = 9\text{ V}$ ($I_o = 2\text{ A}$ to 3 A)

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [PMP9806](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [PMP9806](#).

4.3 Altium Project

To download the Altium project files, see the design files at [PMP9806](#).

4.4 Gerber Files

To download the Gerber files, see the design files at [PMP9806](#).

4.5 Assembly Drawings

To download the assembly drawings, see the design files at [PMP9806](#).

5 Related Documentation

1. Texas Instruments, [TPS61088 10-A Fully-Integrated Synchronous Boost Converter](#), TPS61088 Datasheet (SLVSCM8)

5.1 Trademarks

All trademarks are the property of their respective owners.

6 About the Author

HELEN CHEN is an application engineer on the Texas Instruments BMC-BCS team. She brings more than 12 years of experience in power supply product design. Helen started her career as an AC-DC server power design engineer in Delta Power Electronics before joining TI in 2014. Helen specializes in various circuit topologies such as buck, boost, RCC, buck-boost, full-bridge, half-bridge, fly-back, CCM PFC, and DCMB PFC. She also has experience in the magnetic components design, PCB layout, and EMI solutions.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated