

TAS5132DDV2EVM

Fred Shipley

Digital Audio and Video Products

ABSTRACT

The TAS5132V2EVM PurePath Digital™ customer evaluation module (EVM) demonstrates the integrated circuits TAS5086PAG and TAS5132DDV from Texas Instruments (TI). This application report covers the EVM specifications, audio performance and power efficiency measurements graphs, and design documentation that includes schematics, parts list, layout, and mechanical design.

Contents

1	Introduction	2
2	TAS5132V2EVM Specification.....	3
3	Component Notes	9
4	References	10

List of Figures

1	TAS5132DDV2EVM Evaluation Module.....	2
2	THD+N vs Power (BTL – 6Ω).....	4
3	THD+N vs Power (BTL – 8Ω).....	5
4	THD+N vs Frequency (BTL – 8Ω).....	5
5	FFT Spectrum With –60 dBFS Tone (BTL)	6
6	Idle Noise FFT Spectrum (BTL)	6
7	Channel Separation	7
8	Frequency Response (BTL)	7
9	High-Current Protection (BTL)	8
10	Pop/Click (BTL)	8
11	Output Stage Efficiency	9

List of Tables

1	General Test Conditions	3
2	TAS5086 Register Settings	3
3	Electrical Data.....	3
4	Audio Performance	3
5	Thermal Specification	4
6	Physical Specifications.....	4

1 Introduction

The TAS5132V2EVM PurePath Digital™ customer evaluation module (EVM) demonstrates the integrated circuits TAS5086PAG and TAS5132DDV from Texas Instruments (TI).

TAS5086DBT is a high-performance, 32-bit (24-bit input) multichannel PurePath Digital™ pulse width modulator (PWM) based on Equibit™ technology with fully symmetrical AD modulation scheme. The device also has digital audio processing (DAP) that provides 48-bit signal processing, advanced performance, and a high level of system integration.

The TAS5132DDV is a high-performance, integrated stereo Digital Amplifier Power Stage designed to drive 8-Ω speakers at up to 20 W per channel. Incorporating TI's Equibit™ technology, the device is designed to be used with TI's Equibit™ modulators. This system requires only a simple passive demodulation filter to deliver high-quality, high-efficiency audio amplification. This EVM is configured with two BTL channels.

This EVM is a complete 2-channel digital audio amplifier system which includes digital input (S/PDIF), interface to PC and DAP features like digital volume control, input and output multiplexers, and bass management. The EVM is designed to demonstrate the functionality of the TAS5132DDV in a minimum component size/count scenario. Therefore, the TAS5132DDV is capable of better performance than this EVM demonstrates; however, increased performance comes at increased price.

This 2.0 system is designed for applications such as television and plasma display panels (PDP).

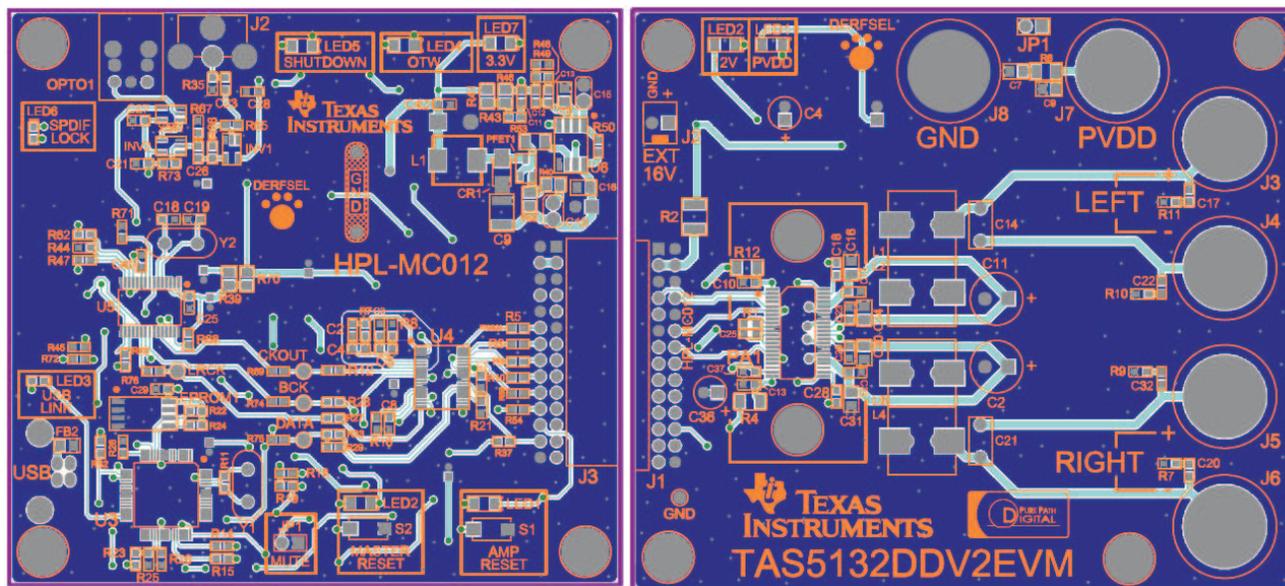


Figure 1. TAS5132DDV2EVM Evaluation Module

For EVM setup and use, see *TAS5132V2EVM User's Guide* ([SLLU097](#)).

The following sections of this document cover EVM specifications, audio performance and power efficiency measurements graphs, and design documentation that includes schematics, parts list, layout, and mechanical design.

2 TAS5132V2EVM Specification

Table 1. General Test Conditions

General Test Conditions		Notes
Output stage supply voltage: System supply voltage:	18 V	Laboratory power supply (Agilent 6574A) Derived from Output Stage Supply; GVDD = 12 V
Load impedance :	6-8 Ω	
Sampling frequency	48 kHz	
PWM processor	TAS5086DBT	
Output stage	TAS5132DDV	PG1.1
TI input-USB board	HPLMC012	Rev 1
EVM configuration file	Version 1.00	TAS5132EVM.cfg

Table 2. TAS5086 Register Settings⁽¹⁾

Register	Register	Value	Notes
Modulation index limit register	0x10	0x04	Set modulation index set to 96.1%
Master volume register	0x07	0x30	Master volume set to 0 dB
Clock control register	0x00	0x6D	48-kHz sample rate; 256 FS MCLK frequency
OSC_TRIM register	0x1B	0x03	Select field trim
PWM start register	0x18	0x3F	Start channels as part of system start
Split cap charge period register	0x1A	0x00	Split-capacitor charge time = 0 ms
System control register 2	0x05	0x20	All channels started; VALID1 = VALID2

⁽¹⁾ These register settings are used for all test, unless otherwise specified.

Table 3. Electrical Data

Electrical Data		Notes/Conditions
Output power, BTL, 6 Ω :	18 W	1 kHz, unclipped (0 dBFS), $T_A = 25^\circ\text{C}$
Output power, BTL, 6 Ω :	25 W	1 kHz, 10% THD+N, $T_A = 25^\circ\text{C}$
Output power, BTL, 8 Ω :	15 W	1 kHz, unclipped (0 dBFS), $T_A = 25^\circ\text{C}$
Output power, BTL, 8 Ω :	21 W	1 kHz, 10% THD+N, $T_A = 25^\circ\text{C}$
Rated load impedance, BTL:	6-8 Ω	
Rated load impedance, PBTL:	3-8 Ω	
Maximum peak current, BTL:	>5 A	1-kHz burst, 3 Ω , $R_{OC} = 22k$
Output stage efficiency:	>90 %	2x20 W, 8 Ω
System supply current:	<110 mA	1 kHz, -60-dBFS signal, with TI input board
H-Bridge supply current:	<33 mA	1 kHz, no signal, 10- μH output inductors

Table 4. Audio Performance

Audio Performance			Notes/Conditions
THD+N, BTL, 6 Ω :	1 W	< 0.05%	1 kHz
THD+N, BTL, 6 Ω :	10 W	< 0.06%	1 kHz
THD+N, BTL, 6 Ω :	20 W	< 0.1%	1 kHz
THD+N, BTL, 8 Ω :	1 W	< 0.05%	1 kHz
THD+N, BTL, 8 Ω :	10 W	< 0.05%	1 kHz
THD+N, BTL, 8 Ω :	15 W	< 0.09%	1 kHz
Dynamic range:		> 108 dB	Reference: rated power, A-weighted, AES17 filter
Noise voltage:		< 35 μV_{rms}	A-weighted, AES17 filter

Table 4. Audio Performance (continued)

Audio Performance		Notes/Conditions
Click/pop, BTL:	< 20 mV	Mute/unmute, no input signal, 8 Ω
Channel separation	> 60 dB	1 kHz, P _{OUT} = 20 W
Frequency response:	± 2 dB	15 W/ 8 Ω, unclipped (0 dBFS)


Table 5. Thermal Specification

Thermal Specification	T _{PCB} ⁽¹⁾	Notes/Conditions
Idle, all channels switching	<30°C	1 kHz, 15 minutes, -60-dBFS signal, T _A = 25°C
2 x 1.875 W, 8 Ω, (1/8 power)	<35°C	1 kHz, 1 hour, T _A = 25°C
2 x 15 W, 8 Ω, (full power)	<50°C	1 kHz, 5 minutes, T _A = 25°C

⁽¹⁾ Measured on component side of PCB, under the heat sink.


Table 6. Physical Specifications

Physical Specifications		Notes/Conditions
PCB dimensions (in mm)	200 × 100 × 25	HPLMC012-TAS5132EVMV2 total dimension
TAS5132V2EVM Amplifier Module	100 x 100 × 25	Width × length × height (mm) (power stage section = 27 mm × 50 mm)
HPL-MC012 Modulator/Controller Module Total weight	<1 kg	Components + PCB + heat sink + mechanics

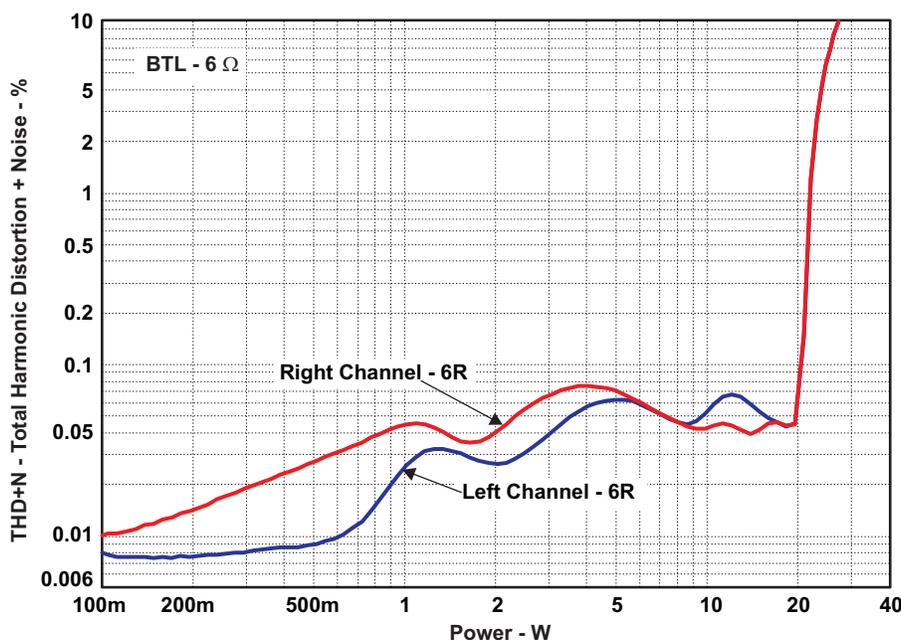


Comments: Power supply: 18 Vdc Load: 6 Ω Filter: AES17
 Input signal: 1 kHz +2.5-dB gain in TAS5086 Sample frequency: 48 kHz
 One trace for each channel, one channel loaded, the other muted

Figure 2. THD+N vs Power (BTL – 6Ω)

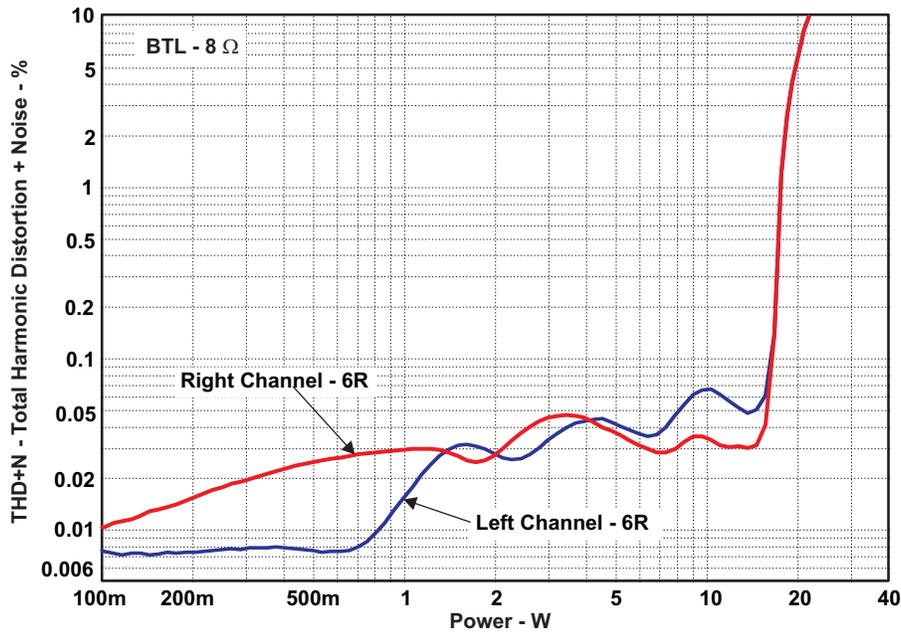

Comments: Power supply: 18 Vdc Load: 8 Ω Filter: AES17
 Input signal: 1 kHz +2.5-dB gain in TAS5086 Sample frequency: 48 kHz
 One trace for each channel, one channel loaded, the other muted


Figure 3. THD+N vs Power (BTL – 8Ω)

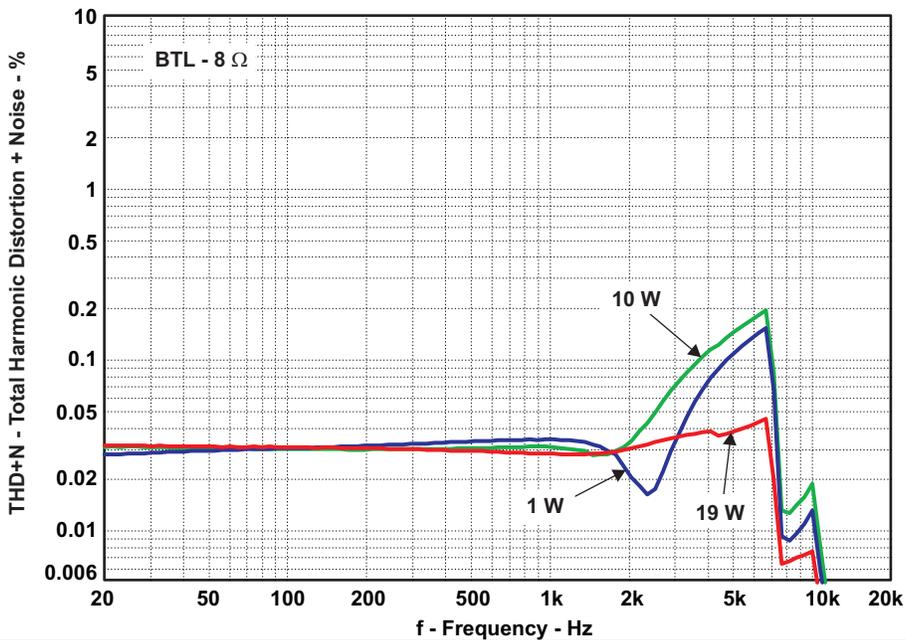

Comments: Blue: 1 W Green: 10 W Red: 19 W Sample frequency: 48 kHz
 Power supply: 18 Vdc Load: 8 Ω Filter AES17


Note: THD+N at high frequencies depend on the output-filter coil material.

Figure 4. THD+N vs Frequency (BTL – 8Ω)

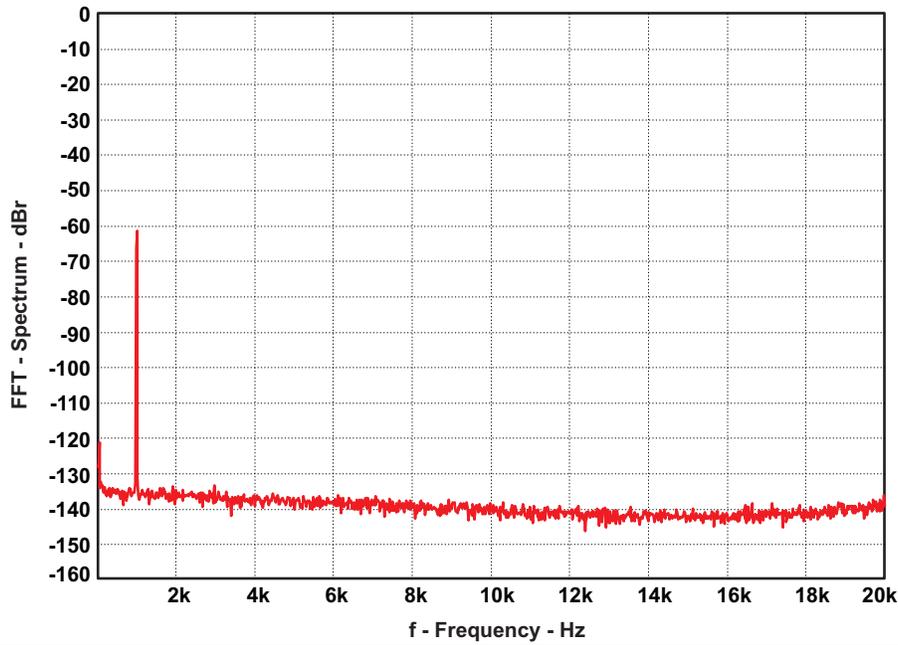


Comments: Power supply: 18 Vdc Load: 8 Ω Filter: AES17 Reference: 0 dBFS
 Input signal: 1 kHz Sample frequency: 48 kHz FFT size: 16k

Figure 5. FFT Spectrum With -60 dBFS Tone (BTL)

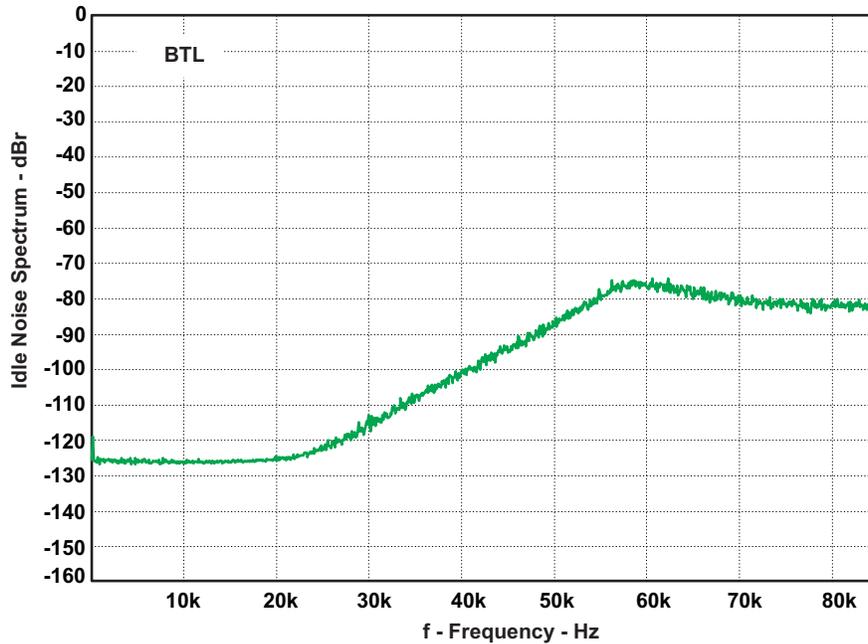


Comments: Power supply: 18 Vdc Load: 8 Ω FFT size: 16k Reference: 0 dBFS
 Input signal: Mute Sample frequency: 48 kHz Auto mute disabled – none

Figure 6. Idle Noise FFT Spectrum (BTL)

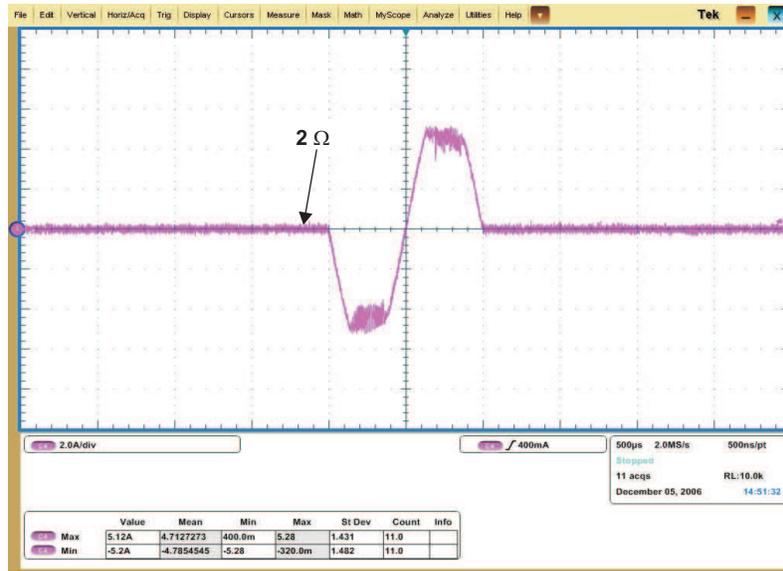


Comments: Green: 6 Ω Input signal: 1 kHz Sample frequency: 48 kHz Power supply: 18 Vdc

Figure 9. High-Current Protection (BTL)

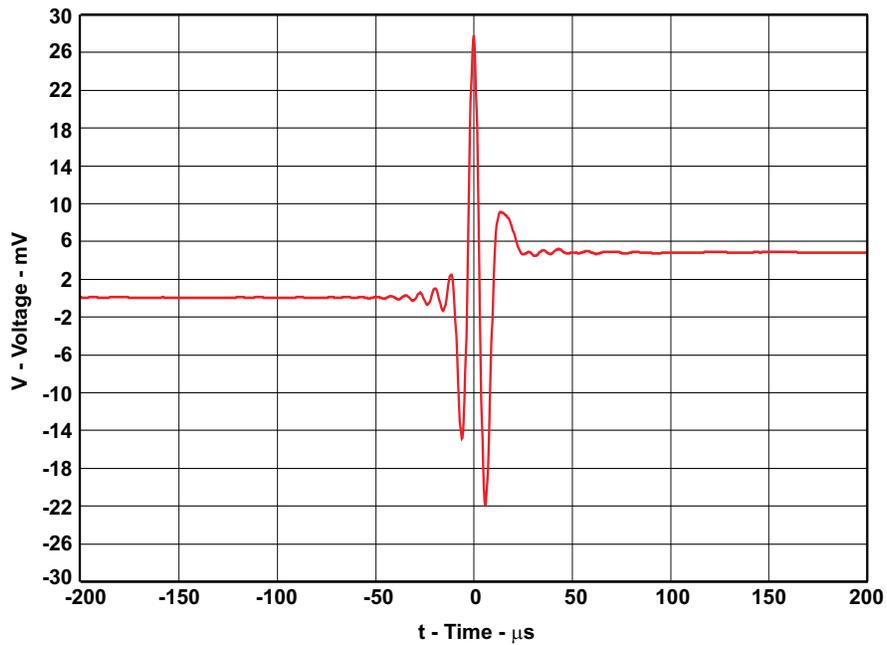

Comments: Load: 8 Ω Input signal: 1 kHz Sample frequency: 48 kHz Power supply: 18 Vdc

Figure 10. Pop/Click (BTL)

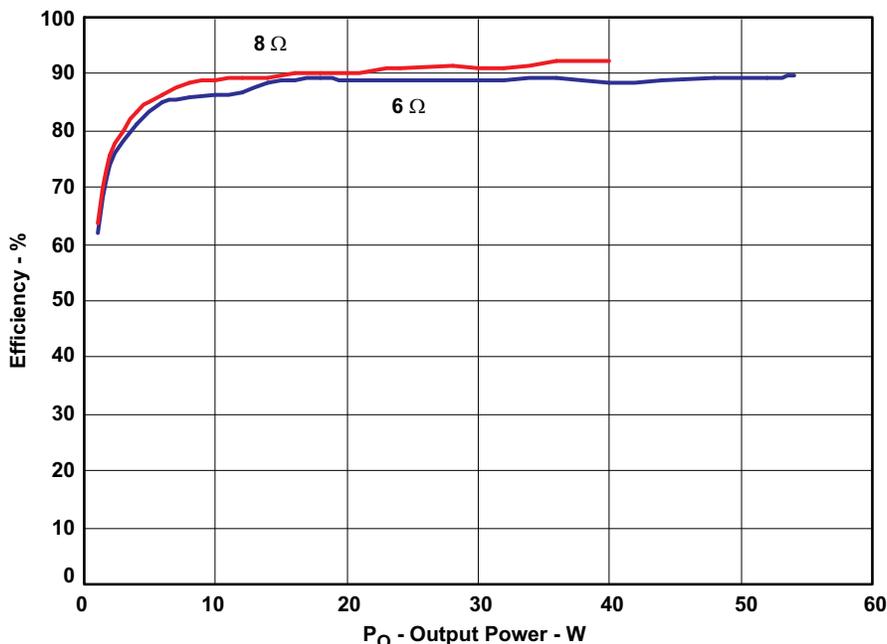

Comments: Stereo Power Output (BTL) Power supply: 18 Vdc
 BTL Load: 6 Ω and 8 Ω Sample frequency: 48 kHz Input signal: 1 kHz

Figure 11. Output Stage Efficiency

3 Component Notes

3.1 PVDD Capacitors

The PVDD capacitors, 220 μF at 25 V were chosen to reject power supply noise and keep crosstalk below -60 dB from 20 Hz to 20 KHz. Good-quality, low-ESR capacitors should be selected to reduce the possibility of excessive noise at the amplifier's output and to keep crosstalk within the Dolby Specification of -60 dB within the audio band. These capacitors can be increased, if necessary.

3.2 Output Filter Inductors

The inductors were selected to form part of the output LC demodulation filter. They have dc resistance <50 mΩ and an inductance of 10 μH. This inductance can be increased to 16 μH to provide a lower frequency cutoff for the demodulation filter. As long as the inductance remains stable for peak current within the power band, the inductor should not present problems, as long as it provides adequate residual inductance during an output error condition to protect the amplifier (short-circuit protection).

3.3 Output Filter Capacitors

Good-quality film capacitors should be used for the 0.47-μF capacitors used in the output demodulation filter. They should have a voltage rating of not less than 2 times the PVDD supply voltage.

4 References

1. *System Design Considerations for True Digital Audio Power Amplifiers* application report ([SLAA117](#))
2. *Digital Audio Measurements* application report ([SLAA114](#))
3. *TAS5086: 6 Channel Digital Audio PWM Processor* data sheet ([SLES131](#))
4. *TAS5132: Stereo Digital Amplifier Power Stage* data sheet ([SLES190](#))
5. *PSRR for PurePath Digital Audio Amplifiers* application report ([SLEA049](#))
6. *Power Rating in Audio Amplifier* application report ([SLEA047](#))
7. *PurePath Digital AM Interference Avoidance* application report ([SLEA040](#))
8. *Click & Pop Measurements Technique* application report ([SLEA044](#))
9. *Power Supply Recommendations for DVD-Receivers* application report ([SLEA027](#))
10. *TAS5132DDV2 User's Guide* ([SLLU097](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
Low Power Wireless	www.ti.com/lpw

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated