

Bart Stiller

Since its definition in 1983, RS-485 has become the preferred interface standard for many industrial fieldbus applications. In this RS-485 basics series on the new TI E2E Community Industrial Strength Blog, we hope to create present a useful, informative, and centralized resource for understanding the fundamentals of RS-485 and addressing common application guestions that arise when designing RS-485 networks.

RS-485, formally known as American National Standards Institute (ANSI) Telecommunications Industry Association (TIA)/Electronic Industries Alliance (EIA)-485-A, is a balanced data transmission standard for serial communication. RS-485 allows for robust transmission of moderate data rates over long distances in multipoint communication applications, such as factory and building automation, motor control, and other field bus applications.

The RS-485 standard only specifies the electrical characteristics of drivers and receivers; it does not specify a protocol. Many higher-level interface standards reference RS-485 for their physical layer, such as Modicon bus (ModBus), process field bus (ProfiBus), DMX512 and others.

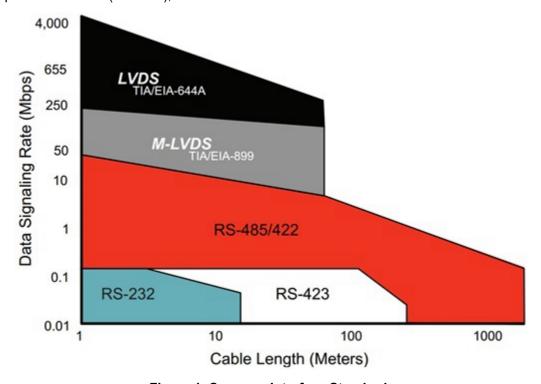


Figure 1. Common Interface Standards

Figure 1 shows the landscape of common interface standards arranged by data rate and distance. RS-485 improves noise immunity and extends the distance supported by RS-232 by implementing a differential, rather than single-ended, signaling technique. And while electrically similar, RS-485 extends RS-422 to allow for bidirectional communication.

Additionally, RS-485 allows for communication over greater distances than multipoint low-voltage differential signaling (M-LVDS) because of its larger signaling levels and wider common-mode range. However, for data rates higher than 20 megabits per second, M-LVDS becomes increasingly advantageous for its reduced power consumption relative to RS-485.

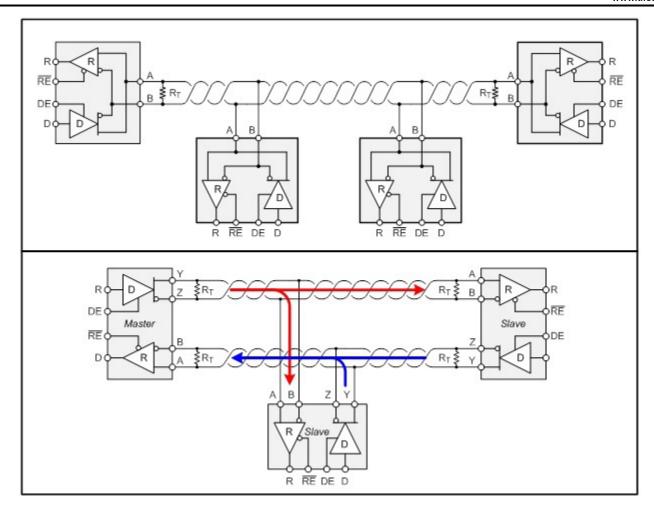


Figure 2. Half- and Full-duplex RS-485 Network Connections

RS-485 networks consist of multiple nodes connected in parallel to a bus. Figure 2 shows the typical network connections for half- and full-duplex RS-485 implementations. The majority of RS-485 applications implement half-duplex (two-wire) communication. Full-duplex communication requires two signal pairs (four-wire), and facilitates higher throughput by allowing nodes to transmit and receive data simultaneously. Modern transceiver designs allow hundreds of nodes to connect to the bus.

The next two installments in this series will discuss the basic design and operation of the RS-485 driver and receiver. We'll also cover receiver failsafe operation, transceiver power dissipation, transient protection and more. If there are topics you would like us to address, please let us know in the comments section.

Additional Resources:

RS-422 and RS-485 Standards Overview and System Configurations, SLLA070D

Dual Isolated Half-Duplex RS-485 Repeater, TIDA-00333

Not all ESD specs cover the IEC ESD strike zone: Look for high IEC61000-4-2 coverage

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2023, Texas Instruments Incorporated