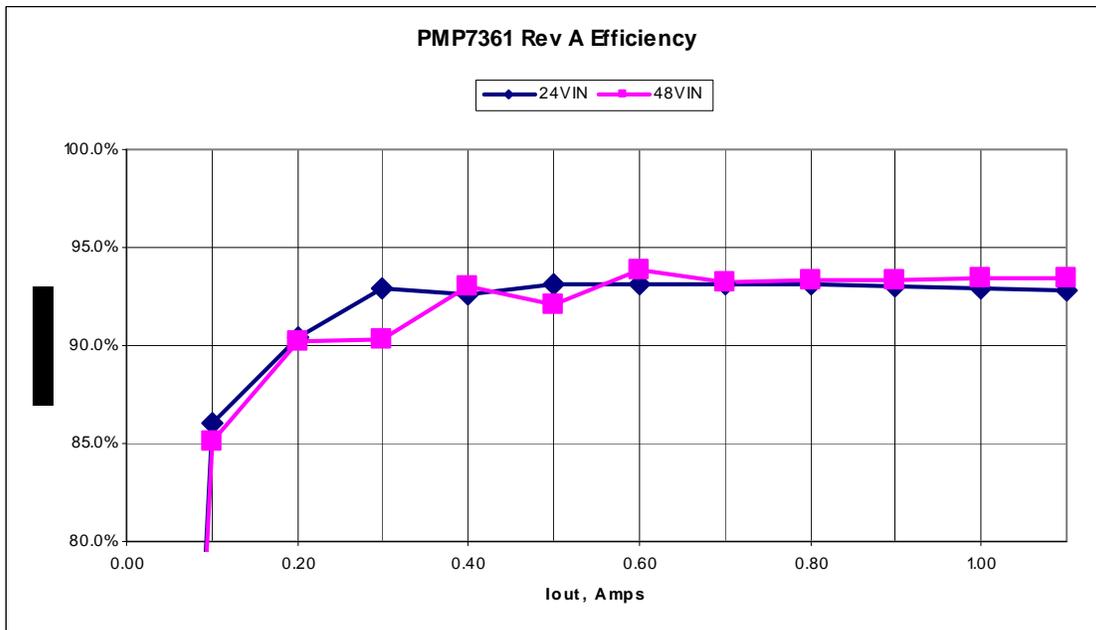


Efficiency

The efficiency of the converter is shown below:


<u>Iout</u>	<u>Vout</u>	<u>J1 lin</u>	<u>J1 Vin</u>	<u>J1 Eff</u>	<u>Vout</u>	<u>J1 lin</u>	<u>J1 Vin</u>	<u>J1 Eff</u>
0.00	53.94	0.025	24.0	0.0%	53.96	0.018	48.0	0.0%
0.10	53.92	0.261	24.0	86.1%	53.93	0.132	48.0	85.1%
0.20	53.92	0.497	24.0	90.4%	53.92	0.249	48.0	90.2%
0.30	53.92	0.725	24.0	93.0%	53.92	0.373	48.0	90.3%
0.40	53.91	0.970	24.0	92.6%	53.91	0.483	48.0	93.0%
0.50	53.91	1.206	24.0	93.1%	53.91	0.610	48.0	92.1%
0.60	53.91	1.447	24.0	93.1%	53.91	0.718	48.0	93.9%
0.70	53.91	1.688	24.0	93.2%	53.91	0.843	48.0	93.3%
0.80	53.91	1.930	24.0	93.1%	53.91	0.963	48.0	93.3%
0.90	53.91	2.174	24.0	93.0%	53.91	1.083	48.0	93.3%
1.00	53.90	2.418	24.0	92.9%	53.91	1.202	48.0	93.4%
1.10	53.90	2.6620	24.0	92.8%	53.91	1.3220	48.0	93.5%




Ripple and Noise

Ripple measurements taken with a 1.1A load and 20MHz BWL.

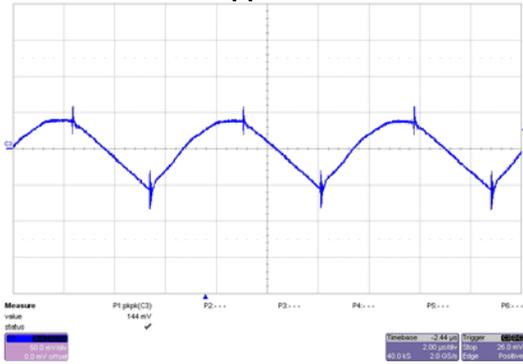
Output ripple across C20, 48Vin
50mV/div; 2usec/div
Measured 144mVpp:



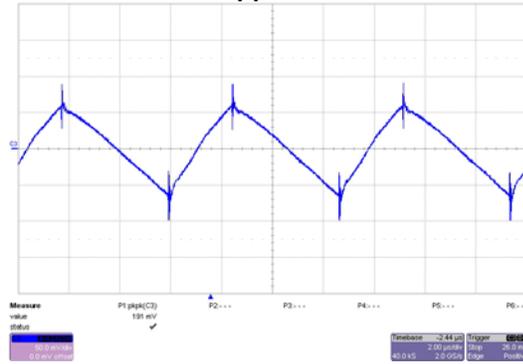
Output ripple across C20, 24Vin
50mV/div; 2usec/div
Measured 191mVpp:



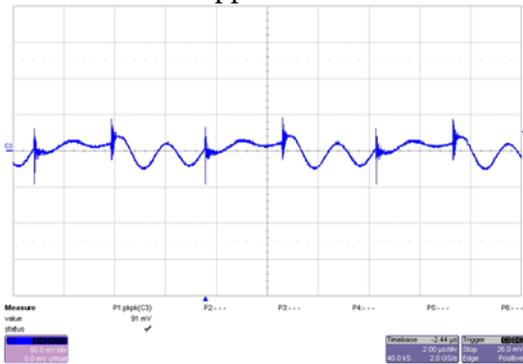Input ripple across J1, 48Vin
50mV/div; 2usec/div
Measured 91mVpp:




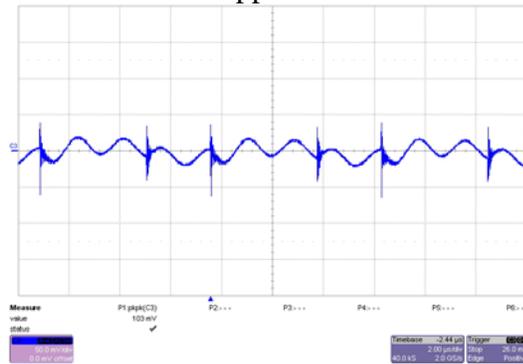Input ripple across J1, 24Vin
50mV/div; 2usec/div
Measured 103mVpp:




Dynamic Loading

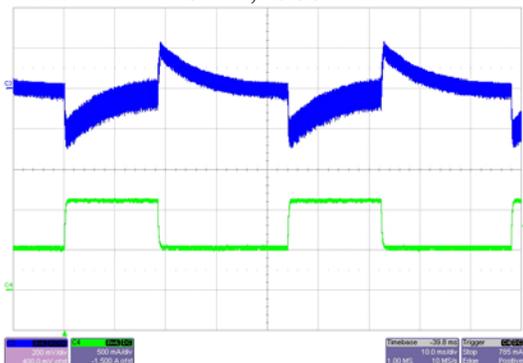Output load step, 0.55A to 1.1A, 48Vin
200mV/div; 0.5A/div; 10msec/div
Measured +240mV; -300mV:




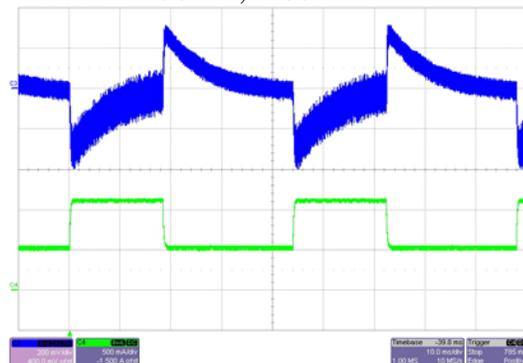Output load step, 0.55A to 1.1A, 24Vin
200mV/div; 0.5A/div; 10msec/div
Measured +30mV; -400mV:




Turn On Response

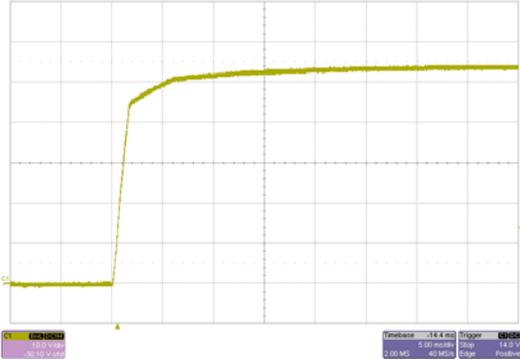Turn-on response: 48Vin, 1.1 load
10V/div; 5msec/div:



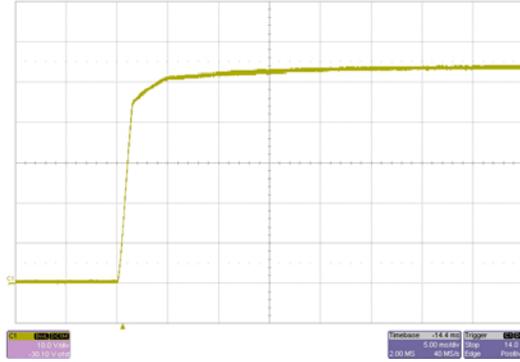
Turn-on response: 48Vin, 0A load
10V/div; 5msec/div:



Turn-on response: 24Vin, 1.1 load
10V/div; 5msec/div:




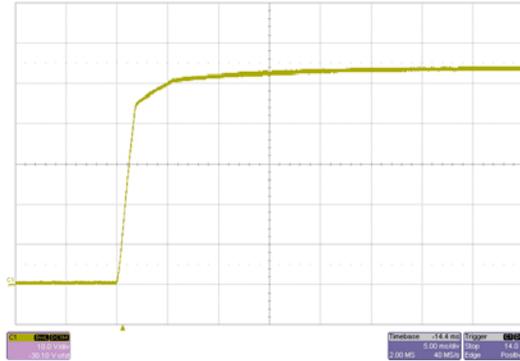Turn-on response: 24Vin, 0A load
10V/div; 5msec/div:




Hold Up Capacitor Charge and Discharge:

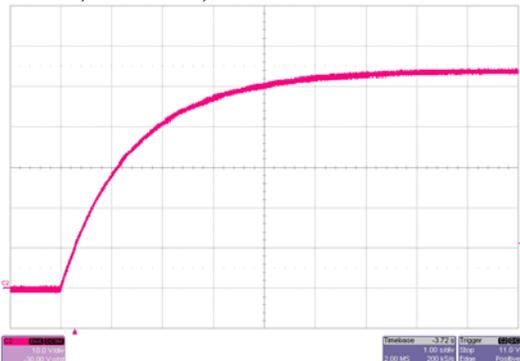
Hold up capacitor charge time
48Vin; 10V/div; 1sec/div:



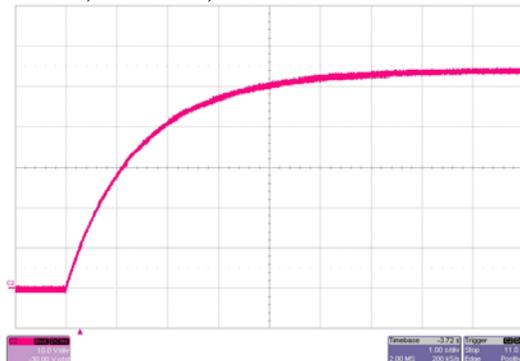
Hold up capacitor charge time
24Vin; 10V/div; 1sec/div:



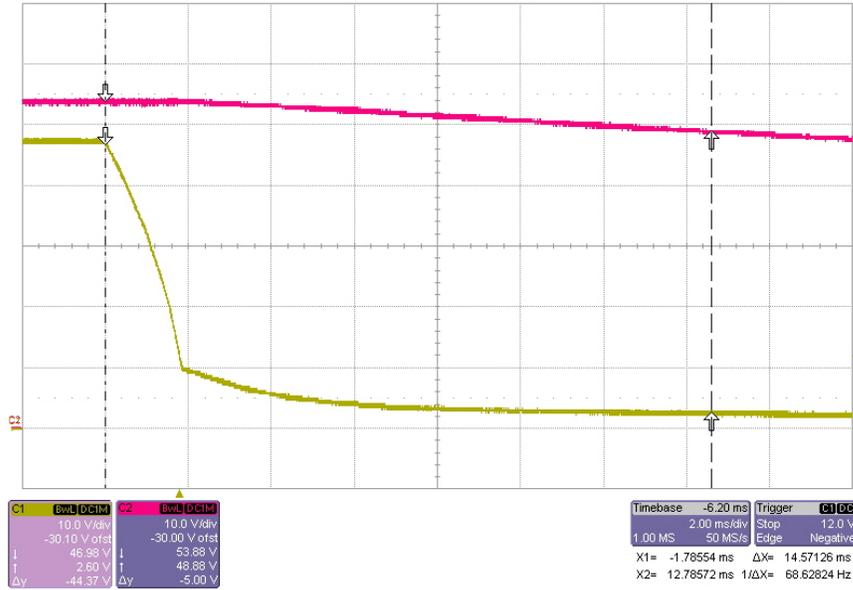Hold up time; 48Vin; 1.1A load
Top: Vout
Bottom: Vin
10V/div; 2msec/div
14.5msec hold up time to 5V droop:




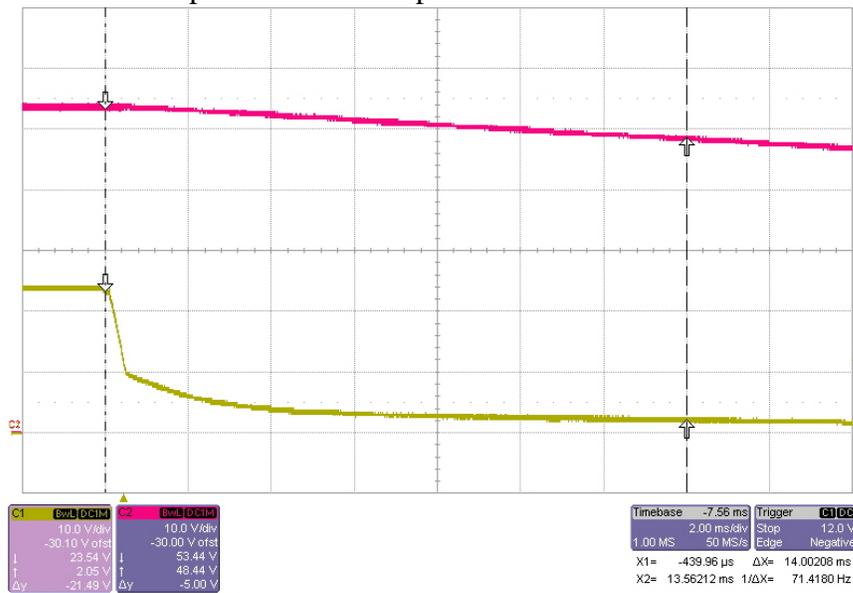Hold up time; 24Vin; 1.1A load
Top: Vout
Bottom: Vin
10V/div; 2msec/div
14msec hold up time to 5V droop:




Stability Analysis (Loop Gain)

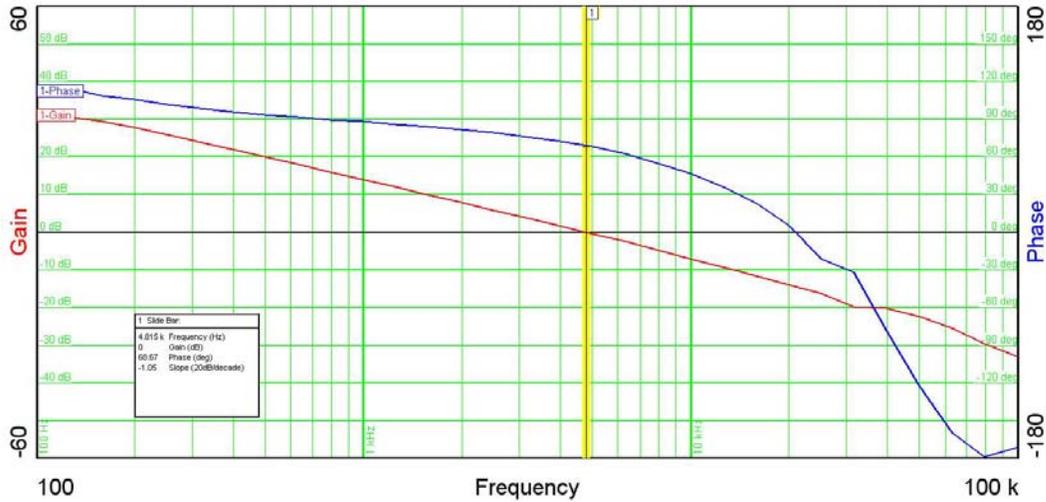The figure below is the loop gain of the converter with a 48V input and a 1.1A load. The Bandwidth is 4.8 KHz, the Phase Margin is 68 degrees, and the Gain Margin is 13 dB.




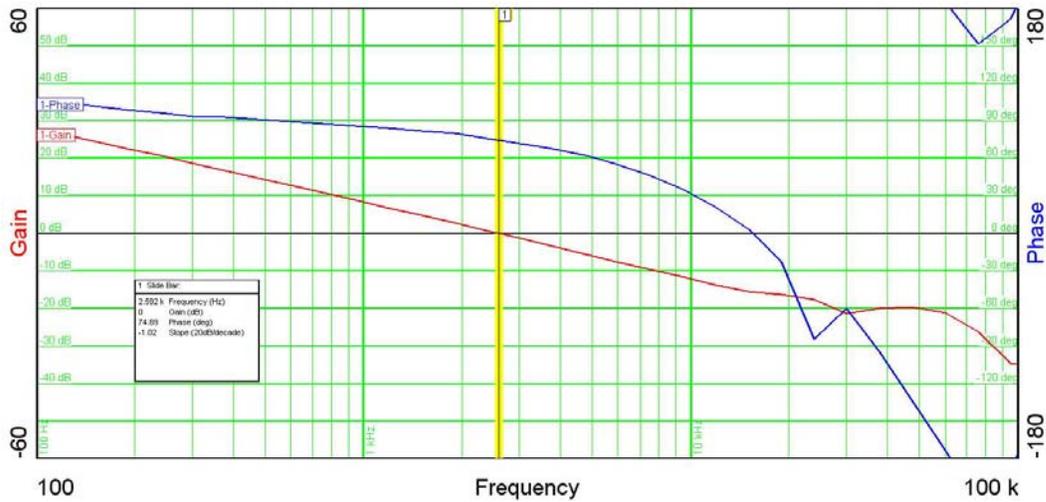The figure below is the loop gain of the converter with a 24V input and a 1.1A load. The Bandwidth is 2.6 KHz, the Phase Margin is 74 degrees, and the Gain Margin is 16 dB.




Thermal Plots


48V input and 1.1A load.

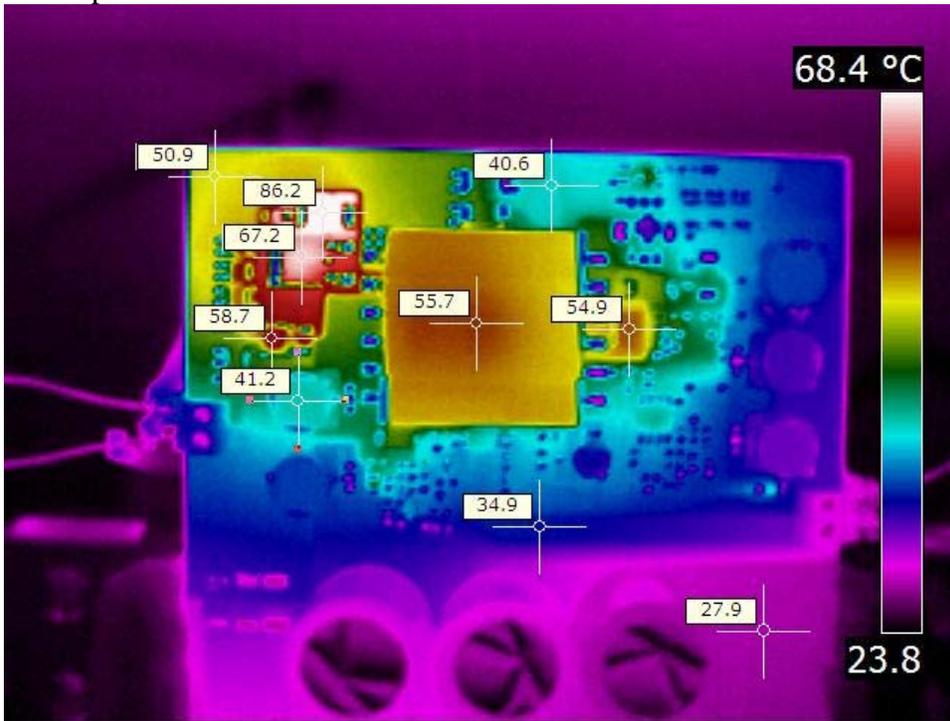

24V input and 1.1A load.

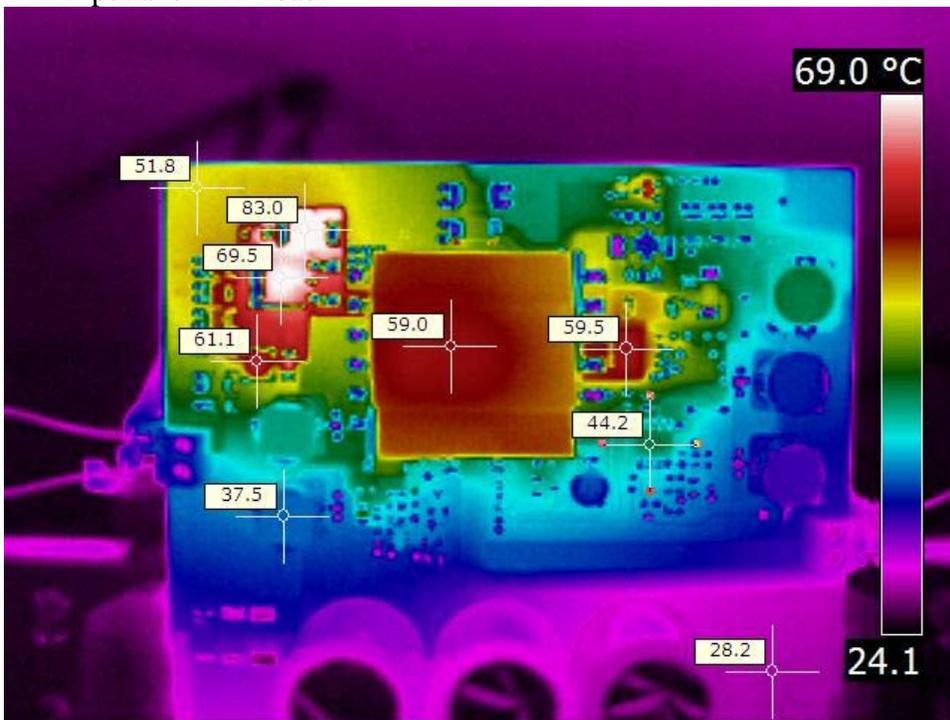

Photo

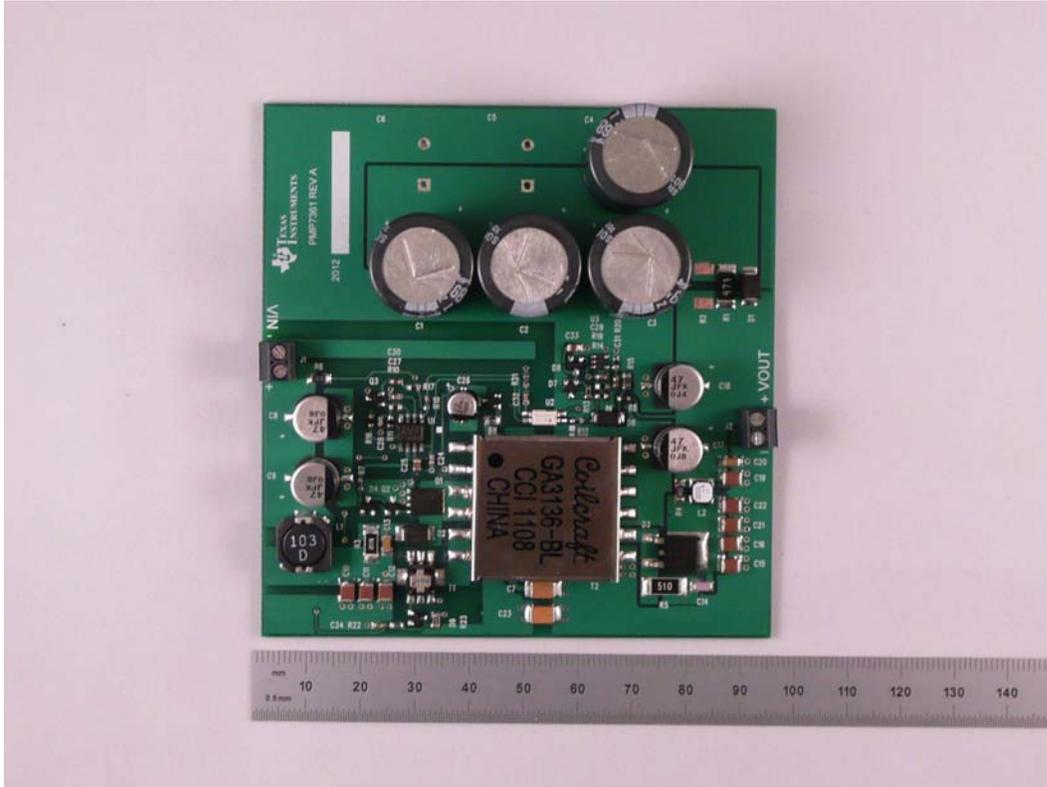

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated